

EE 332: Devices and Circuits II


Lecture 8: Noise

Prof. Sajjad Moazeni

smoazeni@uw.edu


Autumn 2022

Statistical Characteristics of Noise

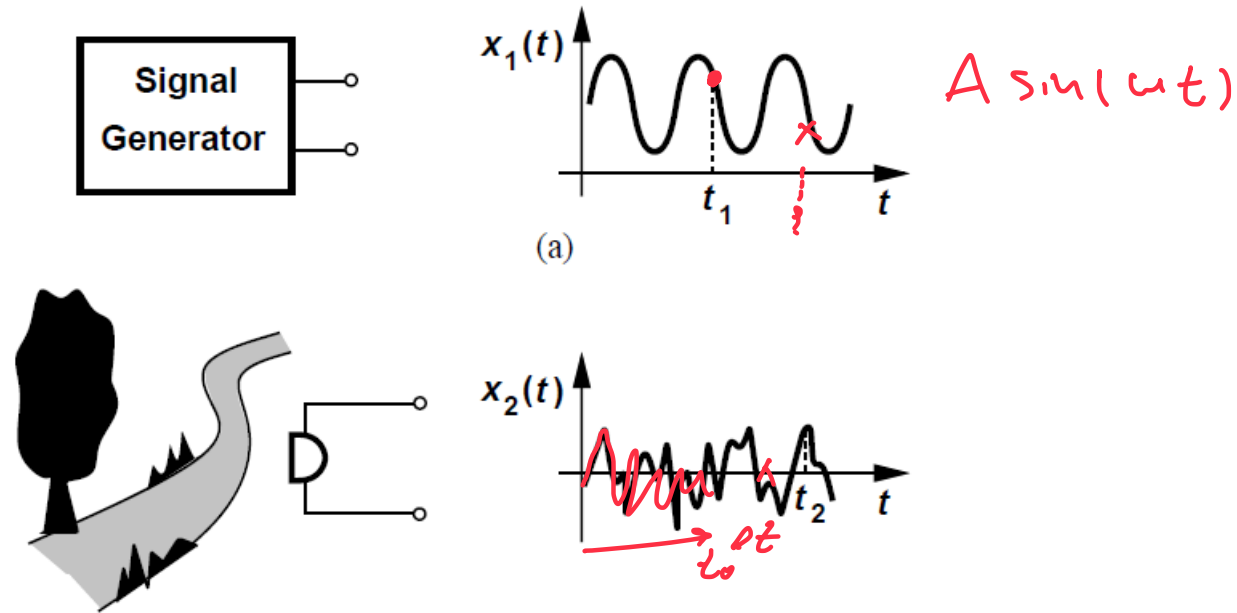


- Noise is a random process
- Value of $x_1(t_1)$ can be predicted from observed waveform, that of $x_2(t_2)$ cannot
 - Difference between deterministic and random phenomena
- Instantaneous value of noise in time domain is unpredictable



Statistical Characteristics of Noise

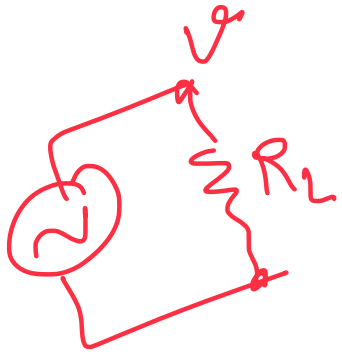

$$P_2 = \frac{v^2}{R_L}$$

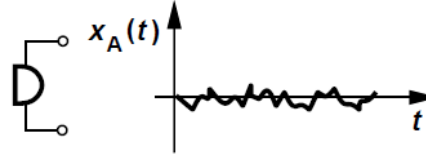


(a)

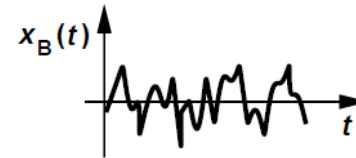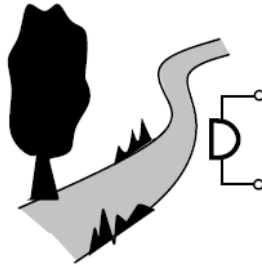

- Need for a “statistical model” for noise
- Average power of noise is predictable
 - Applicable to most sources of noise in circuits
- Average power delivered by a periodic voltage $v(t)$ with period T to a load resistance R_L is defined as

$$P_{av} = \frac{1}{T} \int_{-T/2}^{+T/2} \frac{v^2(t)}{R_L} dt$$

Statistical Characteristics of Noise

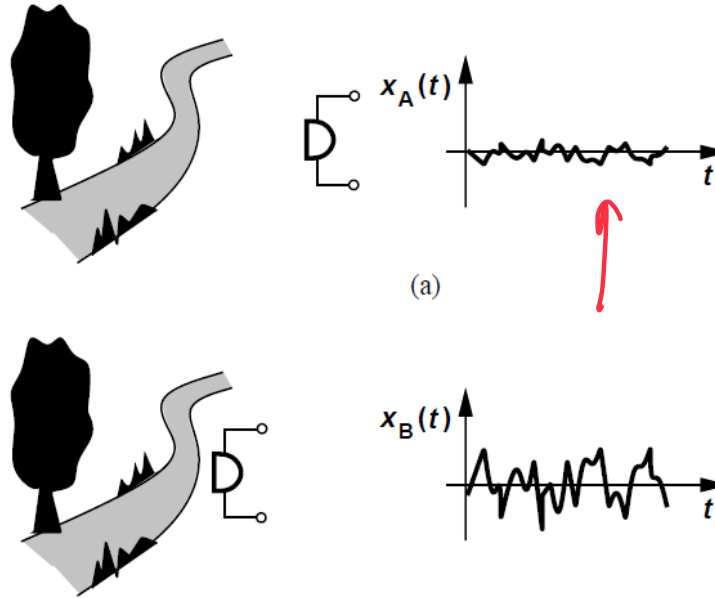

- For a random signal (aperiodic), measurement must be carried out over a long time

Watts $\leftarrow P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{+T/2} \frac{x^2(t)}{R_L} dt$


- $x(t)$ is a voltage quantity
- $x_A(t)$ delivers more power to a resistive load than $x_B(t)$

Statistical Characteristics of Noise

$$A \sin(\omega t)$$

$$\downarrow$$


$$V_{rms} = \frac{A}{\sqrt{2}}$$

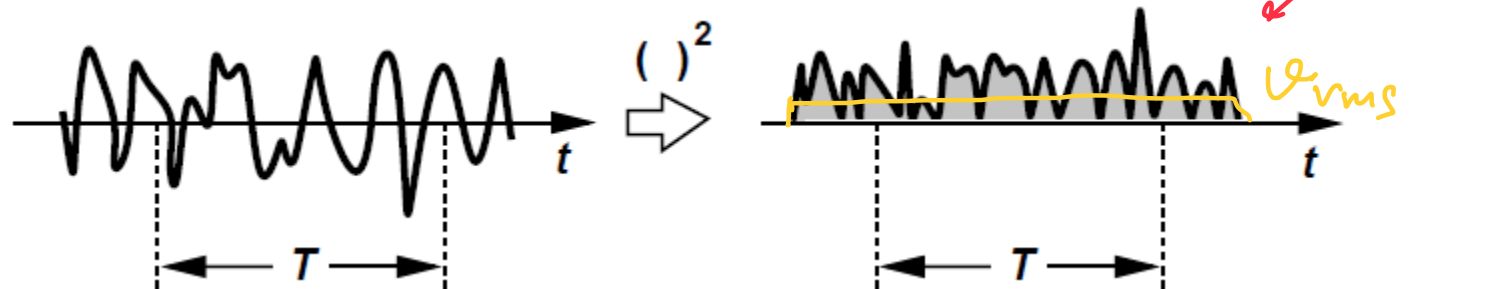


- To calculate average power of (noise) signal $x(t)$
 - Square the signal
 - Find area under resulting waveform for a long period T
 - Normalize area to T
- For simpler calculations, P_{av} is defined as

$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{+T/2} x^2(t) dt$$

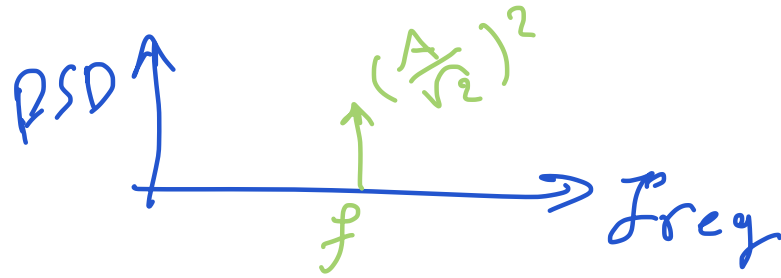
- P_{av} is expressed in V^2 rather than W
- RMS voltage for noise can be defined as $\sqrt{P_{av}} = V_{rms}$



Noise Spectrum

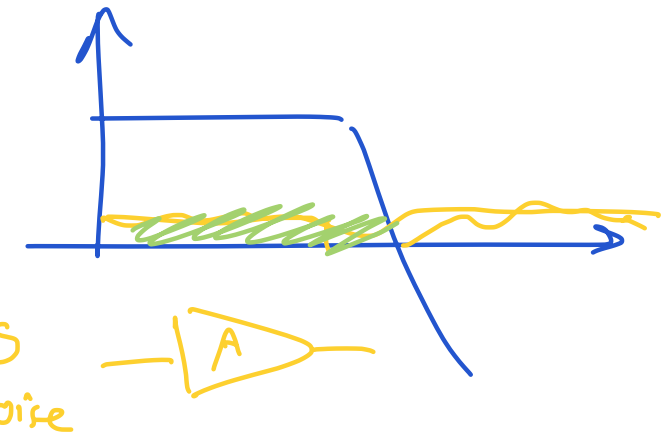


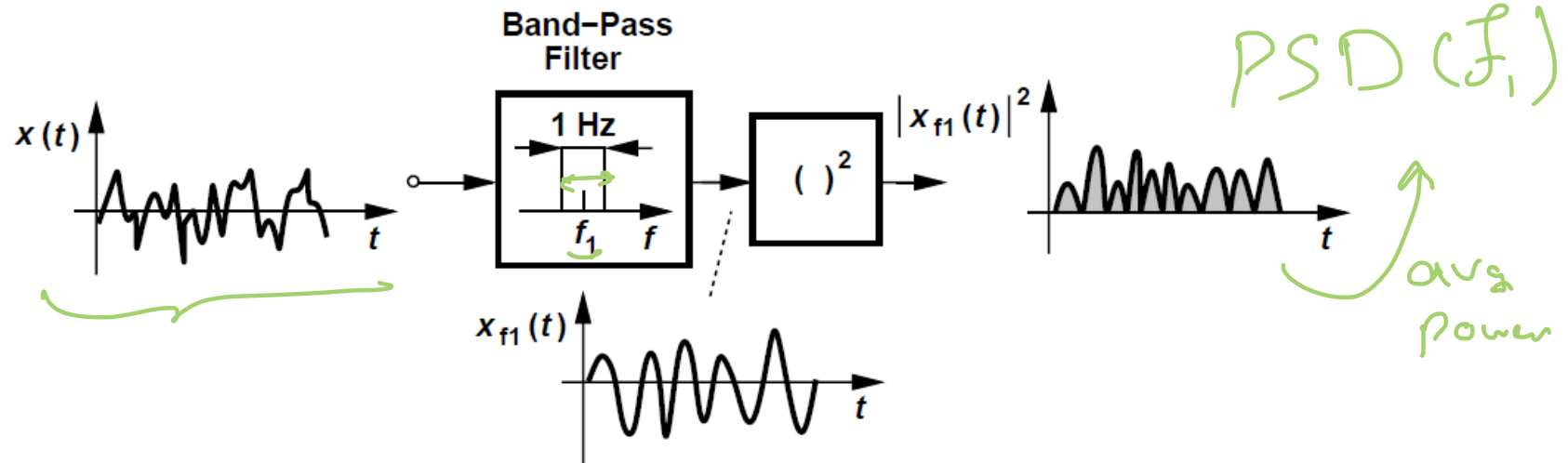- Spectrum describes the *frequency content* of noise
- Also called **Power Spectral Density (PSD)**
 - Shows how much power signal carries at each frequency
- ★ PSD $S_x(f)$ of a noise waveform $x(t)$ is defined as the average power carried by $x(t)$ in a 1-Hz bandwidth around f
- Calculation of $S_x(f_1)$, i.e., power contained in a specific frequency f_1 :



Noise Spectrum

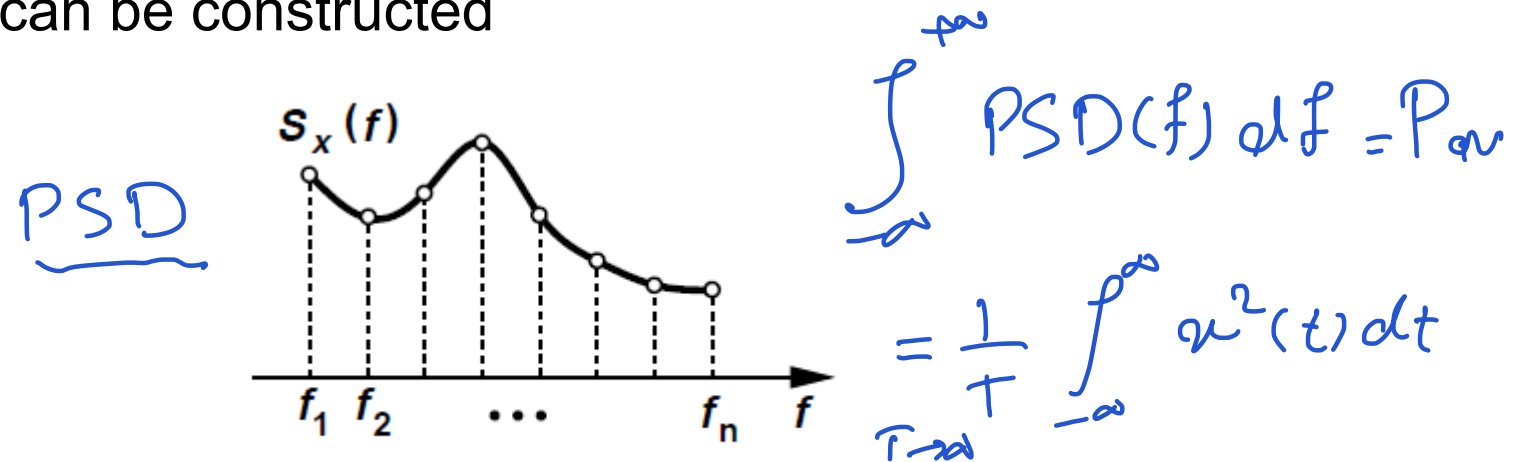- Repeating previous procedure with bandpass filters with different center frequencies, the overall PSD $S_x(f)$ can be constructed




- $S_x(f)$ Represents the power carried by signal (or noise) at all frequencies
 - Generally measured in Watts per Hertz

Handwritten unit derivation:


$$\cancel{\frac{V^2}{\cancel{H^2}}} \xrightarrow{\text{Hz}} \frac{V^2}{\sqrt{H^2}} = \frac{V^2}{H^2}$$



Noise Spectrum

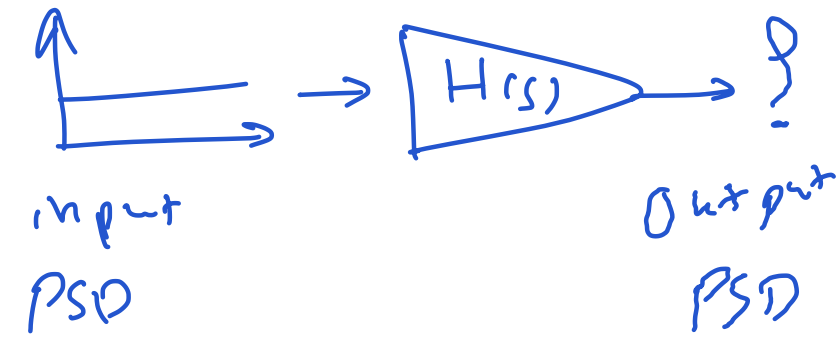

- As with P_{av} , it is customary to eliminate R_L from $S_x(f)$
- $S_x(f)$ is expressed in V^2/Hz rather than W/Hz
- Also common to take the square root of $S_x(f)$, expressing result in $V/\sqrt{\text{Hz}}$
- Common type of noise PSD is “white noise”
 - Displays same value at all frequencies
- White noise does not exist strictly speaking since total power carried by noise cannot be infinite
 - Noise spectrum that is flat *in the band of interest* is usually called white

$$PSD \propto \frac{1}{f}$$

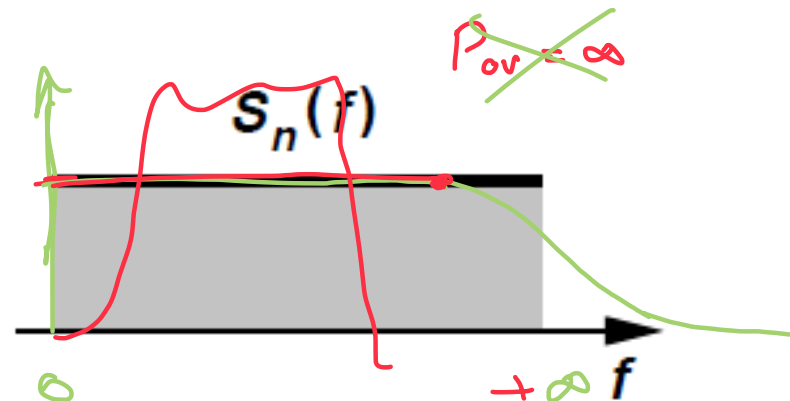

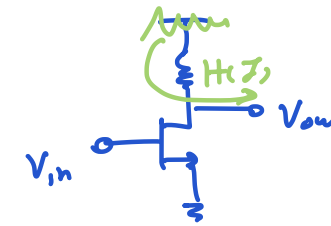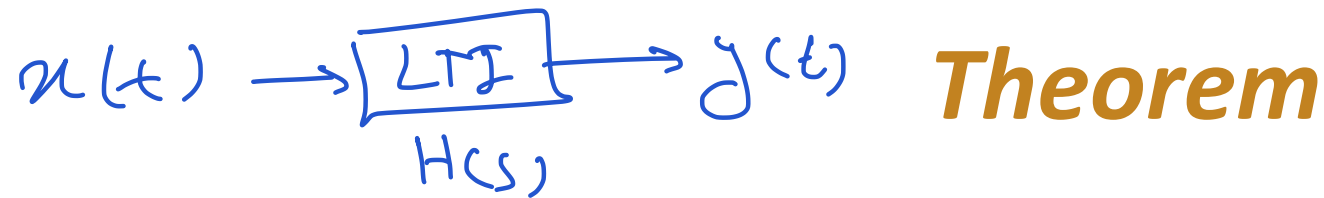

- If a signal with spectrum $S_x(f)$ is applied to a linear time-invariant (LTI) system with transfer function $H(s)$, then the output spectrum $S_y(f)$ is given by

$$\frac{y}{x} = H$$


$$S_Y(f) = S_x(f) |H(f)|^2$$

where $H(f) = H(s = j2\pi f)$

PSD of noise
@ output.


PSD of input
noise

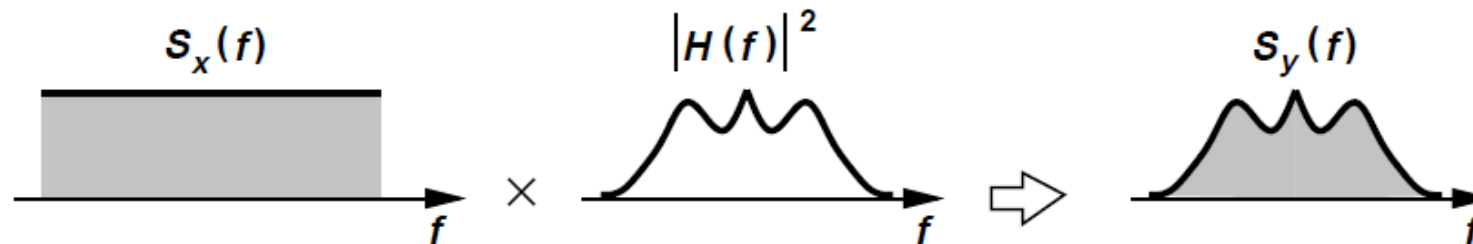- Spectrum of signal is “shaped” by the transfer function of the system (see Fig. below)



Theorem: Example

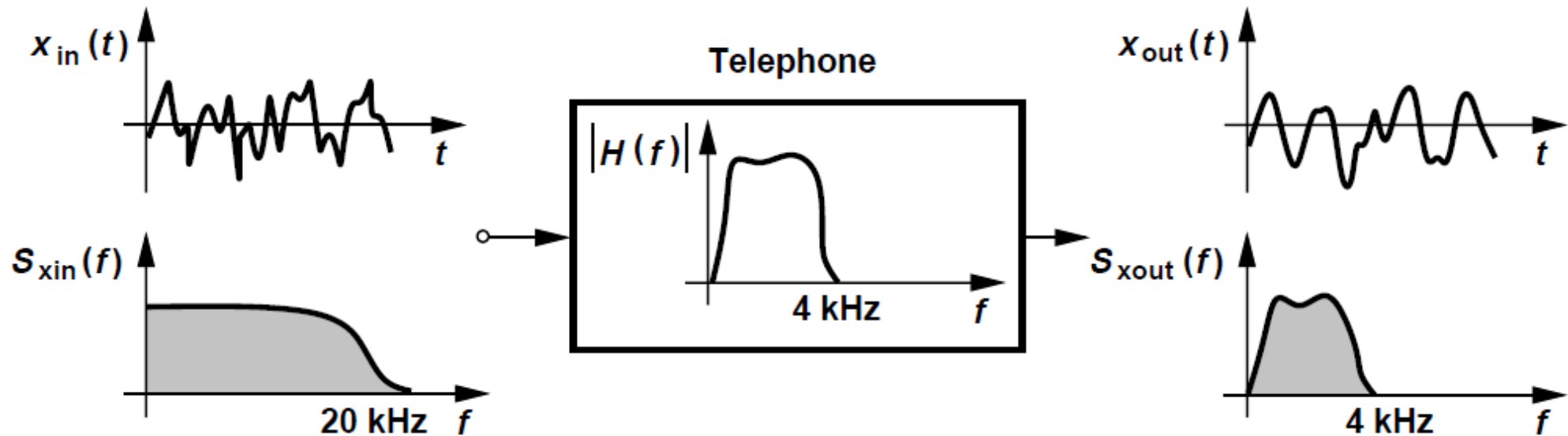- Regular telephones have a bandwidth of approximately 4kHz and suppress higher frequency components in caller's voice
- Due to limited bandwidth, $x_{out}(t)$ exhibits slower changes than $x_{in}(t)$
 - Can be difficult to recognize the caller's voice



Signal-to-Noise Ratio (SNR)

- Signal-to-noise ratio (SNR) is defined as

$$\text{dB} \quad \boxed{\text{SNR} = \frac{P_{\text{sig}}}{P_{\text{noise}}}}$$

- SNR of a noise-corrupted signal should be high for it to be intelligible


– Audio signals require a minimum SNR of 20 dB

- For a sinusoid with peak amplitude A , $P_{\text{sig}} = A^2/2 \leftarrow A \sin(\omega t)$

- The total average power carried by noise is equal to the area under its spectrum


$$P_{\text{noise}} = \int_{-\infty}^{+\infty} S_{\text{noise}}(f) df$$

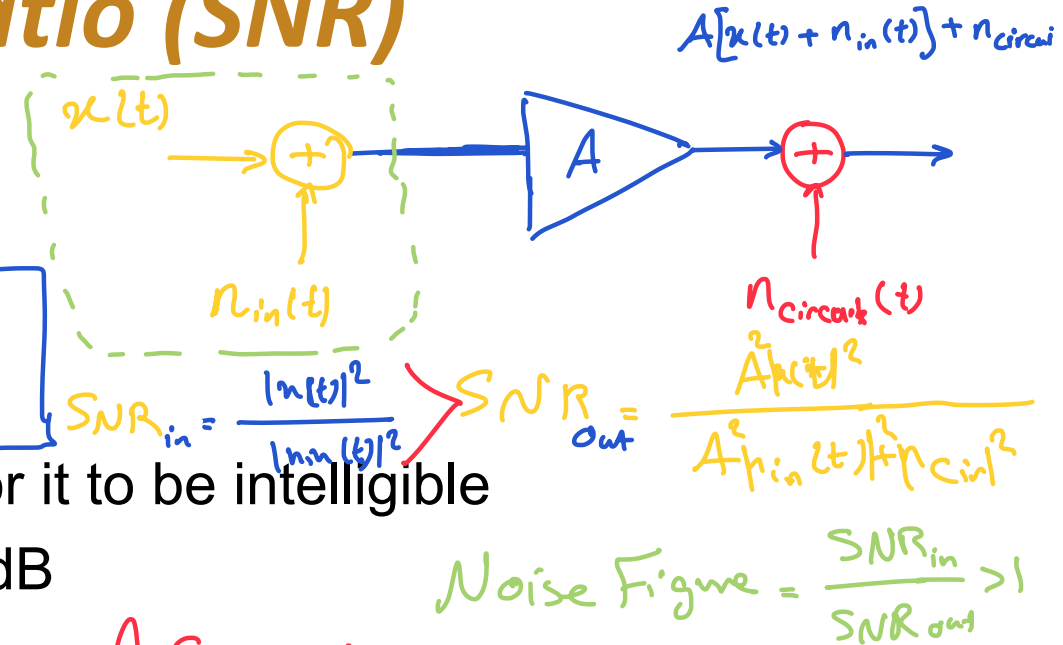- P_{noise} can be very large if $S_{\text{noise}}(f)$ spans a wide frequency range



Signal-to-Noise Ratio (SNR)

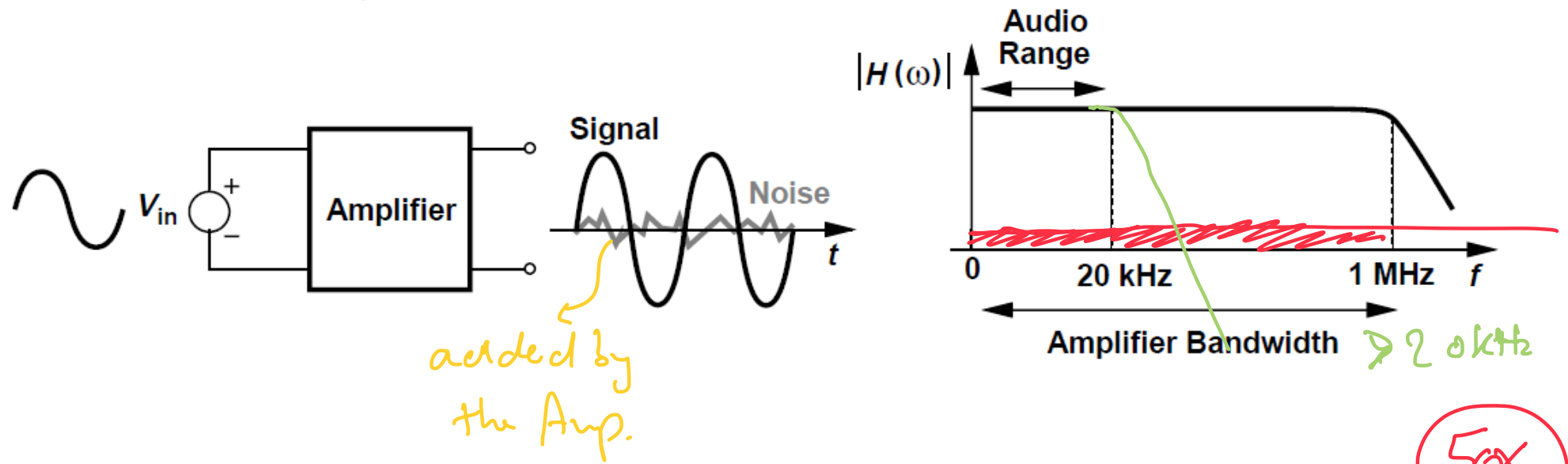- Below amplifier provides a bandwidth of 1 MHz while sensing an audio signal
 - What can be wrong?




$$SNR = \frac{P_{sig}}{P_{noise}}$$

$$\int PSD(f) df = PSD \times BW$$

For white Noise

50X

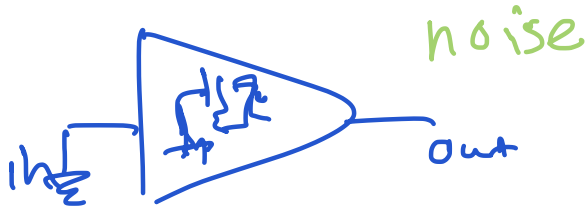

Noise Analysis Procedure

- Output signal of a given circuit is corrupted by noise sources within the circuit
 - Interested in noise observed at the output

- Four steps:
 - 1. Identify the sources of noise and note the spectrum of each
 - 2. Find the transfer function from each noise source to the output
 - 3. Use the theorem $S_Y(f) = S_X(f)|H(f)|^2$ to calculate output noise spectrum contributed by each noise source
 - 4. Add all the output spectra, accounting for correlated and uncorrelated sources

thermal

Res, Photodiode, channels

P/N MOS

PSD

properties of noise source


$H(f)$

$$PSD_{out}(f) = \sum PSD_i(f)$$

- Integrate the output noise spectrum from $-\infty$ to $+\infty$ to get total output noise power

Resistor Thermal Noise

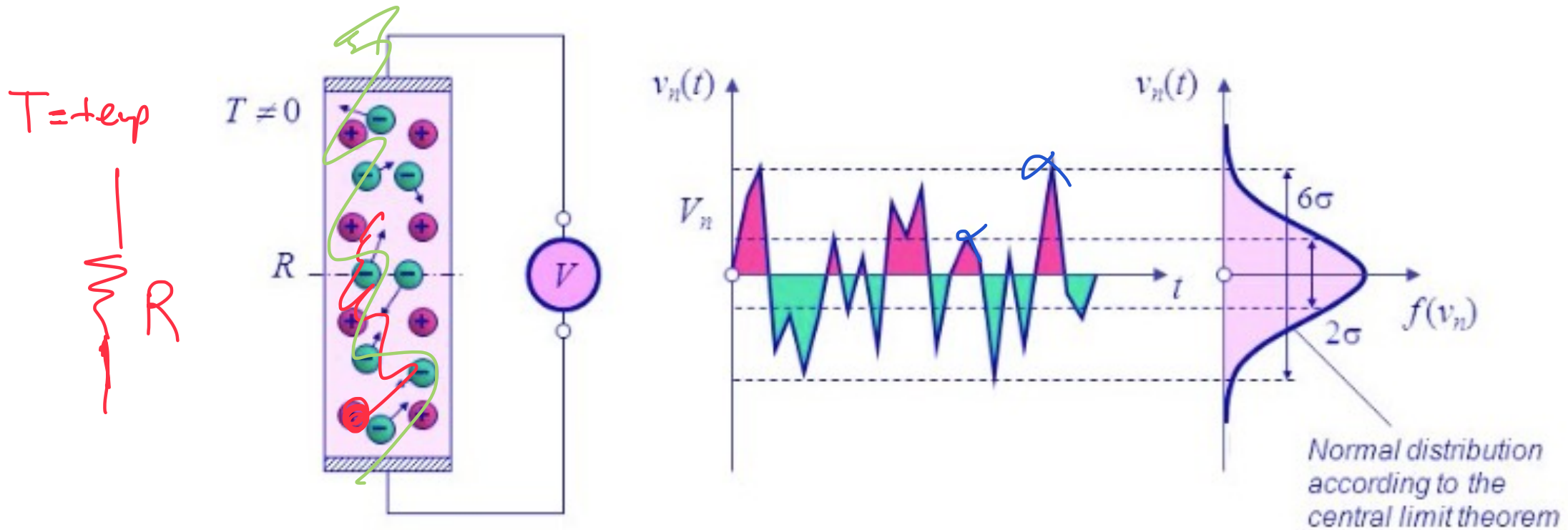- Random motion of electrons in a conductor induces fluctuations in the voltage measured across it even though the average current is zero




Resistor Thermal Noise


- Thermal noise of a resistor R can be modeled by a series voltage source, with one-sided spectral density

$$\underline{S_v(f) = 4kTR}, \quad f \geq 0 \quad \frac{V^2}{Hz}$$

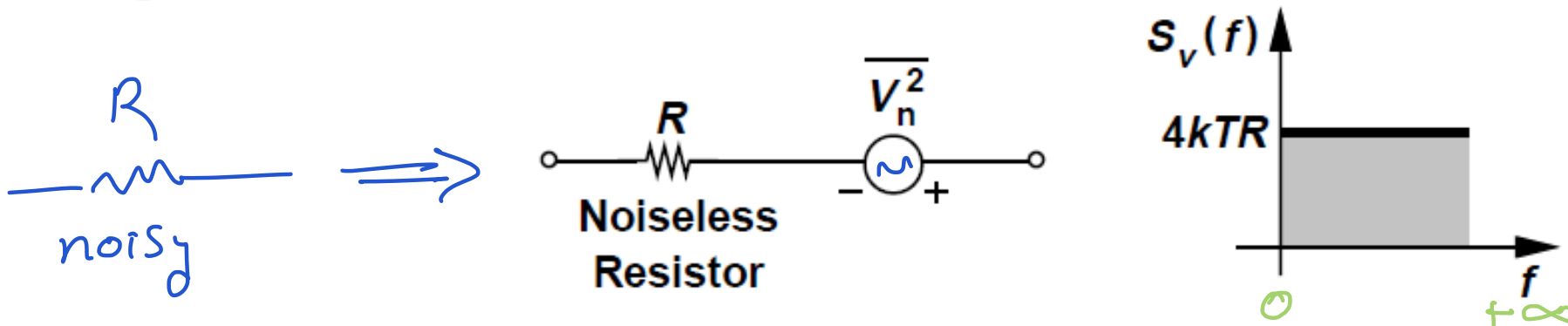- Here, $k = 1.38 \times 10^{-23}$ J/K is the Boltzmann constant
- $S_v(f)$ is expressed in V^2/Hz , we also write $\overline{V_n^2} = 4kTR$
- For a $50\text{-}\Omega$ resistor at $T = 300\text{K}$, thermal noise is $8.28 \times 10^{-19} V^2/Hz$, or $0.91 \text{ nV}/\sqrt{Hz}$
- $S_v(f)$ is flat up to 100THz , and is “white” for our purposes



Resistor Thermal Noise: Example

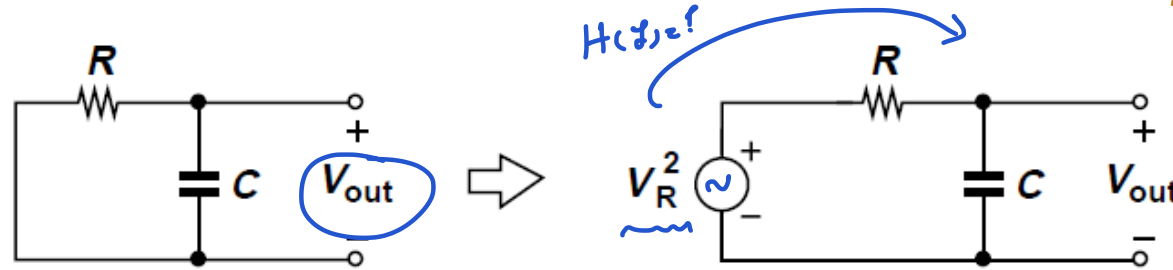

- To find: Noise spectrum and total noise power in V_{out}
- Solution: Noise spectrum of R is given by $S_v(f) = 4kTR$ (V^2/Hz)
- Modeling noise by a series voltage source V_R , transfer function from V_R to V_{out} is

$$\frac{V_{out}}{V_R}(s) = \frac{1}{RCs + 1}$$

- Using theorem, noise spectrum at the output $S_{out}(f)$ is

PSD


$$S_{out}(f) = S_v(f) \left| \frac{V_{out}}{V_R}(j\omega) \right|^2$$

$$= 4kTR \frac{1}{4\pi^2 R^2 C^2 f^2 + 1}$$

$\omega = 2\pi f$


$|1 + j\omega RC|^2$

$\int_0^{+\infty}$

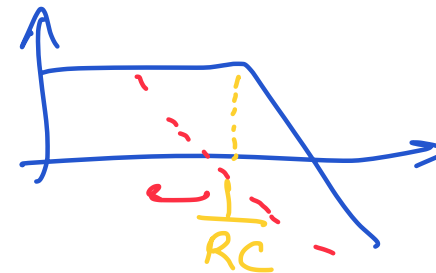

Resistor Thermal Noise: Example

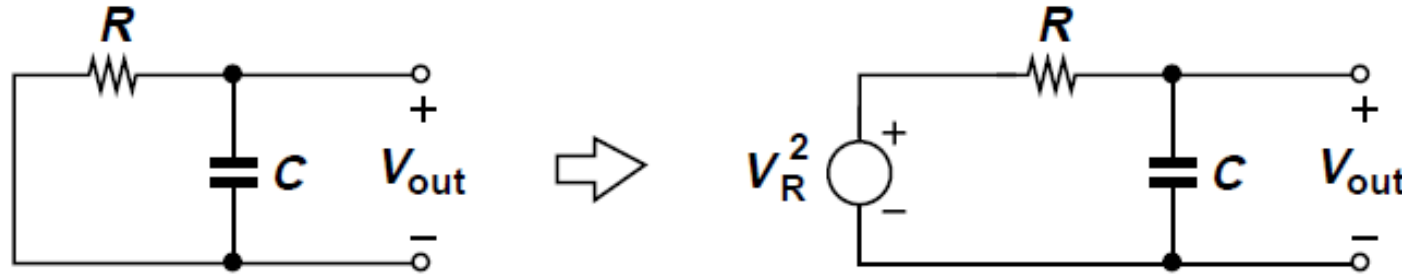$2 \times R$
 $\frac{1}{2} \times$
 $\frac{1}{2} kTR$
 noise power
 $2 \times$



- White noise spectrum of the resistor is shaped by a low-pass characteristic
- Total noise power at the output is

$$P_{n,out} = \int_0^{\infty} \frac{4kTR}{4\pi^2 R^2 C^2 f^2 + 1} df$$


- The integral reduces to

$$\begin{aligned}
 P_{n,out} &= \frac{2kT}{\pi C} \tan^{-1} u \Big|_{u=0}^{u=\infty} \\
 &= \frac{kT}{C}
 \end{aligned}$$



independent of R value!

~~×~~ The unit of $P_{n,out}$ is V^2/Hz , $\sqrt{kT/C}$ may be considered as the total rms voltage measured at the output

Resistor Thermal Noise: Example

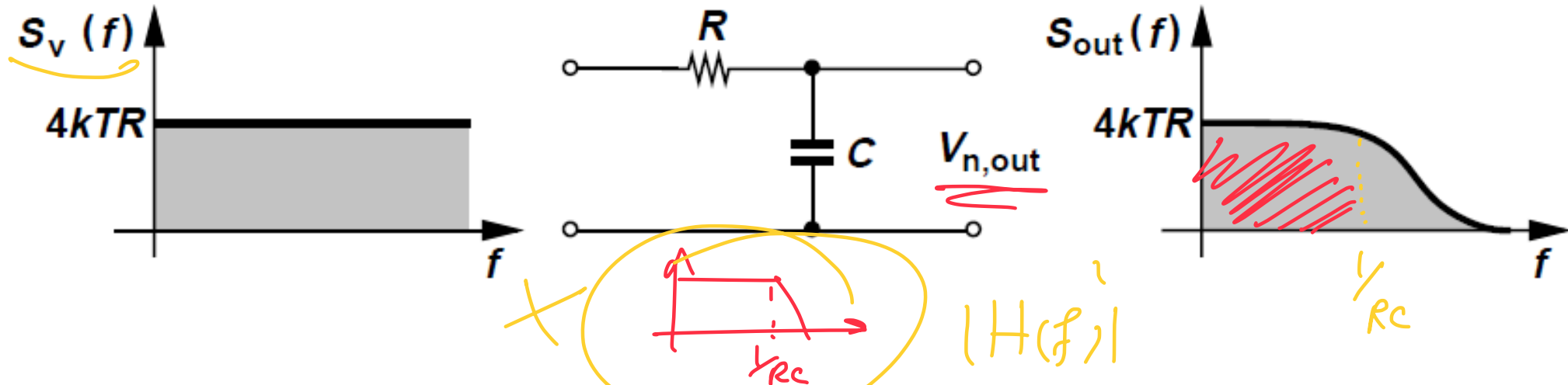

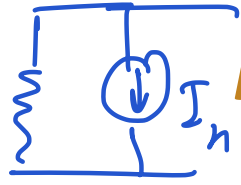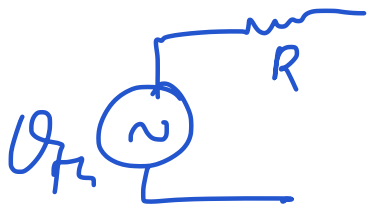- The RC low-pass filter shapes the noise spectrum of the resistor
- ★ Total noise at the output (area under $S_{out}(f)$) is independent of the resistance R
- Intuitively, this is because for larger values of R , noise per unit bandwidth increases but the overall bandwidth of the circuit decreases PSD
- kT/C noise can only be decreased by increasing C (if T is fixed)




Resistor Thermal Noise


$$I_n = V_n / R$$

- Thermal noise of a resistor can be represented by a parallel current source too

Noisy
Model
for Res.

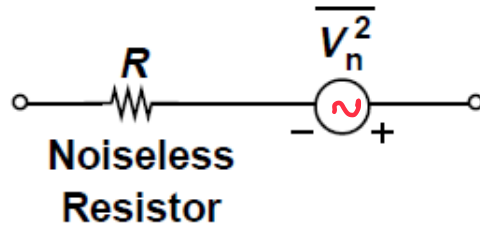

Noiseless
Resistor

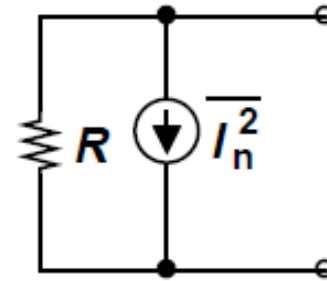

Norton Model

- This representation is equivalent to series voltage source representation with

$$\overline{I_n^2} = \frac{\overline{V_n^2}}{R^2} = \frac{4kTR}{R^2} \rightarrow \overline{I_n^2} = 4kT/R$$

- $\overline{I_n^2}$ is expressed in A^2/Hz
- This notation assumes a 1-Hz bandwidth
- Depending on circuit topology, one model may simplify calculations than the other




MOSFET Thermal Noise

- MOS transistors exhibit thermal noise with the most significant source being the noise generated in the channel
- For long-channel MOS devices operating in saturation, the channel noise can be modeled by a current source connected between the drain and source terminals with a spectral density

$$\overline{I_n^2} = 4kT\gamma g_m$$

- The coefficient 'γ' (not the body effect coefficient) is derived to be 2/3 for long-channel transistors and is higher for submicron MOSFETs
- As a rule of thumb, assume $\gamma = 1$

technology node & region dep.

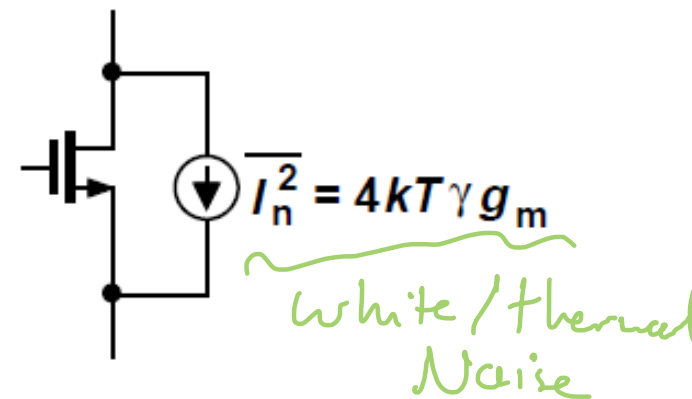

MOSFET Thermal Noise: Example

- The maximum output noise occurs if the transistor sees only its own output impedance as the load, i.e., if the external load is an ideal current source
- Output noise voltage spectrum is given by


PSD of Noise @ output

$$S_{out}(f) = S_{in}(f) |H(f)|^2$$

$$\overline{V_n^2} = \overline{I_n^2} r_O^2$$

$$= (4kT\gamma g_m) r_O^2$$

$$H(f) = \frac{V_{n,out}}{I_n} =$$

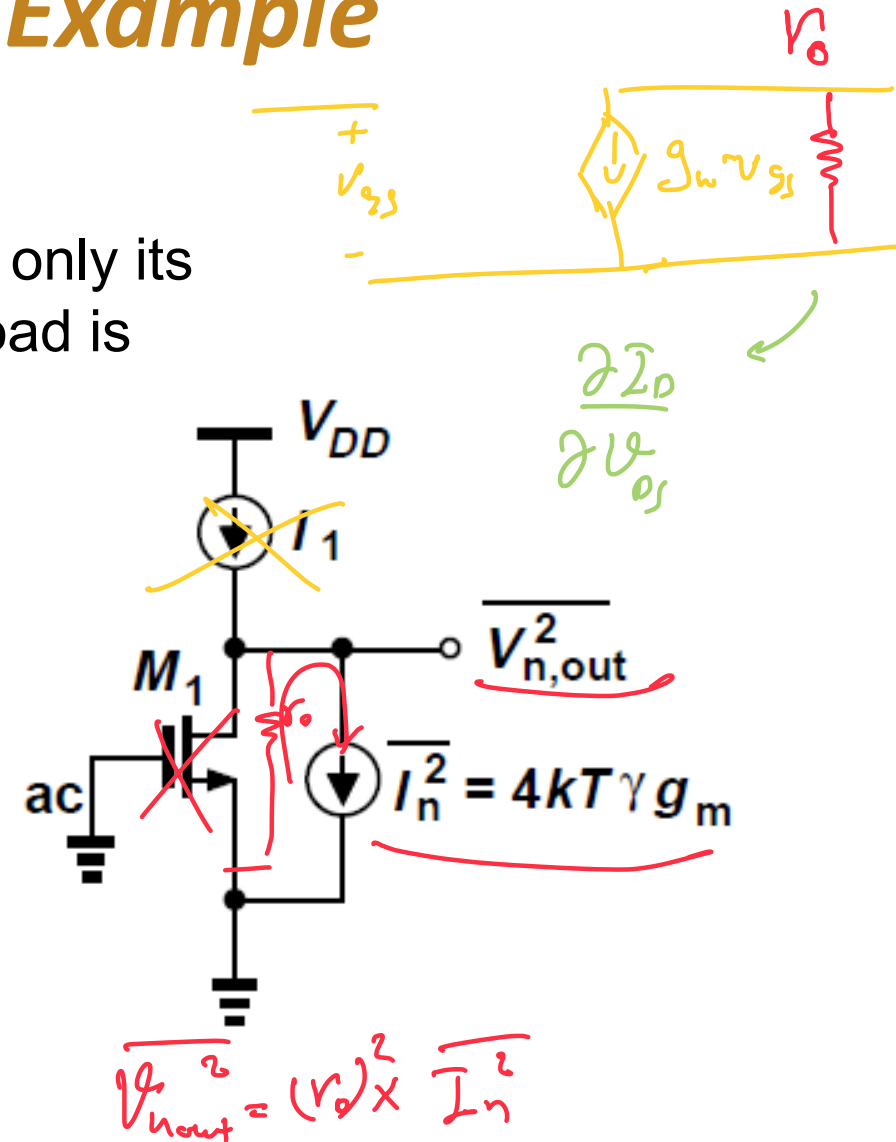

MOSFET Thermal Noise: Example

- Noise current of a MOS transistor decreases if g_m drops
- Noise measured at the output of the circuit does not depend on where the input terminal is because input is set to zero for noise calculation


- The output resistance r_o does not produce noise because it is not a physical resistor!

→ it's only due to modeling of C.L.M
by Noise.


- Another noise source is “Flicker Noise”

- Due to some dangling bonds at the surface -> carriers can get randomly trapped!
- Frequency dependent ($S = 1/f$)

$$S(f) \propto \frac{1}{f}$$

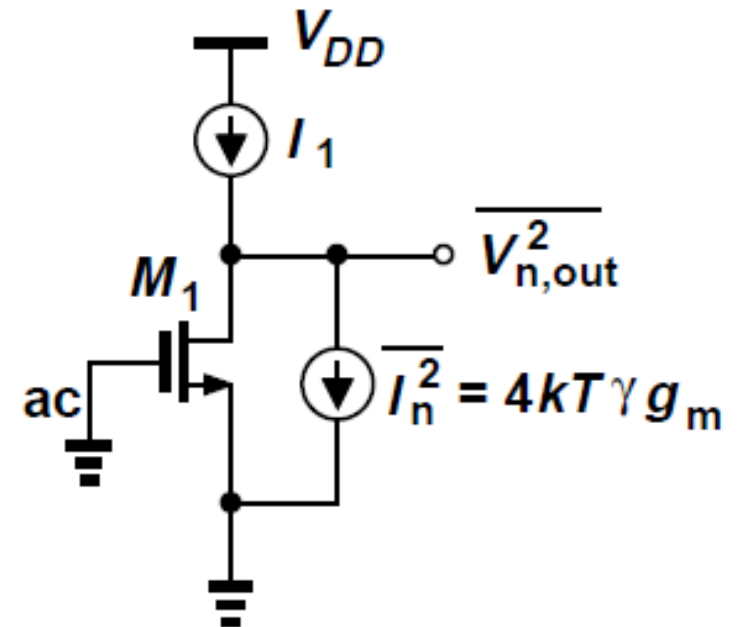


Representation of Noise in Circuits

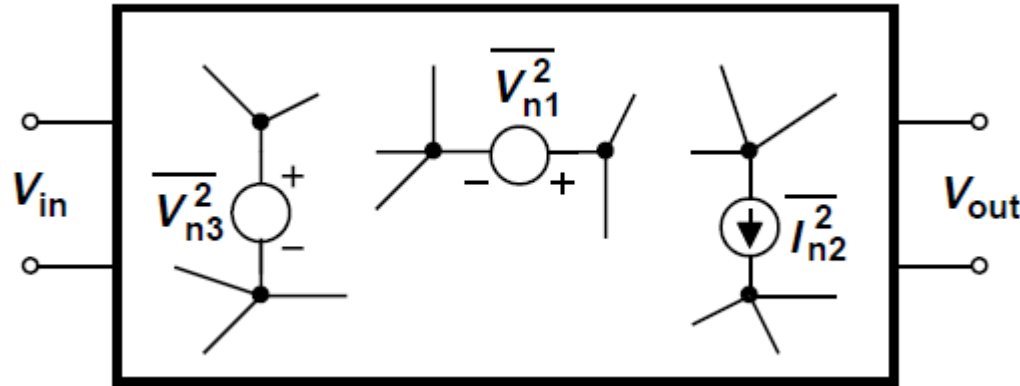

- To find the output noise, the input is set to zero and total noise is calculated at the output due to all the noise sources in the circuit
- This is how noise is measured in laboratories and in simulations

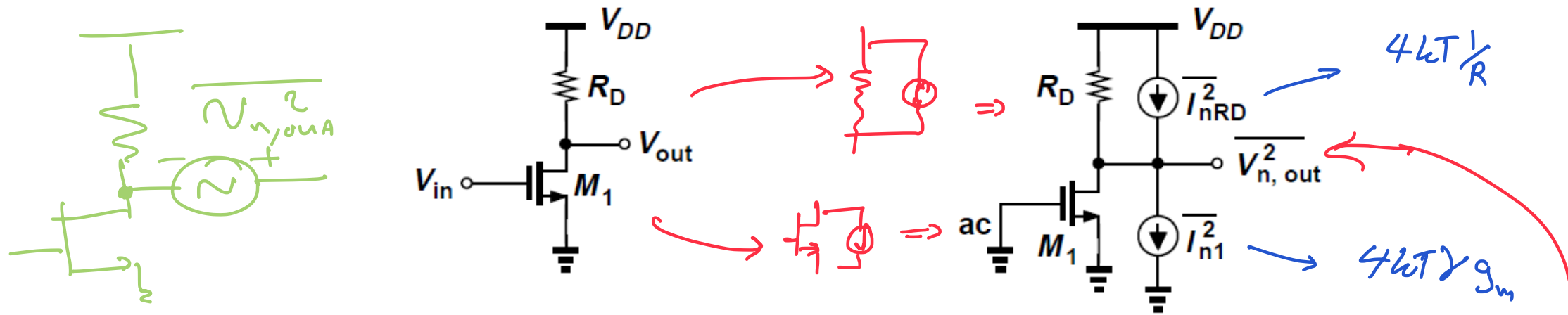Representation of Noise in Circuits: Example




- Find total output noise voltage of the common-source stage

$$V_{out_n} / I_{n1} = R_D \parallel r_o \rightarrow PSD_{nRD} = 4kT/R_D \times (R_D \parallel r_o)^2$$

$$V_{out_n} / I_{nRD} = R_D \parallel r_o \rightarrow PSD_{nM_1} = 4kT \gamma g_m \times (R_D \parallel r_o)^2$$

$$PSD_{n,out} = PSD_{nRD} + PSD_{nM_1}$$

Input-Referred Noise



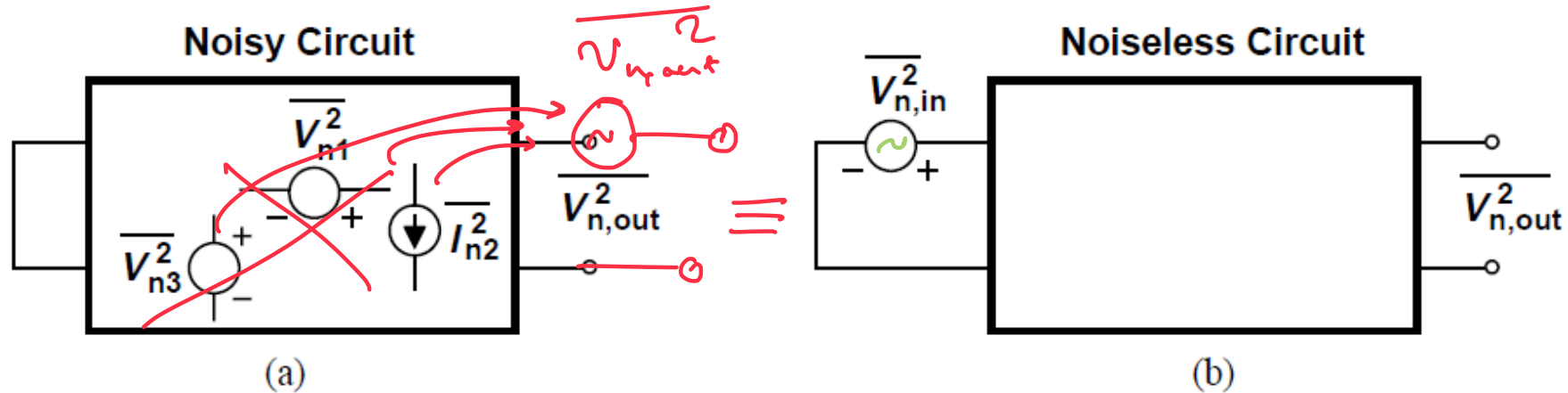


- Input-referred noise represents the effect of all noise sources in the circuit by a single source $V_{n,in}^2$, at the input such that the output noise in Fig. b is equal to that in Fig. a
- If the voltage gain is A_v , then we must have

$$\underline{\overline{V_{n,out}^2} = A_v^2 \overline{V_{n,in}^2}}$$

- The input-referred noise voltage in this simple case is simply the output noise divided by the gain squared.

Input-Referred Noise: Example

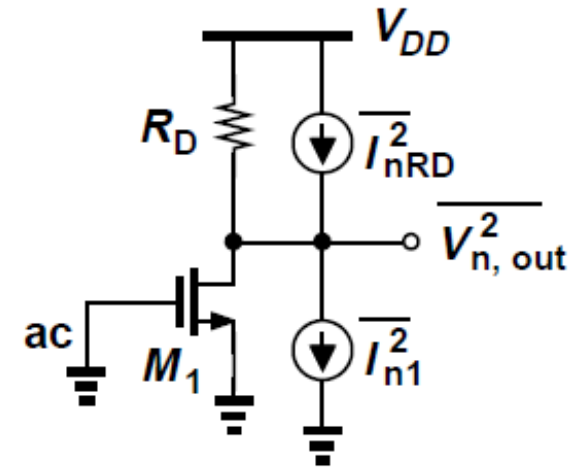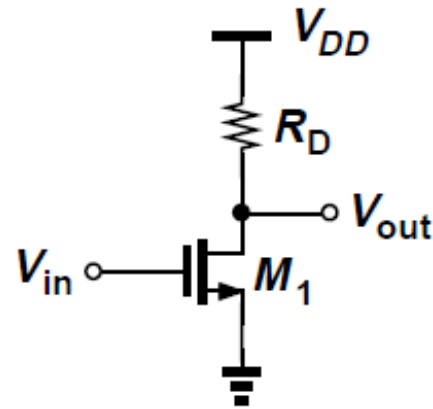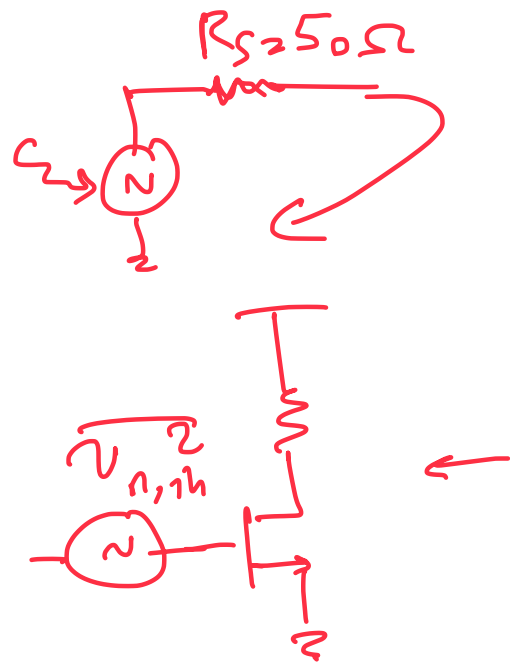

- For the simple CS stage, the input-referred noise voltage is given by ...

$$\overline{V_{n, out}^2} = (4kT\gamma g_m + 4kT\frac{1}{R_D}) (r_o \parallel R_D)^2$$

($\div A^2$ where $A = -g_m (R_D \parallel r_o)$)

$$\overline{V_{n, in}^2} = (4kT\gamma g_m + 4kT\frac{1}{R_D}) / g_m^2 = \frac{4kT\gamma}{g_m} + \frac{4kT g_m^2}{R_D}$$