


Full Name:
SID :

Grade: /100

Assume for all the problems: $V_{DD}=1.2V$, $|V_{th_{n,p}}|=0.3V$, $\mu_n C_{ox} = \frac{0.5mA}{V^2}$, $\mu_n = 2\mu_p$, $\lambda_p = \lambda_n = 0.1V^{-1}$, $\gamma = 0$ for both NMOS and PMOS devices.


1. (35 pts) If $I_1 = 1mA$ (ideal current source), and C_1 is an AC-coupling capacitor (will be shorted in small-signal models and open for DC/bias analysis) answer following questions assuming $\lambda = 0$ for this problem.

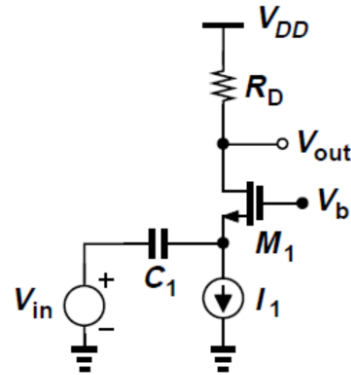- a) Find $(W/L)_1$ such that the input impedance will be 50Ω .
- b) Write down the small-signal gain equation in terms of small-signal parameters and R_D .
- c) Find R_D such that V_{out} bias point will be $V_{DD}/2$.
- d) Find small-signal gain using R_D from part c.
- e) If we realize I_1 current-source with a single NMOS device at a fixed gate bias of $V_{DD}/2$, what would be the W/L for that device?
- f) What can be minimum V_b to make sure all transistors are in saturation?
- g) Assuming $V_{in} = 0.5 + 0.01\sin(\omega t) V$, what is the overall (bias and small-signal) V_{out} ? (C_1 will be shorted at all frequencies)




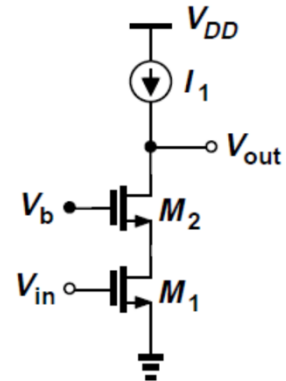2. (30 pts) Design a Cascode amplifier as shown in figure below to achieve a gain of 10k (10,000). Assume an ideal current source of $I_1 = 1\text{mA}$ and $g_m r_o \gg 1$.

- If $V_{GS1} = V_{GS2}$, what should be the value of V_{GS1} ?
- Find R_{out} and R_{in} values for this amplifier.
- Calculate optimal V_b to maximize the output swing.
- To realize the current source load, we will use a PMOS active load with $W/L=800$. Assume the bias current will remain at 1mA, what would be the V_{OD} ($=V_{GS}-V_{th}$) for this device?
- What's the output swing range?



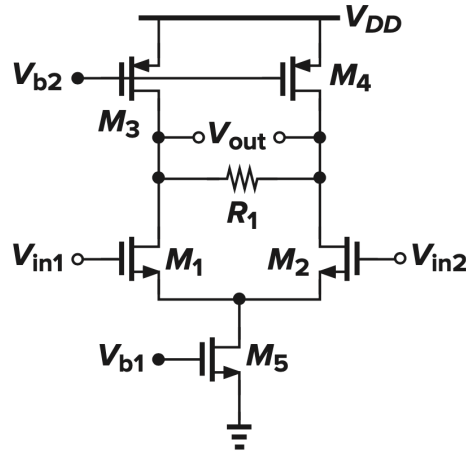3. (35 pts) For the differential amplifier shown below:



- Assuming the target over-drive voltage (V_{od}) for all the transistors is 0.2V, find the V_{b1} , V_{b2} values.
- Find $(W/L)_{1,2}$, $(W/L)_{3,4}$, & $(W/L)_5$ such that current tail will be 10mA.
- Draw the differential-mode half circuit and calculate the differential gain $\left(\frac{v_{out}}{v_{in1}-v_{in2}}\right)$ in terms of small-signal parameters (g_{mS} , r_{oS} , and R_1)?
- Draw the common-mode half circuit and calculate single ended common-mode gain $\left(\frac{v_{out1/2}}{v_{in,cm}}\right)$ in terms of small-signal parameters (g_{mS} , r_{oS} , and R_1)?
- For a differential gain of -10, what should be the value of R_1 ?
- Find differential output peak-to-peak swing.
- Find minimum input common-mode ($V_{in,cm}$) for this amplifier.

