

1. Razavi 3.10 (Only part a)

$V_{DD}=3V$. Assume threshold voltages from table 2.1 (uploaded to Canvas).

Consider the circuit of Fig. 3.13 with $(W/L)_1 = 50/0.5$ and $(W/L)_2 = 10/0.5$. Assume that $\lambda = \gamma = 0$.

- (a) At what input voltage is M_1 at the edge of the triode region? What is the small-signal gain under this condition?


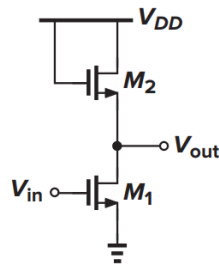


Figure 3.13 CS stage with diode-connected load.

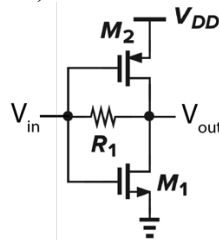2. Remember the amplifier with both NMOS and PMOS drivers we analyzed in the lecture. Here we add a resistor (R_1) in between input and output. Consider the output resistance of M_1 and M_2 in this problem (i.e. $\lambda \neq 0$).



- A major disadvantage with the original circuit (before adding R_1) was that output bias was hard to determine and very sensitive to PVT variations. Explain how adding R_1 helps with this. What's the equation to determine the bias voltage for V_{OUT} as a function of V_{IN} ? (Here assume $\lambda = 0$, just write down the equation)
- Draw the small-signal model and calculate the gain (A_v) as a function of small-signal parameters (g_m , r_o) and R_1 .
- Calculate input and output impedance of the amplifier.
- Recalculate gain using the lemma ($A_v = -G_m R_{out}$) and show it is the same as part b.
- Another important aspect of amplifiers is how sensitive is the output to supply fluctuations/noise (on V_{DD}). Since we can model these fluctuations with small-signal analysis, treating the V_{DD} node as the input, derive the gain from V_{DD} node to the output and compare that with the A_v . (Hint: Same small-signal model as part b, but this time V_{in} node should be AC-grounded and place a small-signal (AC) voltage source to model supply noises at the V_{DD} node)

3. Razavi 3.2

For the following problem, if not specified, use the following parameters: (parameters are defined for a nominal gate length (L) of $0.5\mu\text{m}$)

$$\mu_n = 350 \text{ cm}^2/\text{V}/\text{s}$$

$$\mu_p = 100 \text{ cm}^2/\text{V}/\text{s}$$

$$C_{ox} = 77.6 \text{ fF}/\mu\text{m}^2$$

$$V_{THN} = 0.7 \text{ V}$$

$$V_{THP} = -0.8 \text{ V}$$

$$\lambda_{nmos} = 0.1 \text{ V}^{-1}$$

$$\lambda_{pmos} = 0.2 \text{ V}^{-1}$$

In the circuit of Fig. 3.18, assume that $(W/L)_1 = 50/0.5$, $(W/L)_2 = 50/2$, and $I_{D1} = I_{D2} = 0.5 \text{ mA}$ when both devices are in saturation. Recall that $\lambda \propto 1/L$.

(a) Calculate the small-signal voltage gain.

(b) Calculate the maximum output voltage swing while both devices are saturated.

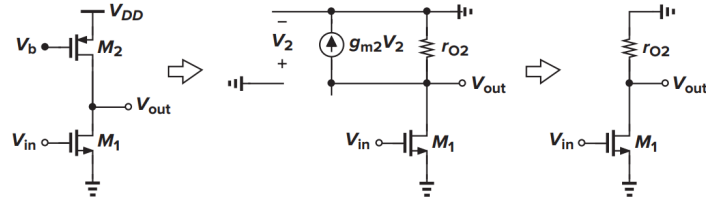


Figure 3.18 CS stage with current-source load.