

# EE 332: Devices and Circuits II

## Lecture 3: Single-stage Amplifiers (Part 1)


Prof. Sajjad Moazeni

[smoazeni@uw.edu](mailto:smoazeni@uw.edu)


Autumn 2022
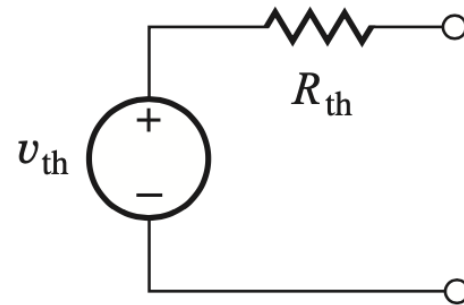
# Thevenin/Norton Models

- **Thevenin** equivalent theorem: any one-port linear network can be reduced to a single voltage source in series with a resistance (can have a complex impedance).
- **Norton** equivalent: similar to Thevenin theorem, but this time a current source in parallel to a single resistance.
- Notice:
  - $V_{th}$  is the open-circuit voltage of the port
  - $I_n$  is the short-circuit current of the port
  - $R_{th}$  is the impedance “seen” through the port by nulling the independent sources
  - $V_{th} = I_n \times R_{th}$




**Thevenin**

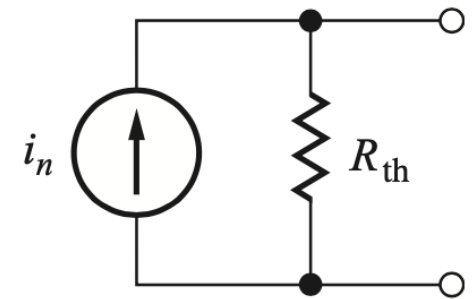

**Norton**

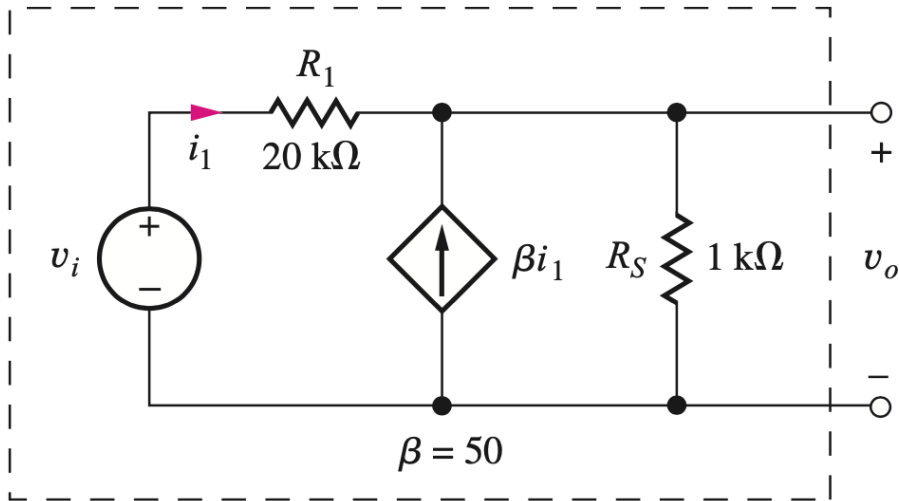
## An example ...

- Derive the Thevenin & Norton models (*Method: Calculate open-circuit  $V_o$  and Measure output impedance by nulling independent sources*)



# Input/Output Impedance

- Two-port model from circuit theory

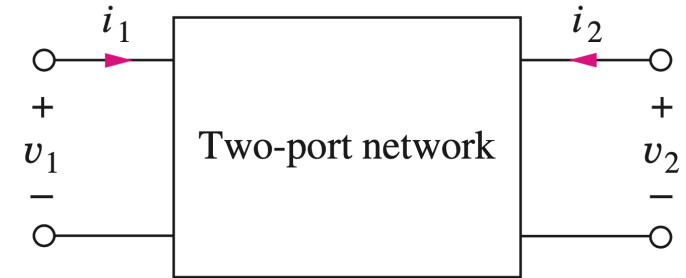

$$\mathbf{v}_1 = z_{11}\mathbf{i}_1 + z_{12}\mathbf{i}_2$$

$$\mathbf{v}_2 = z_{21}\mathbf{i}_1 + z_{22}\mathbf{i}_2$$

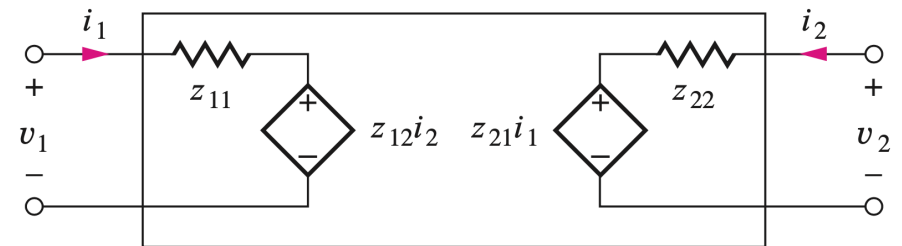


Figure C.4 Two-port z-parameter representation.

# Ideal vs Non-ideal Amplifier

- Ideal amplifier (Fig. a)


$$y(t) = \alpha_0 + \alpha_1 x(t)$$

- Large-signal characteristic is a straight line
- $\alpha_1$  is the “gain”,  $\alpha_0$  is the “dc bias”


- Nonlinear amplifier (Fig. b)

$$y(t) = \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \cdots + \alpha_n x^n(t)$$

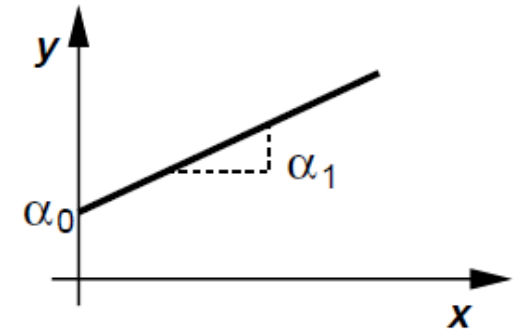- Large signal excursions around bias point
- Varying “gain”, approximated by polynomial
- Causes distortion of signal of interest




(a)

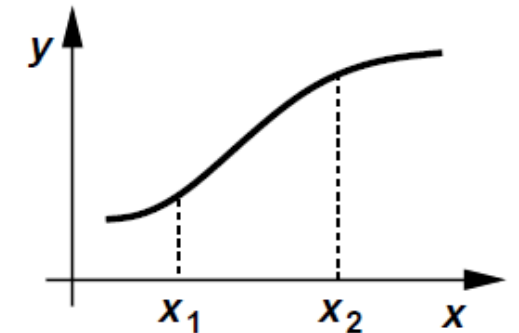





(b)
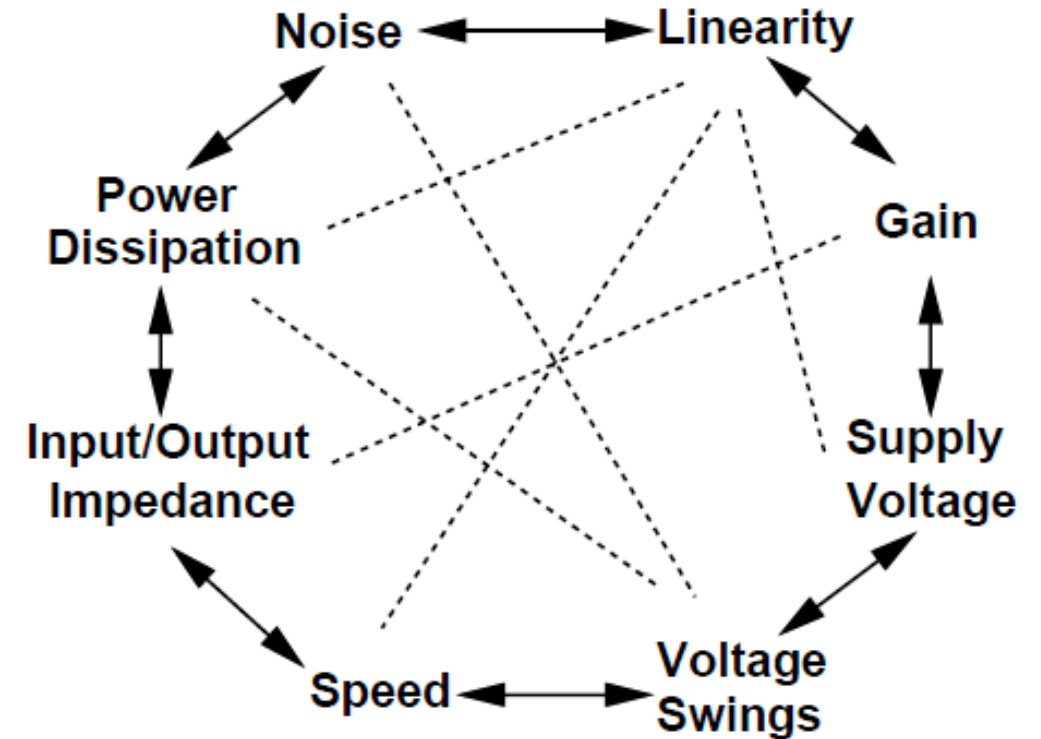
# Analog Design Tradeoff


- Along with gain and speed, other parameters also important for amplifiers
- Input and output impedances decide interaction with preceding and subsequent stages
- Note that linearity will be analyzed using the large-signal models (not the small-signal!)
- Performance parameters trade with each other
  - Multi-dimensional optimization problem



# Common-“X” Single-stage Amps.

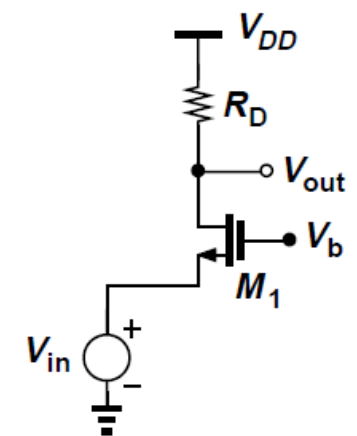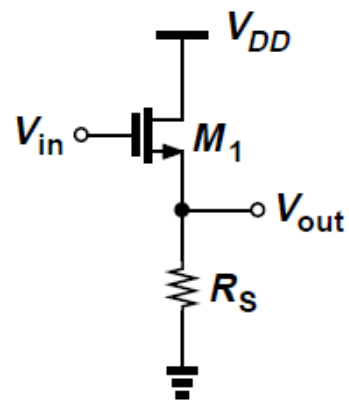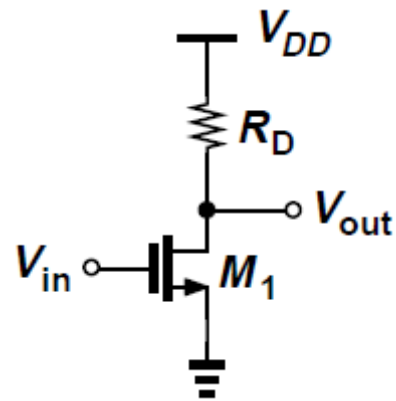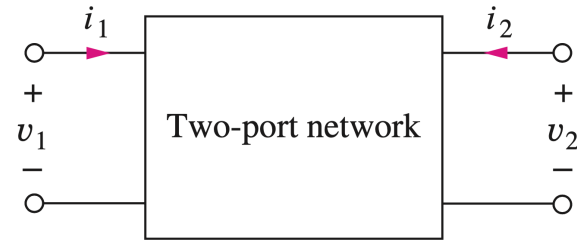

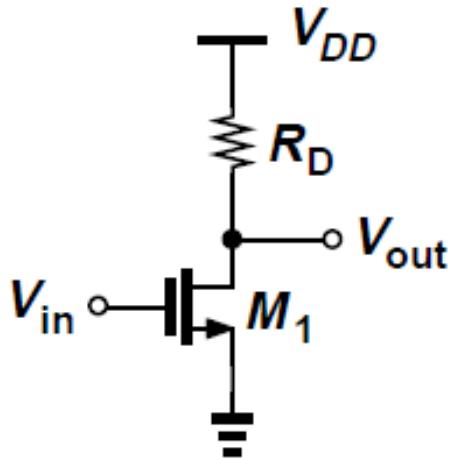
# Common-Source stage with Resistive load



- For  $V_{in} < V_{TH}$ ,  $M_1$  is off and  $V_{out} = V_{DD}$
- When  $V_{in} > V_{TH}$ ,  $M_1$  turns on in saturation region,  $V_{out}$  falls
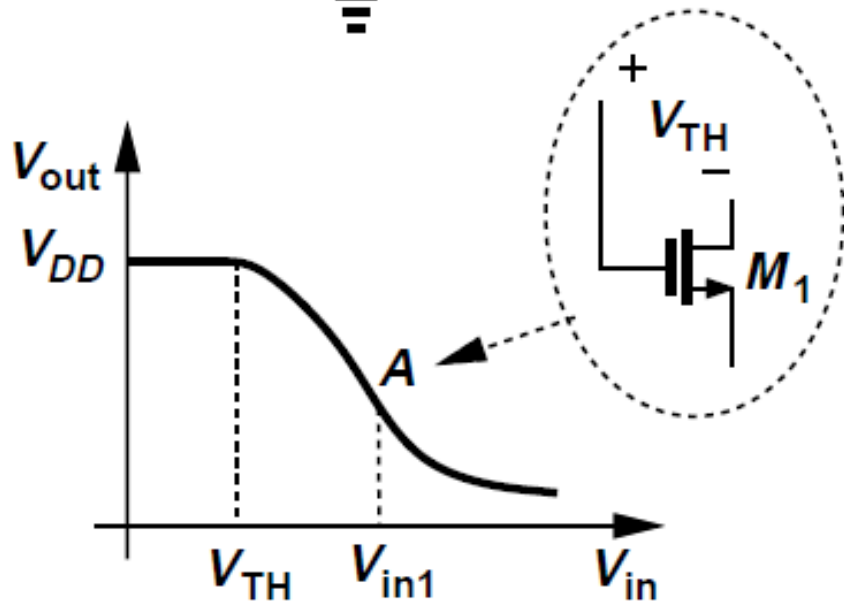
$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$




- When  $V_{in} > V_{in1}$ ,  $M_1$  enters triode region
- At point A,  $V_{out} = V_{in1} - V_{TH}$

$$V_{in1} - V_{TH} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH})^2$$


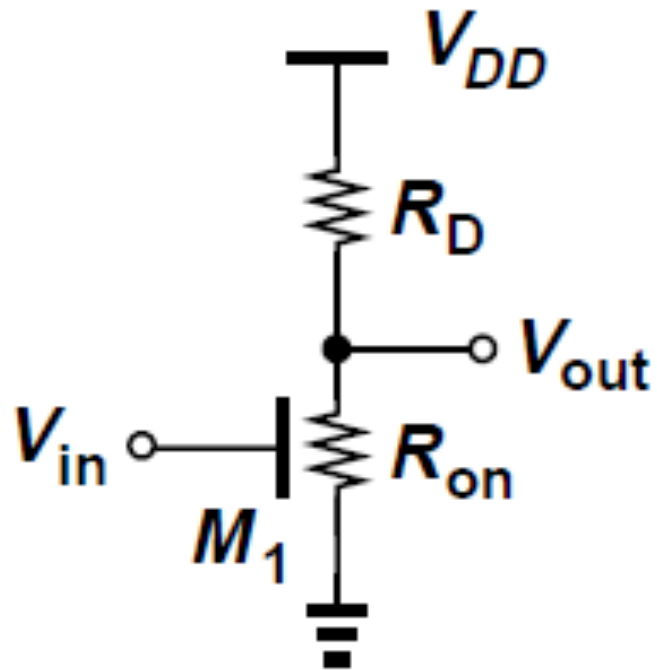
# Common-Source stage with Resistive load



- For  $V_{in} > V_{in1}$ ,



$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{in} - V_{TH})V_{out} - V_{out}^2]$$

- If  $V_{in}$  is high enough to drive  $M_1$  into deep triode region so that  $V_{out} \ll 2(V_{in} - V_{TH})$ ,

$$\begin{aligned} V_{out} &= V_{DD} \frac{R_{on}}{R_{on} + R_D} \\ &= \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})} \end{aligned}$$

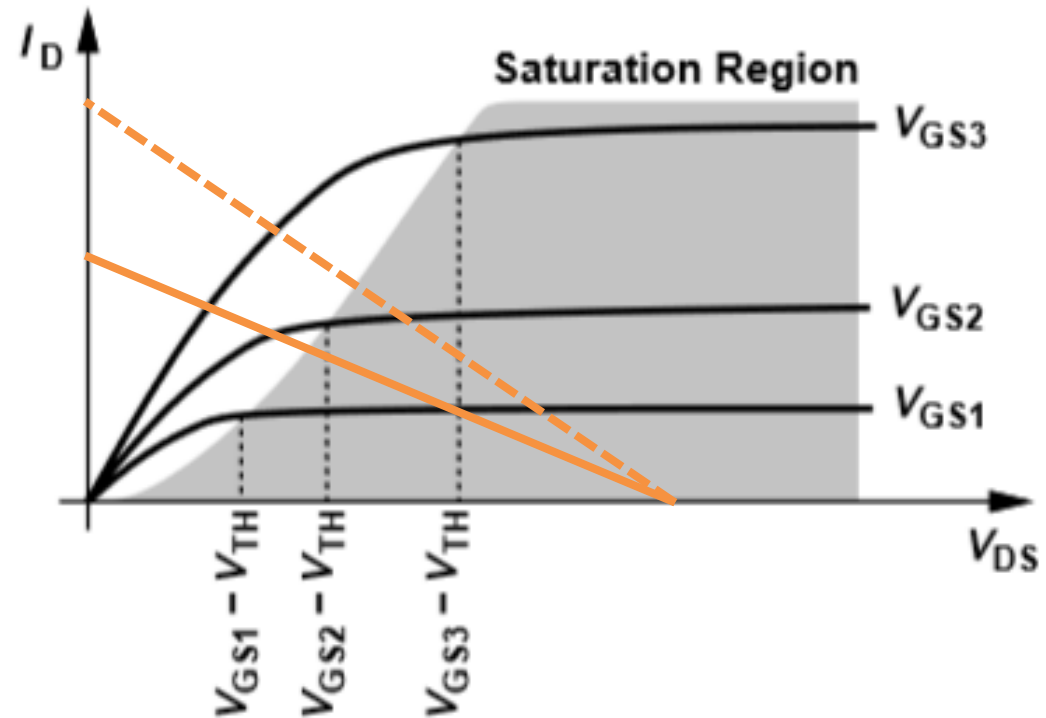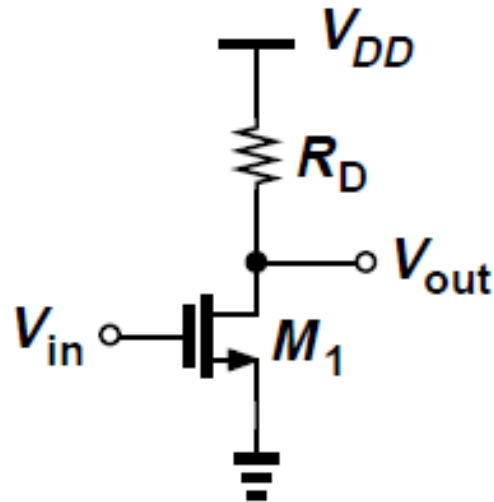
# Load-line & Bias point

- Visualizing the “equations” by load-lines to find the operating (bias) point


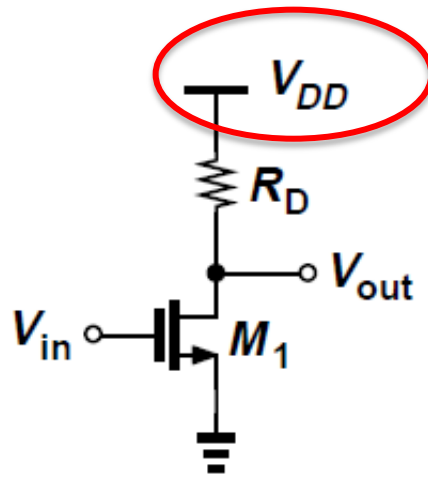
# Small-signal models for CS Stage

Notice the notations for small-signal in this book! ( $V_{in}$  = small-signal source)



**DC Supplies  
will be nulled  
for SS-models!**

**For NMOS**


**For PMOS**

# Common-Source stage with Resistive load

- Taking derivative of  $I_D$  equation in saturation region, small-signal gain is obtained

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$
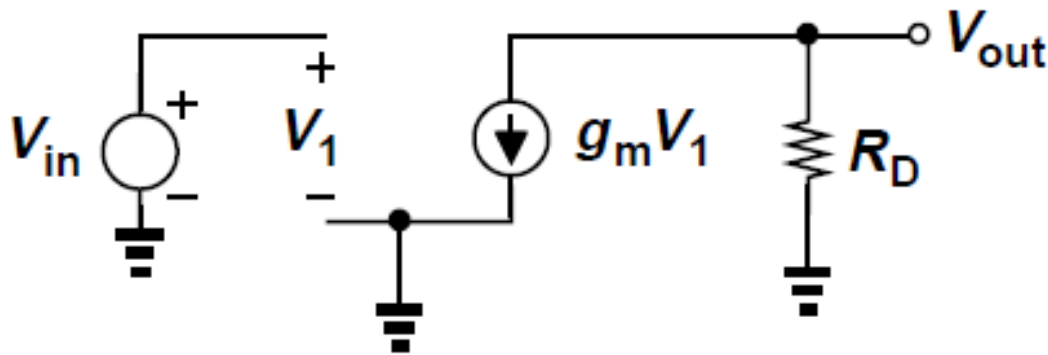
$$\begin{aligned} A_v &= \frac{\partial V_{out}}{\partial V_{in}} \\ &= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) \\ &= -g_m R_D \end{aligned}$$



- Same result is obtained from small-signal equivalent circuit

$$V_{out} = -g_m V_1 R_D = -g_m V_{in} R_D$$

- $g_m$  and  $A_v$  vary for large input signal swings according to


$$g_m = \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})$$

Examples 3.1 & 3.2 from Razavi

- This causes non-linearity!!!
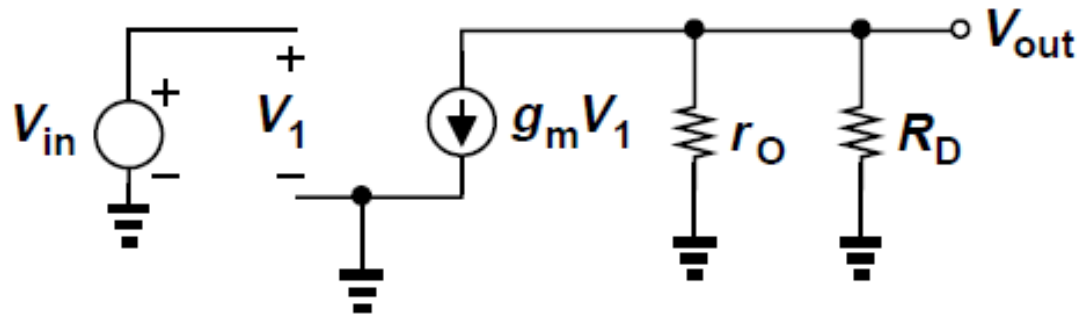
# Common-Source stage with Resistive load

- Above result is also obtained from small-signal equivalent circuit



$$V_1 = V_{in}$$

$$g_m V_1 (r_O \parallel R_D) = -V_{out}$$

$$V_{out} / V_{in} = -g_m (r_O \parallel R_D)$$

- For large values of  $R_D$ , channel-length modulation of  $M_1$  becomes significant,  $V_{out}$  equation becomes


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$

- Voltage gain is

$$A_v = -g_m \frac{r_O R_D}{r_O + R_D}$$

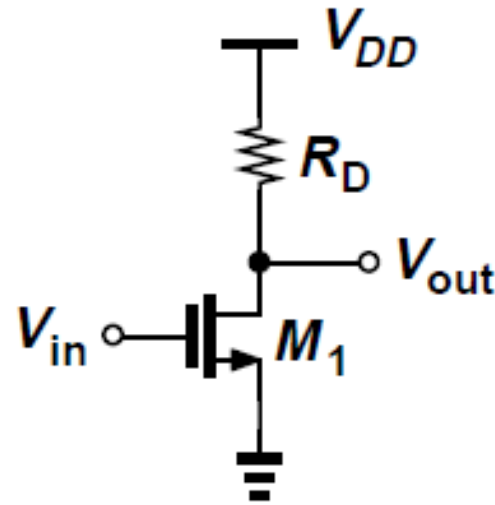
# CS Stage Example

- What's the voltage swing of  $V_{out}$ ? What's the optimal bias point for  $V_{out}$  to achieve max swing?


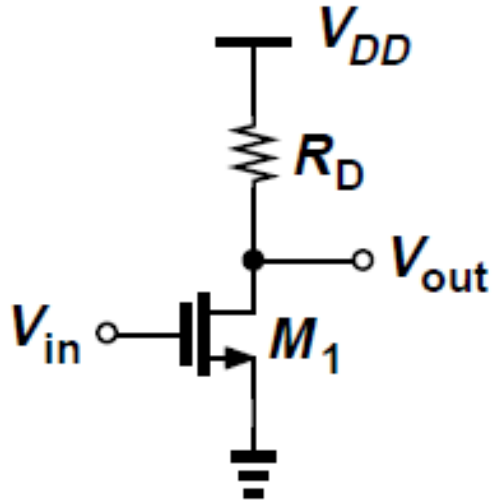
# CS Stage Example

- Find  $V_{in}$  &  $R_D$  value such that:  $V_{out} = V_{DD}/2$  & Gain  $> 10$



$$\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$$


$$W/L = 10$$

$$V_{TH} = 0.3 \text{ V}$$


$$\lambda = 0.1 \text{ V}^{-1}$$
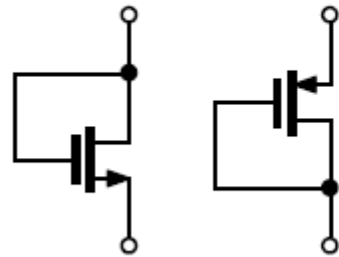
# Diode-Connected MOSFET

- A MOSFET can operate as a small-signal resistor if its gate and drain are shorted, called a “diode-connected” device
- Transistor always operates in **saturation** (why?)



Diode-Connected Device

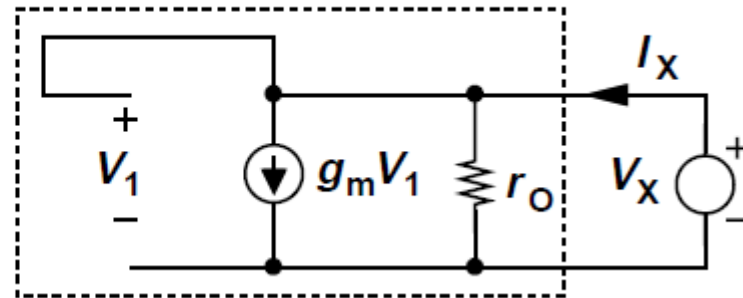



- Impedance of the device can be found from small-signal equivalent model

$$V_1 = V_X \qquad I_X = V_X / r_o + g_m V_X$$

$$V_X / I_X = (1 / g_m) \parallel r_o \approx 1 / g_m$$



# Diode-Connected MOSFET

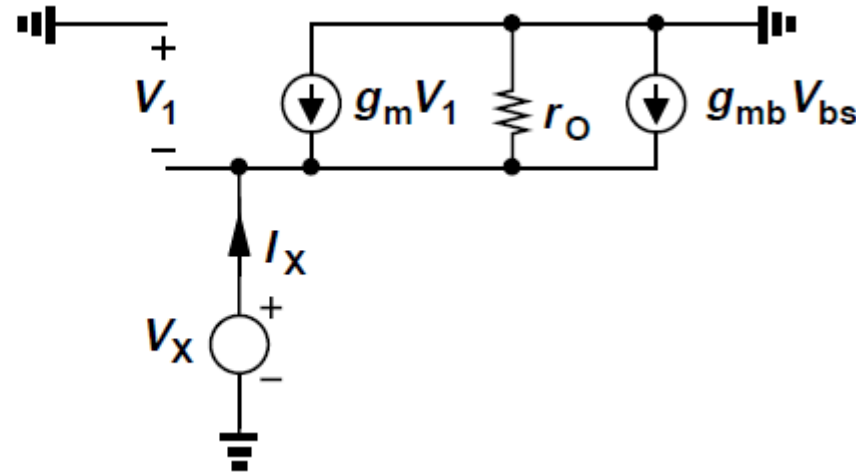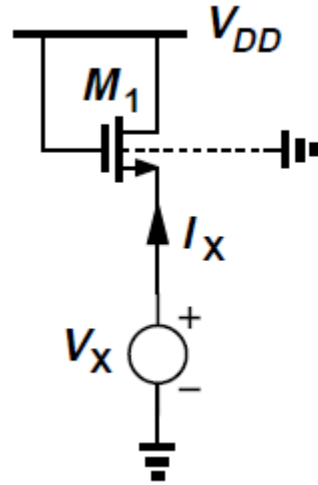

- Including body-effect, impedance “looking into” the source terminal of diode-connected device is found as



$$V_1 = -V_X \quad V_{bs} = -V_X$$

$$(g_m + g_{mb})V_X + \frac{V_X}{r_O} = I_X$$

$$\begin{aligned} \frac{V_X}{I_X} &= \frac{1}{g_m + g_{mb} + r_O^{-1}} \\ &= \frac{1}{g_m + g_{mb}} \parallel r_O \\ &\approx \frac{1}{g_m + g_{mb}} \end{aligned}$$

# Diode-Connected MOSFET: Example

- Find  $R_X$  if  $\lambda = 0$

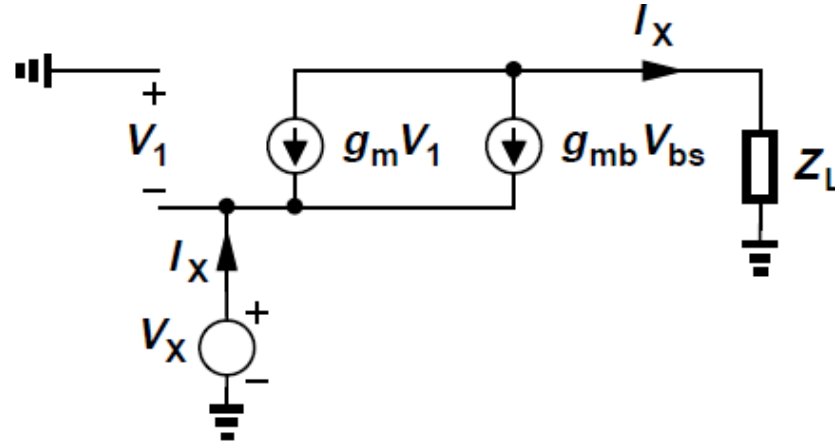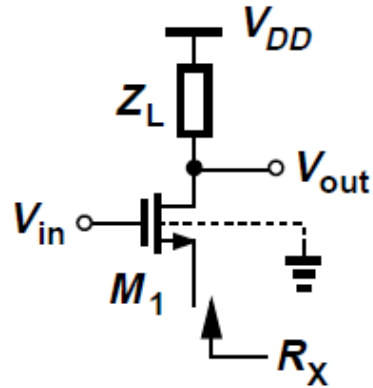

- Set independent sources to zero, apply  $V_X$  and find resulting  $I_X$

$$V_1 = -V_X$$


$$V_{bs} = -V_X$$

$$(g_m + g_{mb})V_X = I_X$$

$$\frac{V_X}{I_X} = \frac{1}{g_m + g_{mb}}$$

- Result is same compared to when drain of  $M_1$  is at ac ground, but only when  $\lambda = 0$
- Loosely said that looking into source of MOSFET, we see  $1/g_m$  when  $\lambda = \gamma = 0$

# CS Stage with Diode-Connected Load

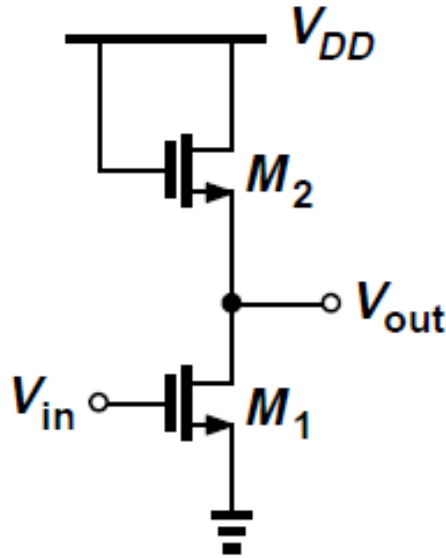

- Neglecting channel-length modulation, using impedance result for diode-connected device,

$$A_v = -g_{m1} \frac{1}{g_{m2} + g_{mb2}}$$
$$= -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$

where,

$$\eta = g_{mb2}/g_{m2}$$

- Expressing  $g_{m1}$  and  $g_{m2}$  in terms of device dimensions,

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

- This shows that gain is a weak function of bias currents and voltages, i.e., relatively linear input-output characteristic

# Process Variations in CMOS

- Real-world is non-deterministic ...
- Additionally many parameters such as mobility ( $\mu$ ) is temperature sensitive
- We use term “**PVT**” dependent: Process-Voltage-Temperature sensitive
- There are all sort of process variations: wafer-to-wafer, chip-to-chip, etc.
- We normally model the variations using Gaussian models and simulate circuit performance using
  - Process corners such as: typical-typical, fast-fast, etc.
  - Monte-Carlo Simulations

**“Golden”** design rules to minimize the impacts of PVT variations:

- Rely on ratios as opposed to absolute values
- Make circuits symmetric



# CS Stage with Diode-Connected Load

- From large-signal analysis,


$$\frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})^2$$

$$\sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L}\right)_2} (V_{DD} - V_{out} - V_{TH2})$$

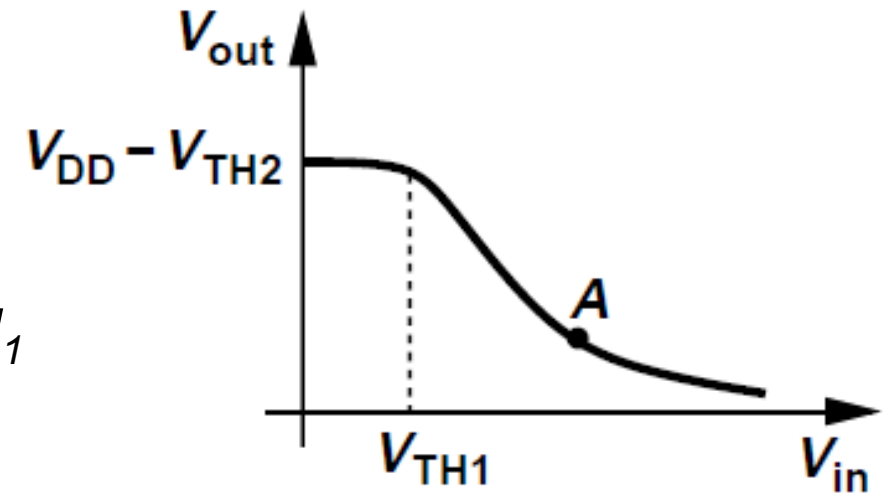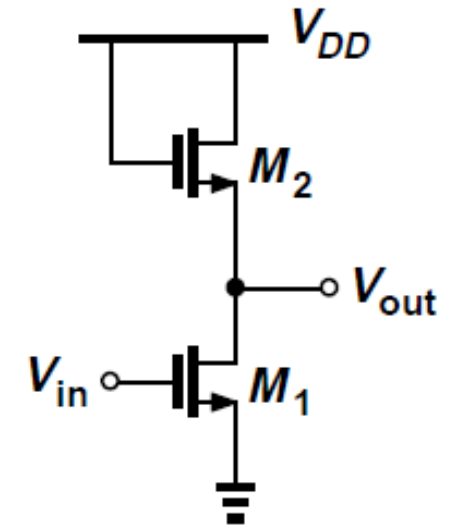- For  $V_{in} < V_{TH1}$ ,  $V_{out} = V_{DD} - V_{TH2}$
- When  $V_{in} > V_{TH1}$ , previous large-signal analysis predicts that  $V_{out}$  approximately follows a single line
- As  $V_{in}$  exceeds  $V_{out} + V_{TH1}$  (to the right of point A),  $M_1$  enters the triode region and the characteristic becomes nonlinear.


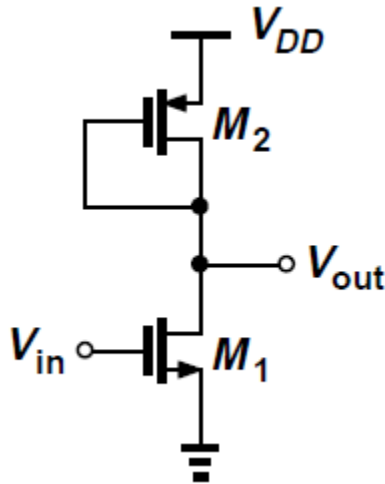
# CS Stage with Diode-Connected PMOS device




- Diode-connected load can be implemented as a PMOS device, free of body-effect
- Small-signal voltage gain neglecting channel-length modulation

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}}$$


- Gain is a relatively weak function of device dimensions
- Since  $\mu_n \approx 2\mu_p$ , high gain requires “strong” input device (large  $W/L_1$ ) and “weak” load device (small large  $W/L_2$ )
- Voltage-swing?

# CS Stage with Current-Source Load

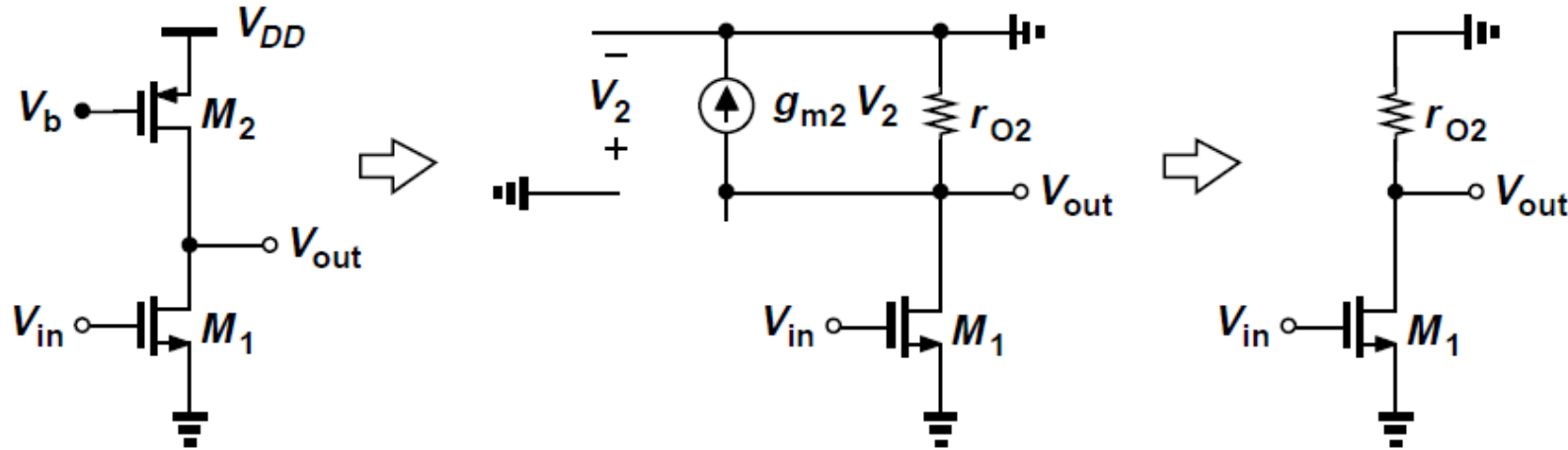

- Current-source load allows a high load resistance without limiting output swing
- Voltage gain ?
- Overdrive of  $M_2$  can be reduced by increasing its width,  $r_{o2}$  can be increased by increasing its length




# CS Stage with Current-Source Load

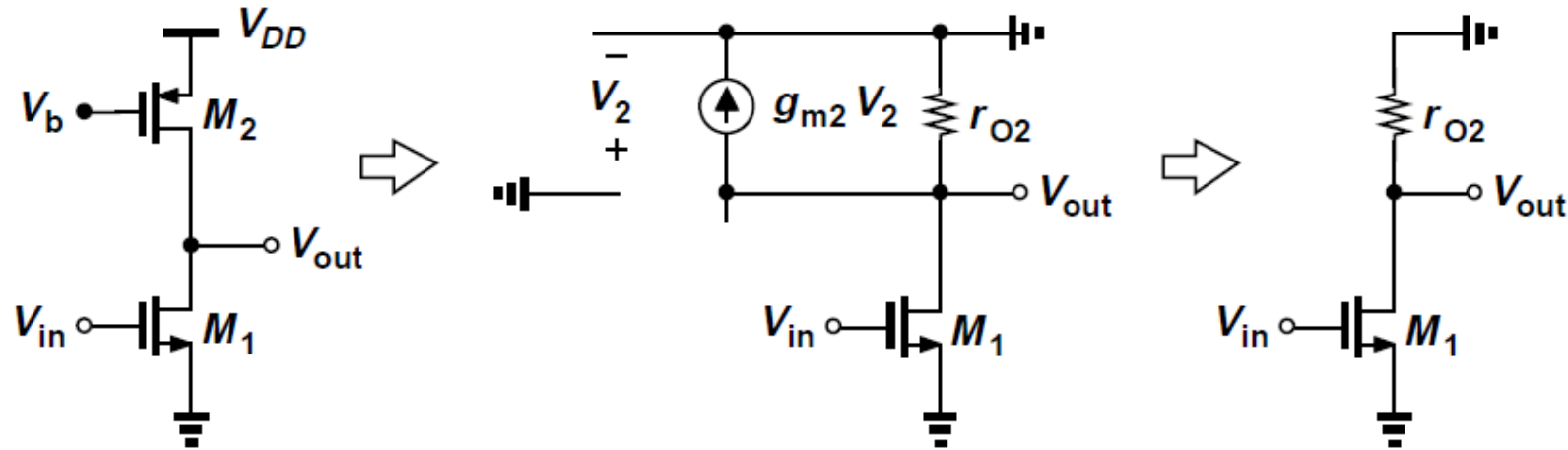


- Output bias voltage is not well-defined (why?)
- Intrinsic gain of  $M_1$  decreases with  $I_D$  (Why?)



# Summary of CS Amps.

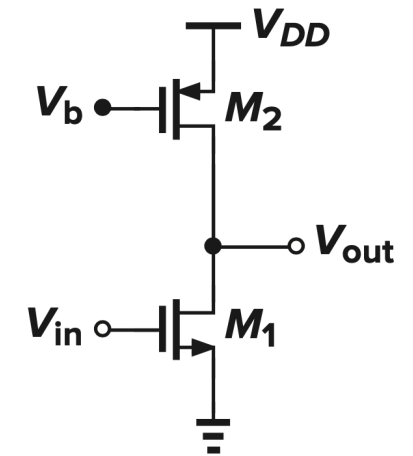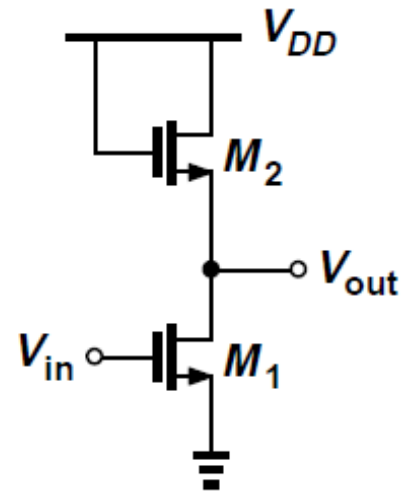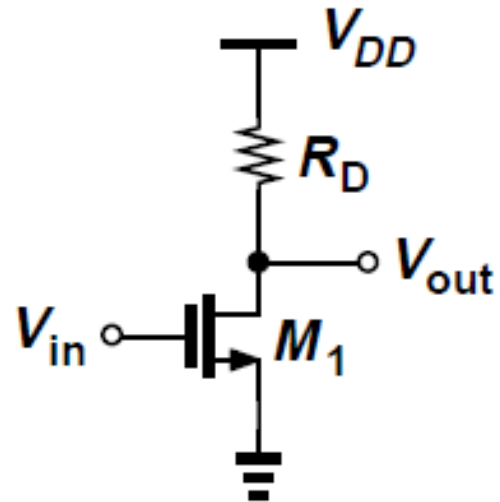

# CS Stage with Active Load

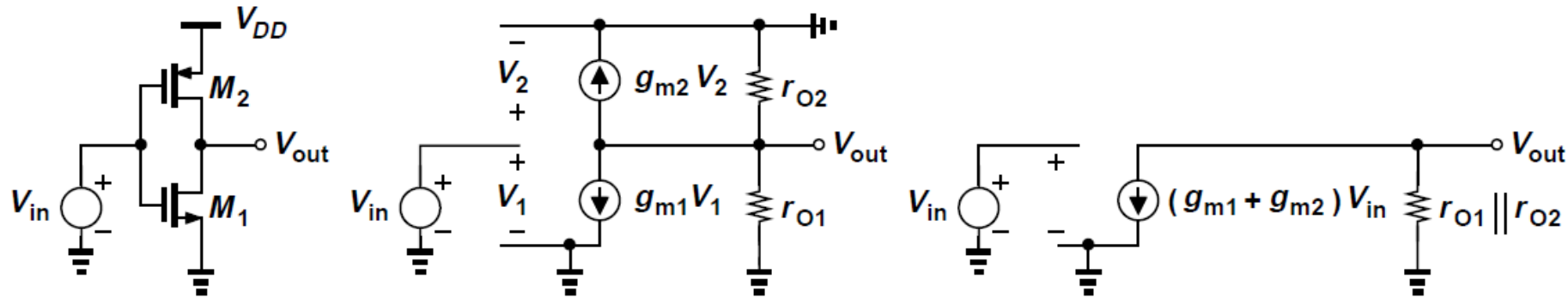

- Input signal is also applied to gate of load device, making it an “active” load
- $M_1$  and  $M_2$  operate in parallel and enhance the voltage gain
- From small-signal equivalent circuit,


$$-(g_{m1} + g_{m2})V_{in}(r_{O1} || r_{O2}) = V_{out}$$

$$A_v = -(g_{m1} + g_{m2})(r_{O1} || r_{O2})$$


- Same output resistance as CS stage with current-source load, but higher transconductance
- Bias current of  $M_1$  and  $M_2$  is a strong function of PVT (why?)
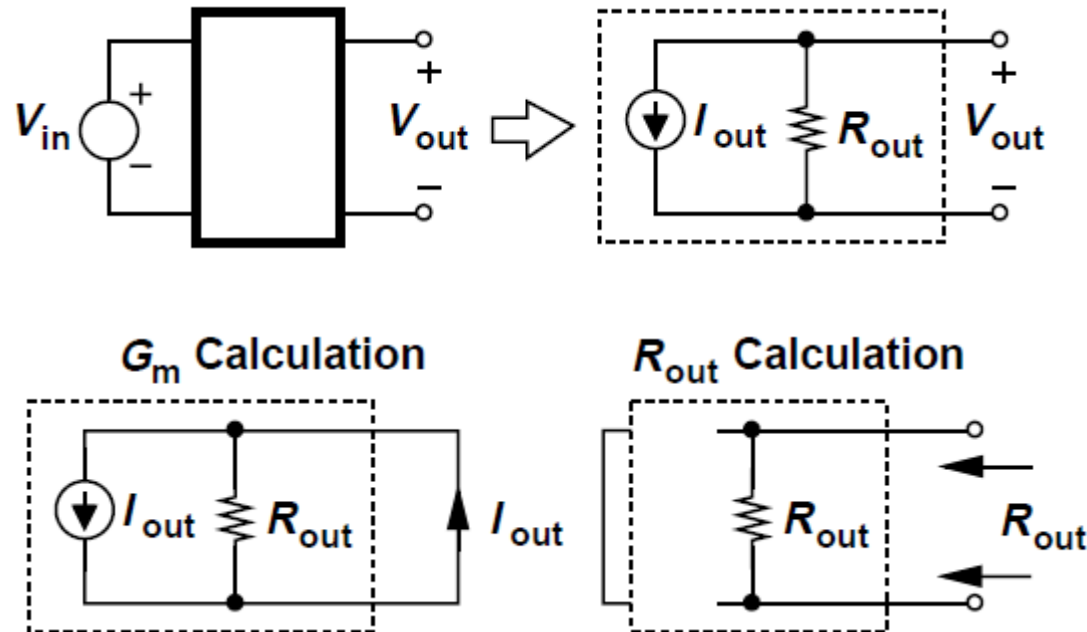
# Lemma

- In a linear circuit, the voltage gain is equal to  $-G_m R_{out}$ 
  - $G_m$  denotes the transconductance of the circuit when output is shorted to ground
  - $R_{out}$  represents the output resistance of the circuit when the input voltage is set to zero
- Norton equivalent of a linear circuit



## Using the Lemma ...

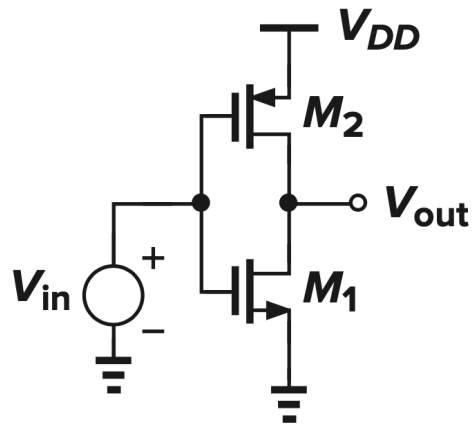


1. Find  $G_m$

2. Find  $R_{out}$


3. Gain =  $-G_m R_{out}$

# CS Stage with Source Degeneration

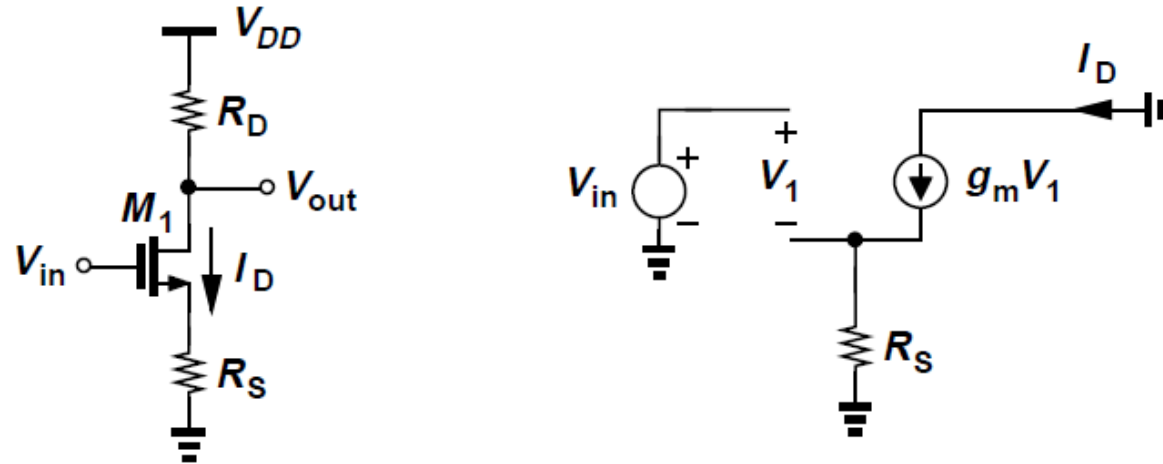

- Degeneration resistor  $R_S$  in series with source terminal makes input device more linear
  - As  $V_{in}$  increases, so do  $I_D$  and the voltage drop across  $R_S$
  - Part of the change in  $V_{in}$  appears across  $R_S$  rather than gate-source overdrive, making variation in  $I_D$  smoother
- Gain is now a weaker function of  $g_m$

# CS Stage with Source Degeneration

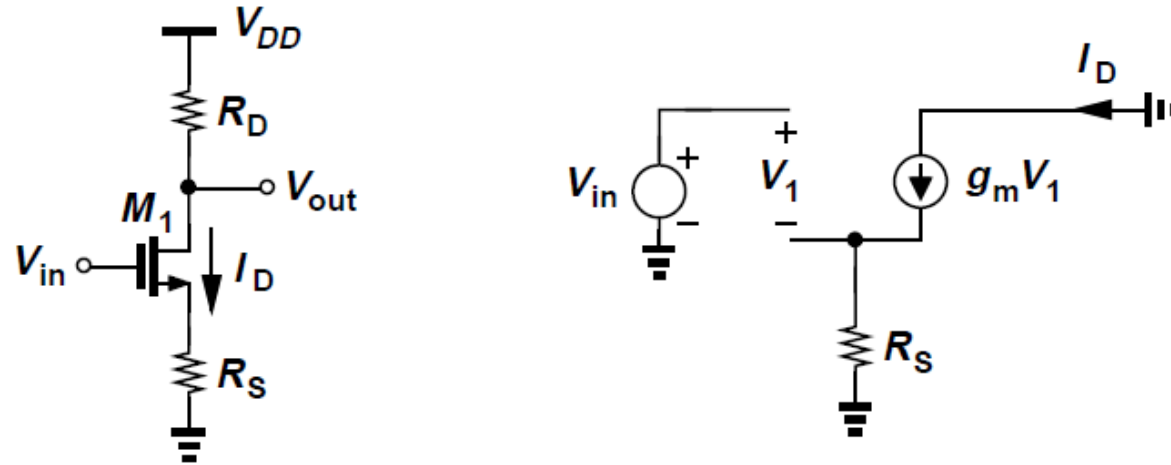

- Nonlinearity of circuit is due to nonlinear dependence of  $I_D$  (and consequently  $g_m$ ) upon  $V_{in}$
- Equivalent transconductance  $G_m$  of the circuit can be defined as


$$V_{in} = V_1 + I_{out} R_S$$

$$I_D = g_m V_1$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

$$\begin{aligned} A_v &= -G_m R_D \\ &= \frac{-g_m R_D}{1 + g_m R_S} \end{aligned}$$


# CS Stage with Source Degeneration

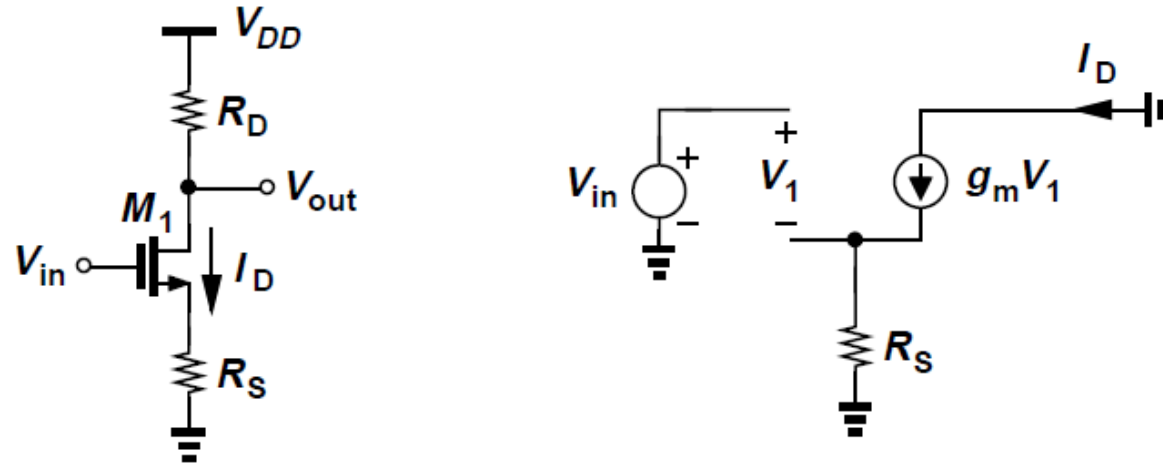

$$A_v = -G_m R_D$$
$$= \frac{-g_m R_D}{1 + g_m R_S}$$

- As  $R_S$  increases,  $G_m$  becomes a weaker function of  $g_m$  and hence  $I_D$
- For  $R_S \gg 1/g_m$ ,  $G_m \approx 1/R_S$ , i.e.,  $\Delta I_D \approx \Delta V_{in}/R_S$
- Most of the change in  $V_{in}$  across  $R_S$  and drain current becomes a “linearized” function of input voltage

# CS Stage with Source Degeneration

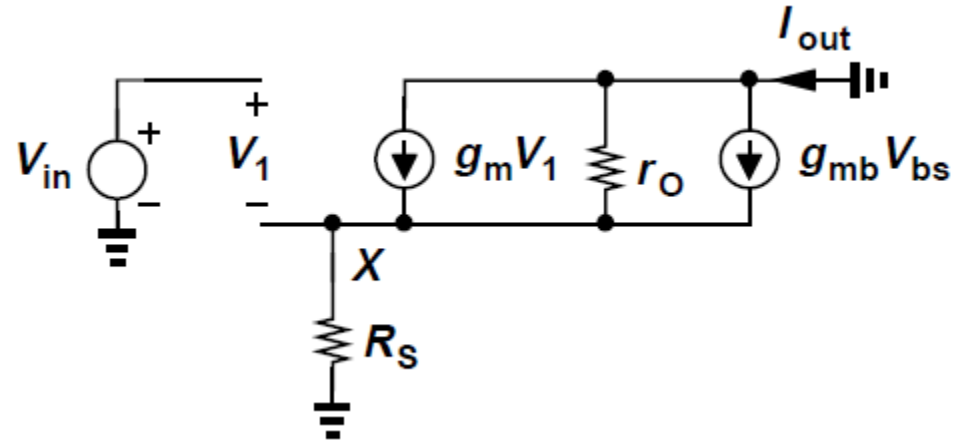

- Including body-effect and channel-length modulation,  $G_m$  is found from modified small-signal equivalent circuit

$$V_{in} = V_1 + I_{out} R_S$$

$$I_{out} = g_m V_1 - g_{mb} V_X - \frac{I_{out} R_S}{r_O}$$

$$= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_O}$$


$$G_m = \frac{I_{out}}{V_{in}}$$

$$= \frac{g_m r_O}{R_S + [1 + (g_m + g_{mb}) R_S] r_O}$$




# CS Stage with Source Degeneration: Large-signal Behavior

$R_S=0$

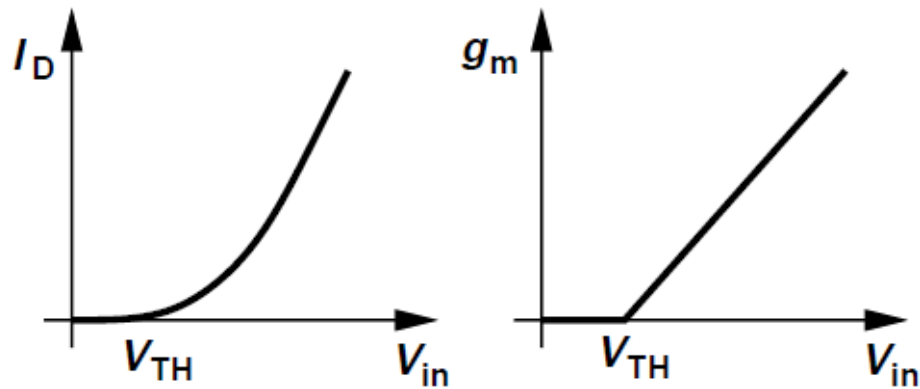

- $I_D$  and  $g_m$  vary with  $V_{in}$  as derived in calculations in Chapter 2

$R_S \neq 0$

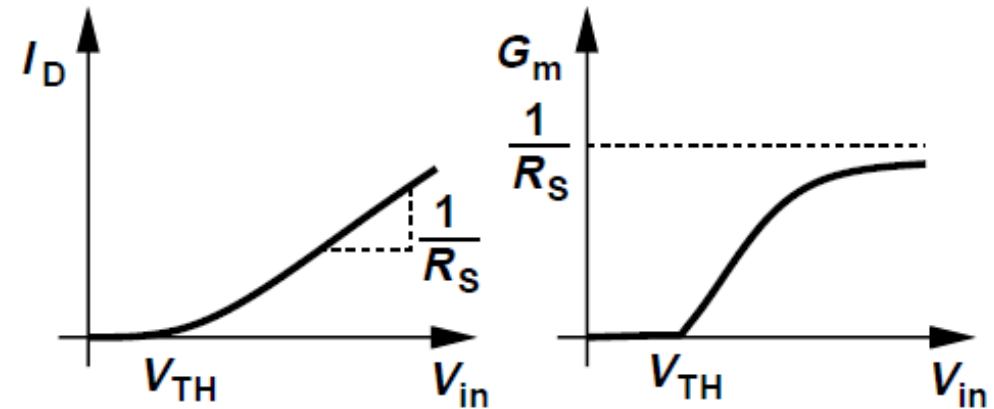


- At low current levels, turn-on behavior is similar to when  $R_S=0$  since  $1/g_m \gg R_S$  and hence  $G_m \approx g_m$
- As overdrive and  $g_m$  increase, effect of  $R_S$  becomes more significant

# CS Stage with Source Degeneration

- Small-signal derived previously can be written as


$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

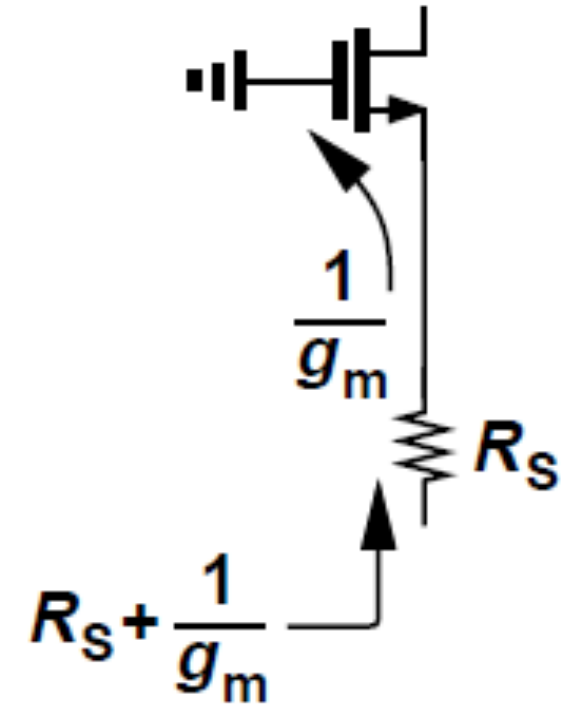- Denominator = Series combination of inverse transconductance + explicit resistance seen from source to ground
- Called “resistance seen in the source path”
- Magnitude of gain = Resistance seen at the drain/ Total resistance seen in the source path


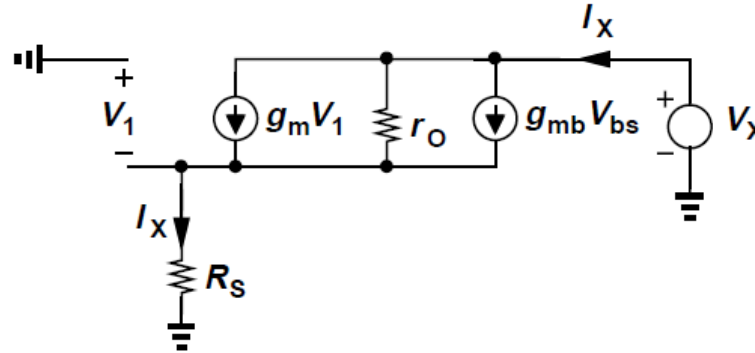
# CS Stage with Source Degeneration

- Degeneration causes increase in output resistance



- Ignoring  $R_D$  and including body effect in small-signal equivalent model,

$$V_1 = -I_X R_S,$$

$$I_X - (g_m + g_{mb})V_1 = I_X + (g_m + g_{mb})R_S I_X$$


$$r_O[I_X + (g_m + g_{mb})R_S I_X] + I_X R_S = V_X$$

$$\begin{aligned} R_{out} &= [1 + (g_m + g_{mb})R_S]r_O + R_S \\ &= [1 + (g_m + g_{mb})r_O]R_S + r_O \end{aligned}$$

- $r_o$  is boosted by a factor of  $\{1 + (g_m + g_{mb})R_S\}$  and then added to  $R_S$
- Alternatively,  $R_S$  is boosted by a factor of  $\{1 + (g_m + g_{mb})r_o\}$  and then added to  $r_o$


# CS Stage with Source Degeneration

- Compare  $R_S = 0$  with  $R_S > 0$

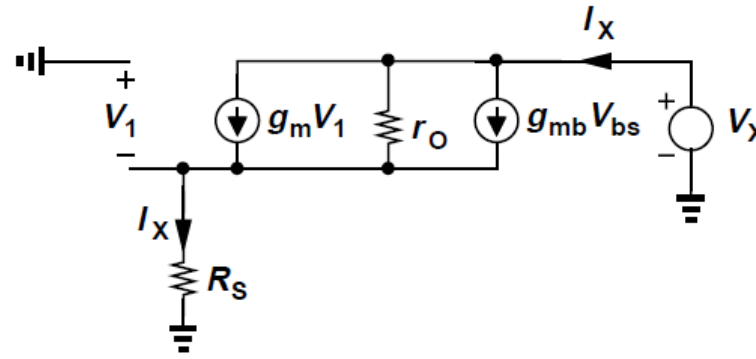

- If  $R_S = 0$ ,  $g_m V_1 = g_{mb} V_{bs} = 0$  and  $I_X = V_X / r_O$
- If  $R_S > 0$ ,  $I_X R_S > 0$  and  $V_1 < 0$ , obtaining negative  $g_m V_1$  and  $g_{mb} V_{bs}$
- Thus, current supplied by  $V_X$  is less than  $V_X / r_O$  and hence output impedance is greater than  $r_O$

# CS Stage with Source Degeneration

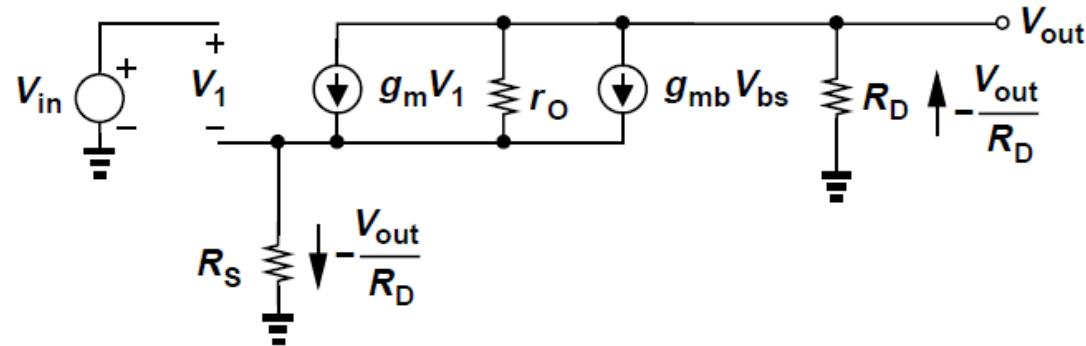


- To compute gain in the general case including body effect and channel-length modulation, consider above small-signal model
- From KVL at input,

$$V_1 = V_{in} + V_{out} R_S / R_D$$

- KCL at output gives

$$\begin{aligned} I_{ro} &= -\frac{V_{out}}{R_D} - (g_m V_1 + g_{mb} V_{bs}) \\ &= -\frac{V_{out}}{R_D} - \left[ g_m \left( V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] \end{aligned}$$

# CS Stage with Source Degeneration

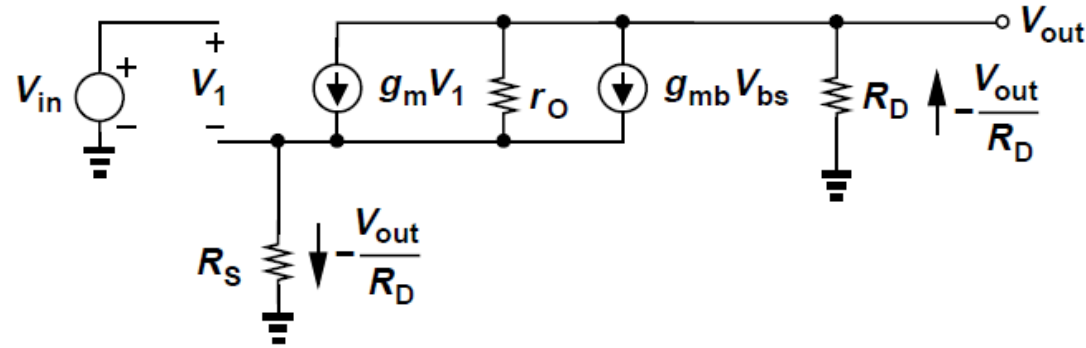

- Since voltage drops across  $r_O$  and  $R_S$  must add up to  $V_{out}$ ,

$$\begin{aligned} V_{out} &= I_{ro} r_O - \frac{V_{out}}{R_D} R_S \\ &= -\frac{V_{out}}{R_D} r_O - \left[ g_m \left( V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] r_O - V_{out} \frac{R_S}{R_D} \end{aligned}$$

- Voltage gain is therefore

$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb}) R_S r_O}$$

# *CS Stage with Source Degeneration*

- Calculate the gain using the lemma ( $A_v = -G_m R_{out}$ ):

