

Homework4 Solution

November 7, 2022

1 Problem 1

1.1 a

$$A_v = \frac{g_m R_S}{1 + g_m) R_S}$$

and

$$g_m = \frac{2I_D}{V_{OD}} = 0.01$$

\Rightarrow

$$A_V = 0.91$$

$$R_{out} = r_o // R_S // \frac{1}{g_m} \approx \frac{1}{g_m}$$

Hence, $R_{out} = 90.1\Omega$ and $R_{in} = \infty\Omega$

Also,

$$\begin{aligned} V_{DD} - V_{OUT} &> (V_{IN} - V_{OUT}) - V_{TH} = V_{GS} - V_{TH} \\ V_{GS} &> V_{TH} \end{aligned}$$

Vout max should be $\min(V_{DD} - V_{od}, V_{IN} - V_{th})$

$\Rightarrow V_{OUT} < \min(V_{DD} - V_{od}, V_{IN} - V_{th})V$

* The question did not give V_{IN} , so no points will be deducted for this voltage swing question

1.2 b

$$A_v = -\frac{g_{m1}}{g_{m2}}$$

because

$$\frac{1}{r_{o1}} = 1 / \frac{1}{\lambda I_D} = \frac{1}{10k} \Omega \text{ too small, ignore it}$$

Hence, $A_V \approx -1V$

$R_{in} = \infty\Omega$ while

$$R_{out} = r_o // \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}} = 100\Omega$$

Also,

$$V_{OUT} > V_{GS} - V_{TH} = 0.2$$

$$V_{DD} - V_{OUT} > V_{TH}$$

$\Rightarrow 2.5V > V_{OUT} > 0.2V$

Voltage swing is 0.2V-2.5V

$$1. \quad R_s = 100 \Omega$$

$$R_D = 10 k\Omega$$

$$V_{DD} = 1V$$

$$V_{Th} = 0.3V$$

$$M_nCox = 100 \mu A/V^2$$

$$(a) \quad Av = \frac{R_D}{1/g_m + R_s}$$

$$= 10.$$

$$10/g_m + 10R_s = R_D$$

$$10/g_m = 9 k\Omega$$

$$g_m = \frac{10}{9000} = \frac{1}{900} \text{ A/V} \quad V_{out} > V_{in} - V_{Th}$$

$$\therefore V_{out,DC} = \frac{V_{DD}}{2} = 0.5V$$

$$I_D = \frac{V_{DD} - V_{out,DC}}{R_D} = \frac{0.5V}{10 k\Omega} = 0.05 \text{ mA}$$


$$g_m = \sqrt{2MnCox \frac{w}{L} I_D} = MnCox \frac{w}{L} (V_{GS} - V_{Th})$$

$$\frac{w}{L} = \frac{g_m^2}{2MnCox I_D} = \frac{(1/900)^2}{2 \times 100 \times 10^{-6} \times 0.05 \times 10^{-3}}$$

$$= 123.5$$

$$V_{GS} = \frac{g_m}{MnCox \frac{w}{L}} + V_{Th} = 0.39V$$
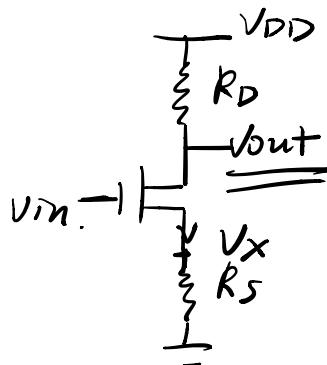
$$V_X = I_D \cdot R_s = 0.05 \times 10^{-3} \text{ A} \cdot 100 \Omega = 0.005V$$



$$V_{out,max} = V_{DD}$$

$$V_{out,min} =$$

$$\therefore V_{in} = V_{GS} + V_x = 0.395V$$

b) With $\lambda \neq 0$, we have r_o in the small signal model. And r_o is in parallel with R_D in the small signal model. in series with R_s (but R_s is very small if neglect it)

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 0.05 \times 10^{-3}} = 200 \text{ k}\Omega$$

So, the new gain

$$r_o \parallel R_D = 9.5 \text{ k}\Omega$$

$$\begin{aligned} A_{v'} &= \frac{R_D \parallel r_o}{1/g_m + R_S} \\ &= \frac{9.5 \text{ k}\Omega}{0.9 \text{ k}\Omega + 0.1 \text{ k}\Omega} = 9.5, \text{ drop a little bit.} \end{aligned}$$

c) $V_{out, max} = V_{DD}$ when $I_D = 0$.

$$\begin{aligned} V_{out, min} &= V_{GS} - V_{Th} + V_x \\ &= 0.395 - 0.3 \\ &= 0.095 V \end{aligned}$$

So the voltage swing is $\frac{1 - 0.095}{2} \cong 0.45V$

(d) t_{ox} will affect g_m .


$$g_m = M_n C_{ox} \frac{W}{L} (V_{GS} - V_{Th})$$

$$t_{ox} \uparrow \text{ by } 10\% \rightarrow C_{ox}' = \frac{1}{1.1} C_{ox}$$

$$g_m' = 0.91 g_m \quad A_v' = \frac{R_D}{1/0.91 g_m + R_S} = \frac{10 \times 10^3}{989 + 10} \approx 0.91 C_{ox}$$

$$= 9.18.$$

(a) w/o source degeneration.

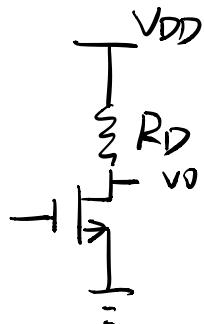

Assume that the V_{OD} is the same in this case.

Then the gain is

$$\begin{aligned} A_{v,w/o} &= (R_D // r_o) g_m \\ &= 9.5 k\Omega \times \frac{1}{900} \Omega^{-1} \\ &= 10.6 \end{aligned}$$


Then after the oxide gets 10% thicker,
 $g_m' = 0.91 g_m$.

$$A_{v,w/o} = 9.5 k\Omega \times 0.91 \times \frac{1}{900} = 9.6$$

With degenerate : $9.5 \rightarrow 9.18$ (3% change)

without degenerate : $10.6 \rightarrow 9.6$ (9% change)

2. (a)

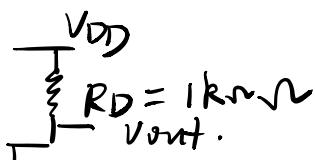

$$V_{in} - \frac{V_{DD}}{2} = I_D R_D$$
$$= \frac{0.5}{1000} = 0.5 \text{ mA}$$

$$\Delta V = g_m R_D = 10$$

$$g_m = \frac{10}{1 \times 10^3 \text{ V}} = 10^{-2} \text{ V}^{-1}$$
$$= \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\frac{W}{L} = g_m^2 / (2 \mu_n C_{ox} I_D)$$
$$= 10^{-4} / (2 \times 10^{-4} \times 0.5 \times 10^{-3})$$
$$= 1000$$

$$(V_{GS} - V_{Th}) = \frac{g_m}{MnC_{ox} \frac{w}{L}} = \frac{10^{-2}}{10^{-4} \times 1000} = 0.1V$$

$$V_{GS, bias} = 0.1 + 0.3 = 0.4V$$

(b) in the small signal model, R_D is in parallel with R_L .

$$\text{So the new } R'_D = R_L // R_D = \frac{1000 * 100}{1000 + 100} = 91\text{ m}\Omega$$

$$\text{Av} = R'_D g_m = 91 \times 10^{-2} = 0.91, \text{ very small!}$$

(c) I will need increase $(\frac{w}{L})$ dramatically, but it's unrealistic


$$(d) \quad \boxed{V_{DD} \cdot I_D} = 1V \times 0.5mA = 0.5mW.$$

$$= \frac{1}{100 // 100} = \frac{10^5}{1000}$$

$$(e) \quad R_s I_{D2} = \frac{V_{DD}}{2} \Rightarrow I_{D2} = \frac{V_{DD}}{2R_s} = \frac{1V}{2 \times 1k\Omega} = 0.5mA$$

$$Ar = \frac{\frac{g_m}{2} R_s // R_L}{g_m R_s + \frac{1}{2}} = 0.5 \Rightarrow \frac{1}{2} g_m R_s // R_L + \frac{1}{2} = g_m R_s // R_L$$
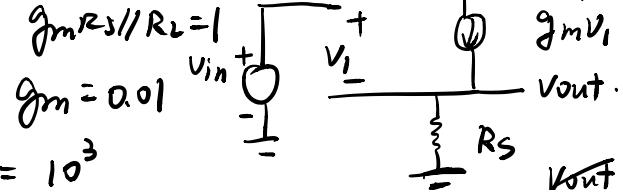
$$\frac{w}{L} = \frac{\frac{g_m}{2} R_s // R_L}{2MnC_{ox} I_{D2}} = \frac{10^{-4}}{10^{-4}} = 10^3$$



$$(V_{GS} - V_{Th}) = \frac{g_m}{\mu_n C_{ox} \times W/L} = \frac{10^{-2}}{\frac{10^{-4} \times 10^3}{0.1}} = 0.1$$

$$V_{in, bias} = 0.1 + \frac{V_{DD}}{2} + 0.3 = 0.9 \text{ V}$$

$$R_{out} = \frac{+V_{out} \cdot g_m + \frac{V_{out}}{R_s}}{g_m R_s + 1}$$

$$G_m = g_m$$

(f) Gain of Common source stage should be 20

$$R_D g_m = 20 \quad g_m = \frac{20 \text{ V}}{1 \text{ k}\Omega} = 2 \times 10^{-2} \text{ A}^{-1}$$

$$V_{out} = 0.5 + 0.4 = 0.9 \text{ V} \quad I_D = \frac{1 - 0.9}{1000} = 0.1 \text{ mA}$$

$$W/L = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{4 \times 10^{-4}}{2 \times 10^{-4} \times 0.1 \times 10^{-3}} = 2 \times 10^4.$$

(g)

$$P = 0.5 \text{ mA} \times 1 \text{ V} + 0.1 \text{ mA} \times 1$$

$$= 0.6 \text{ mW} > 0.5 \text{ mW in (d)}$$


$$V_{GS1} - V_{Th} = \frac{g_m}{\mu_n C_{ox} W/L} = \frac{2 \times 10^{-2}}{10^{-4} \times 2 \times 10^4} \text{ V} = 10^3 \text{ V}$$

$$V_{GS1} = 0.31 \text{ V}$$

3.


(a) For gain.

$$V_{GS} = -V_{in}$$

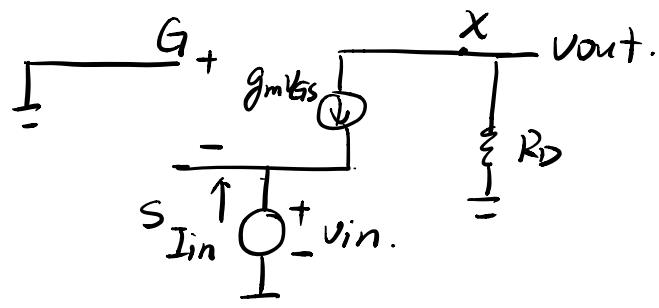

$$G_m = \frac{I_{out}}{V_{in}} = -g_m. \quad \text{Small signal model.}$$

$$R = R_D$$

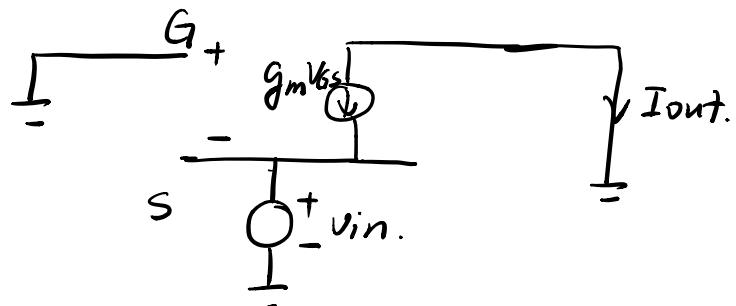

Determine G_m .

$$\Delta V = -G_m \cdot R = g_m R_D = 50$$

Input impedance $Z_{in} = 1/g_m$
 $= 50 \Omega$

$$g_m = \sqrt{2M_nC_{ox}\frac{W}{L}I_1} \Rightarrow g_m = 0.02 \Rightarrow R_D = 2500 \Omega$$

$$\Rightarrow \frac{W}{L} = \frac{g_m^2}{2M_nC_{ox}I_1} = \frac{4 \times 10^{-4}}{2 \times 10^{-4} \times 0.2 \times 10^{-3}} = 10^4$$

$$V_{GS} - V_{Th} = \frac{g_m}{M_nC_{ox}\frac{W}{L}} = \frac{0.02}{10^{-4} \times 10^4} = 0.02 V$$

$$(b) V_{GS} - V_{Th} = 0.5 - 0.3 = 0.2 V$$

$$I_1 = 0.2 \text{ mA}$$

$$= \frac{1}{2} M_n C_{ox} \frac{W}{L} (V_{GS} - V_{Th})^2$$

$$\Rightarrow \frac{W}{L} = \frac{2I_1}{M_n C_{ox} (V_{GS} - V_{Th})^2}$$

$$= 100$$

$$(c) V_x > V_b' - V_{Th}$$

$$V_{out} - V_x > V_b - V_{Th}$$


$$V_{out} > V_x + (V_{GS} - V_{Th}) > V_b' - V_{Th} + (V_{GS} - V_{Th})$$

$$\approx 0.2 \text{ V}$$

$$\text{Upper limit: } V_{DD} - I_D R_D = 1 - 0.2 \times 10^{-3} \times 2500 \\ = 0.5 \text{ V.}$$


Voltage swing : 0.15V

(d) The small signal model.

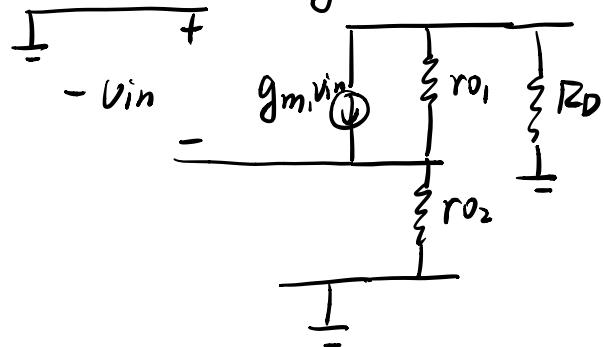

Use Lemma.

• Determine G_m .

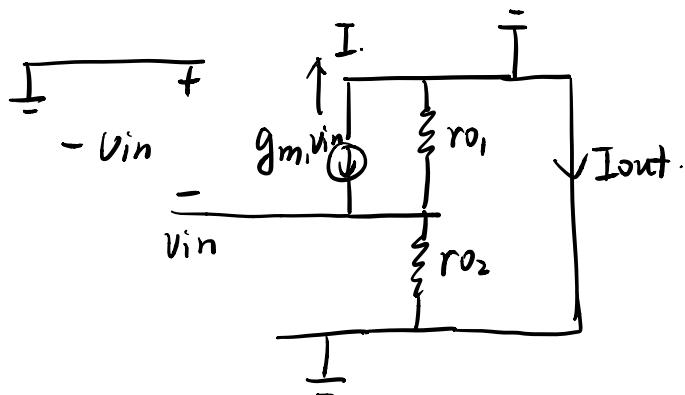

$$I_{out} = g_m v_{in} + v_{in}/r_01 \parallel r_02$$

$$G_m = g_m + \frac{1}{r_01 \parallel r_02} \quad r_0 = \frac{1}{\lambda_1 I_D} = \frac{1}{0.1 \times 0.2 \text{ mA}}$$

$$R = (r_o + r_{o_2}) // R_D = 50k\text{m}$$

$$Av = G_m R = \left(g_m + \frac{1}{r_{o_1} // r_{o_2}} \right) (r_{o_1} + r_{o_2}) // R_D \approx R_D$$

Note previously $Av = \left(g_m + \frac{1}{r_{o_1}} \right) r_{o_1} // R_D$

$$= \left(0.02 + \frac{1}{50000} \right) 50k // 2.5k$$

$$= 47.6$$

(Note in problem a we ignored r_o)

$$\text{Now } Av' = \left(0.02 + \frac{1}{25000} \right) 100k // 2.5k$$

= 48.9 , the total gain slightly increases.

$$(e) f = \frac{1}{R_{in}C}$$

$$= \frac{1}{50C} \leq 300$$

$$\Rightarrow C \geq \frac{1}{6} F$$