

# EE 332: Devices and Circuits II



## Lecture 6: Frequency Response

Prof. Sajjad Moazeni

[smoazeni@uw.edu](mailto:smoazeni@uw.edu)

Autumn 2022

# MOS Device Capacitances

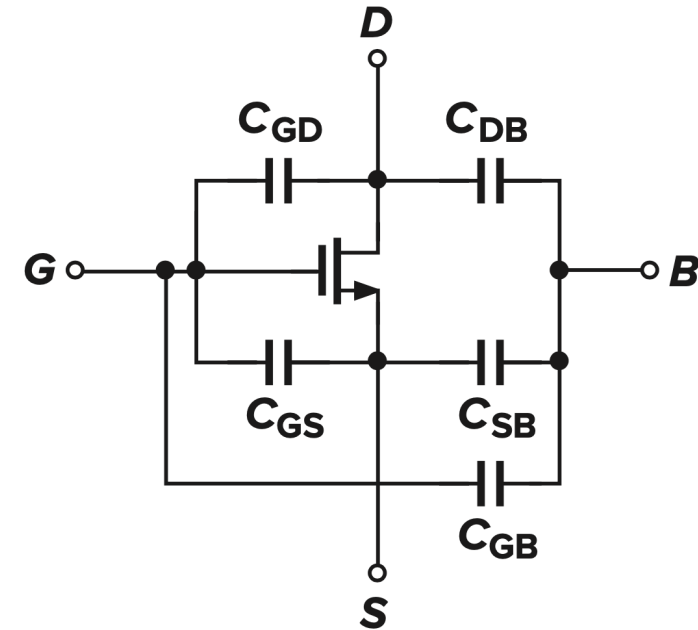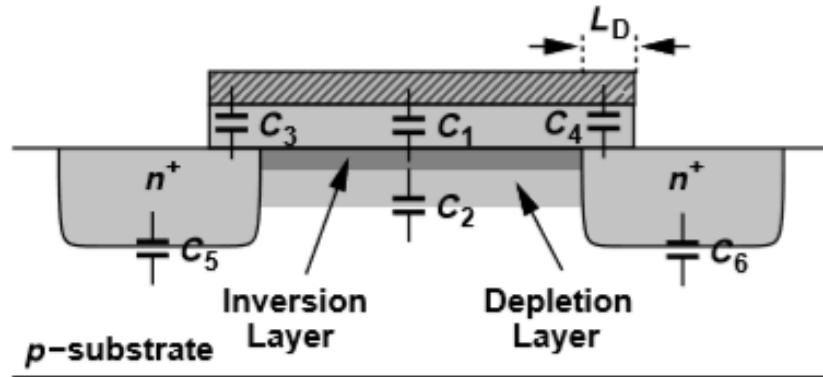


- Device capacitances cause frequency dependent  $A_v$ ,  $Z_{in}$ ,  $Z_{out}$ , etc.
- Capacitance exists almost between every two of the four terminals
- Larger device  $\rightarrow$  Larger caps!

# Frequency Response

$$T(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{s^n + b_{n-1} s^{n-1} + \dots + b_0} \quad T(s) = a_m \frac{(s - Z_1)(s - Z_2) \dots (s - Z_m)}{(s - P_1)(s - P_2) \dots (s - P_n)}$$




$$H(s) = \frac{b_n}{a_m} \cdot \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \dots \left(1 + \frac{s}{\omega_{zn}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \dots \left(1 + \frac{s}{\omega_{pm}}\right)}$$

# General Considerations

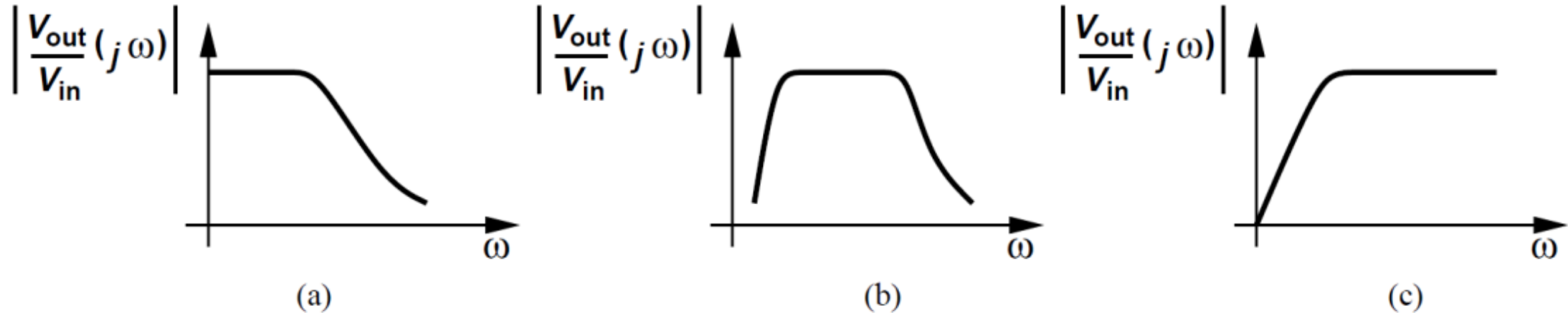


- Zeros and poles are respectively defined as the roots of the numerator and denominator of the transfer function.
- In this chapter, we are primarily interested in the magnitude of the transfer function.
- The magnitude of a complex number  $a + jb$  is given by  $\sqrt{a^2 + b^2}$

# Bode Plot

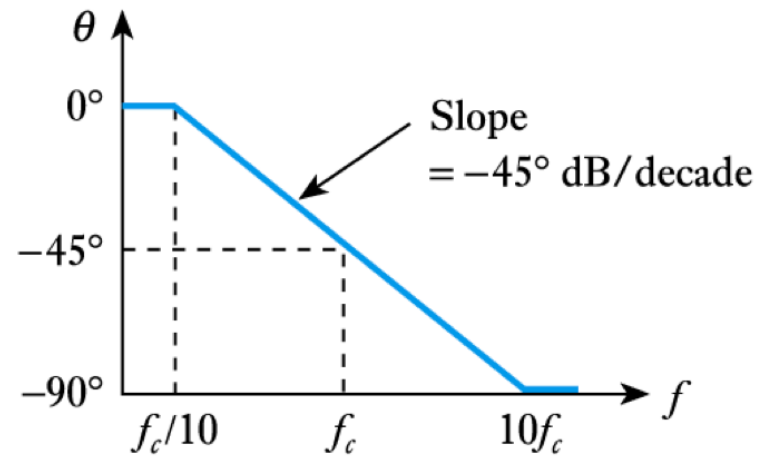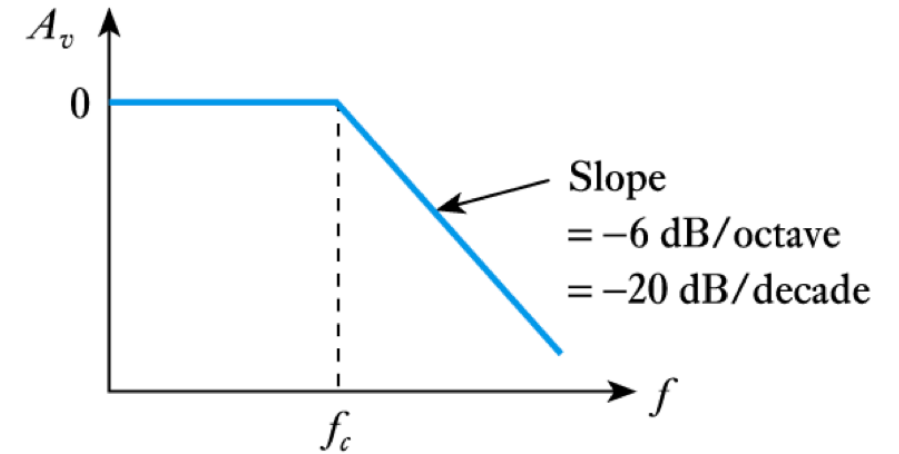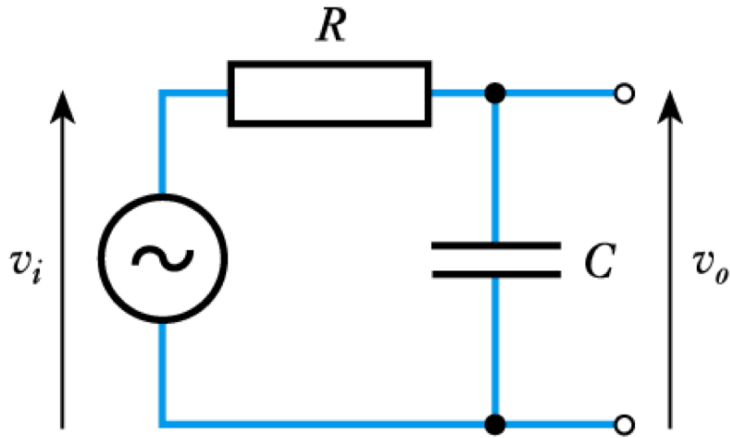


(b) Low-pass circuit

## Example 1

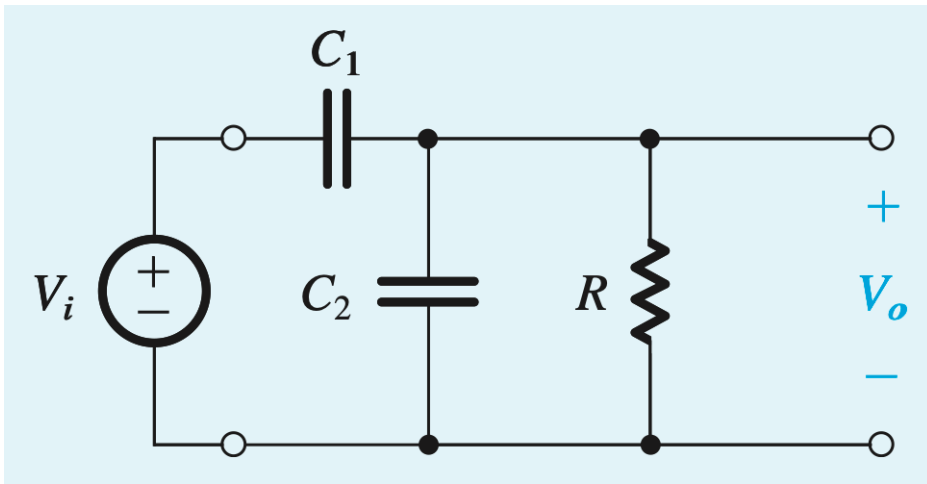


# Association of Poles with Nodes

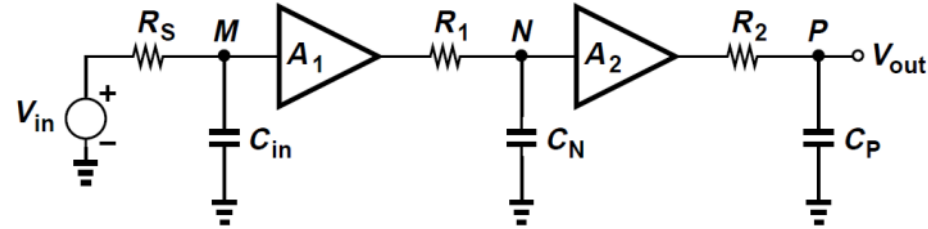


- The overall transfer function can be written as

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + R_S C_{in} s} \cdot \frac{A_2}{1 + R_1 C_N s} \cdot \frac{1}{1 + R_2 C_P s}$$

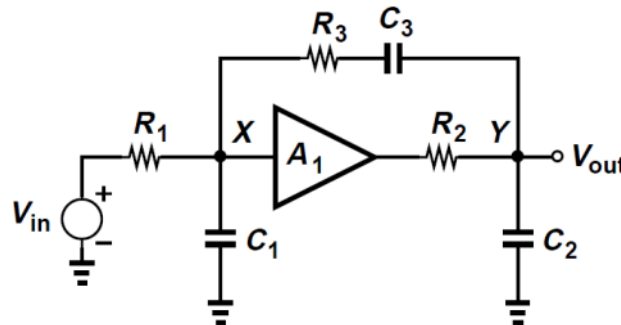- Each node in the circuit contributes one pole to the transfer function.
- Not valid in general. Example:



# Example: Common-Gate Stage

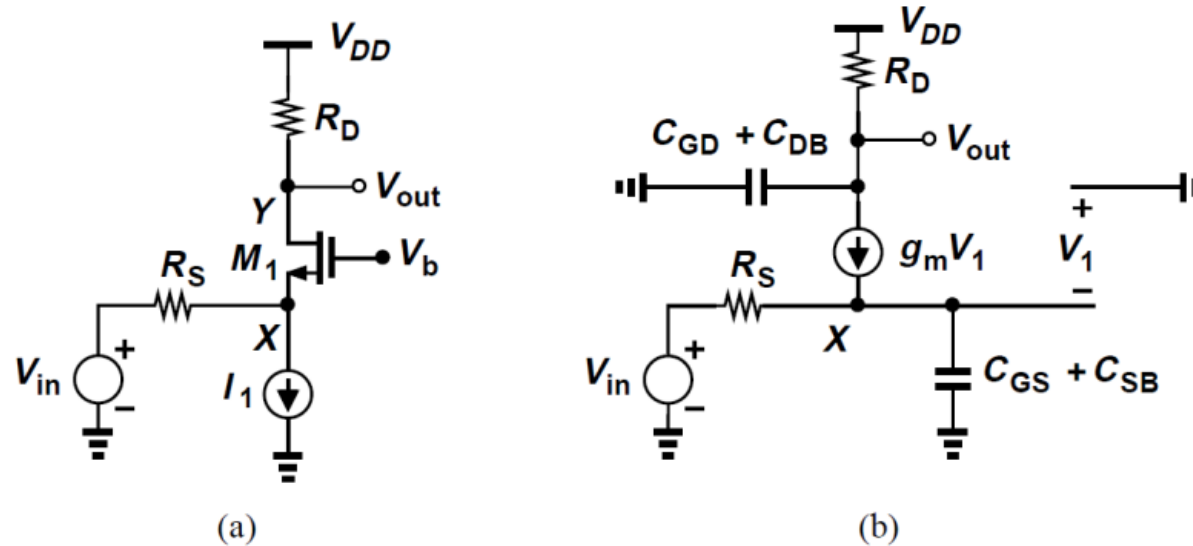

- At node X:

$$\omega_{in} = \left[ (C_{GS} + C_{SB}) \left( R_S \parallel \frac{1}{g_m + g_{mb}} \right) \right]^{-1}$$

- At node Y:


$$\omega_{out} = [(C_{DG} + C_{DB})R_D]^{-1}$$

- The overall transfer function:

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \cdot \frac{1}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$






# Miller effect

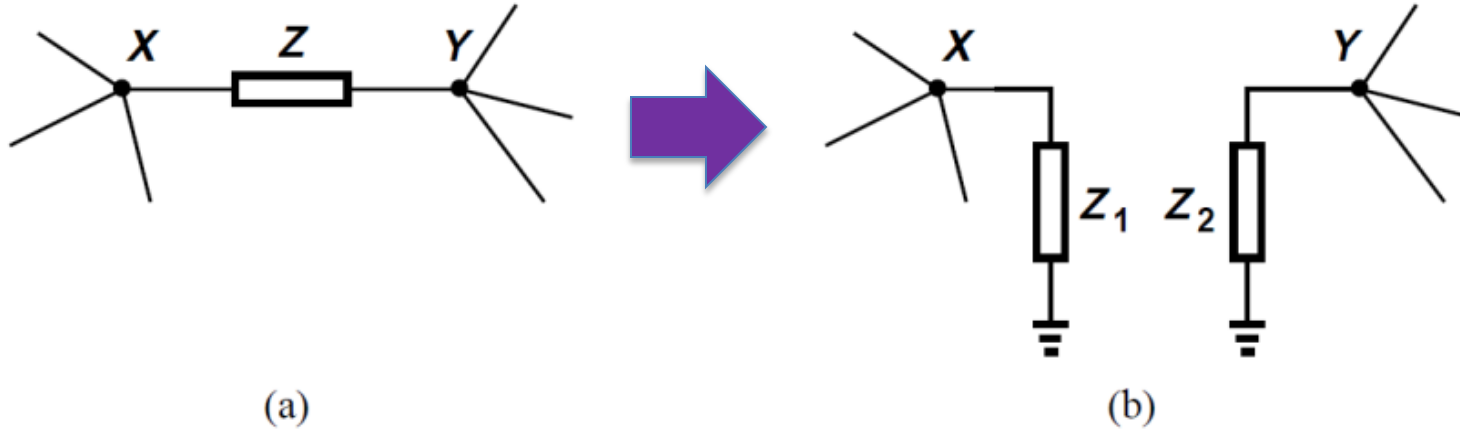


$$\frac{V_X - V_Y}{Z} = \frac{V_X}{Z_1} \quad \Rightarrow \quad Z_1 = \frac{Z}{1 - \frac{V_Y}{V_X}} \quad Z_2 = \frac{Z}{1 - \frac{V_X}{V_Y}}$$


# Example

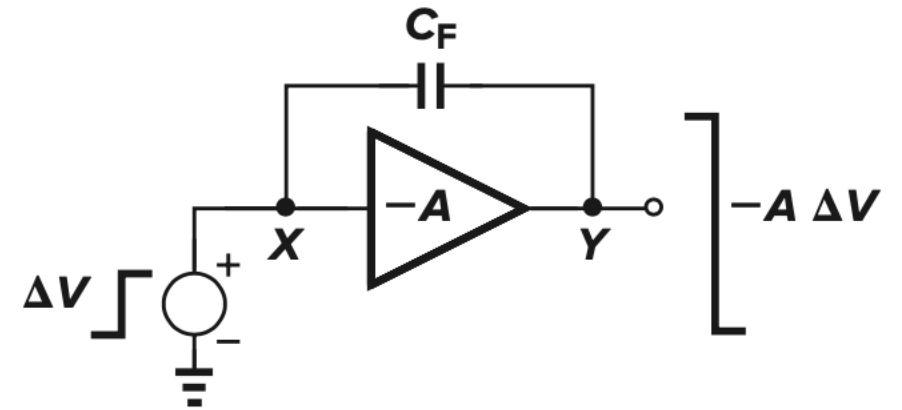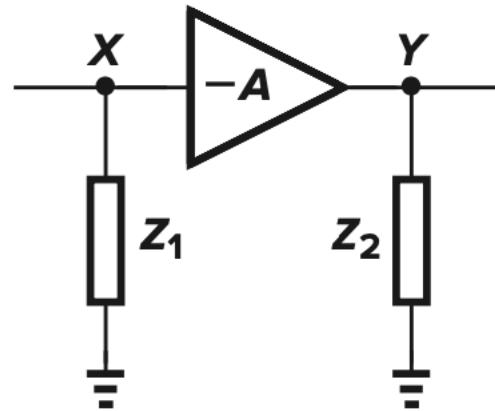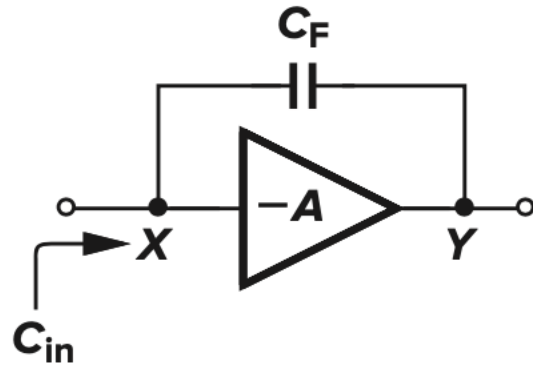

# Validity of Miller's Theorem

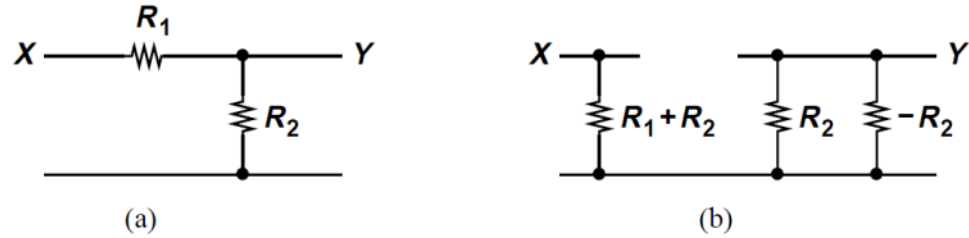

Improper application of Miller's theorem

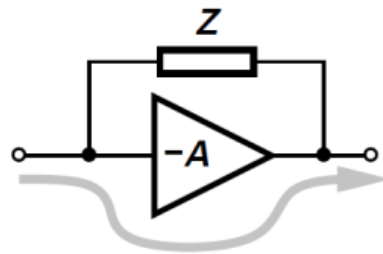


Main Signal Path

Typical case for valid application of Miller's theorem.

- Miller's theorem does not stipulate the conditions under which this conversion is valid.
- If the impedance  $Z$  forms the **only signal path between X and Y**, then the conversion is often invalid.

## Example


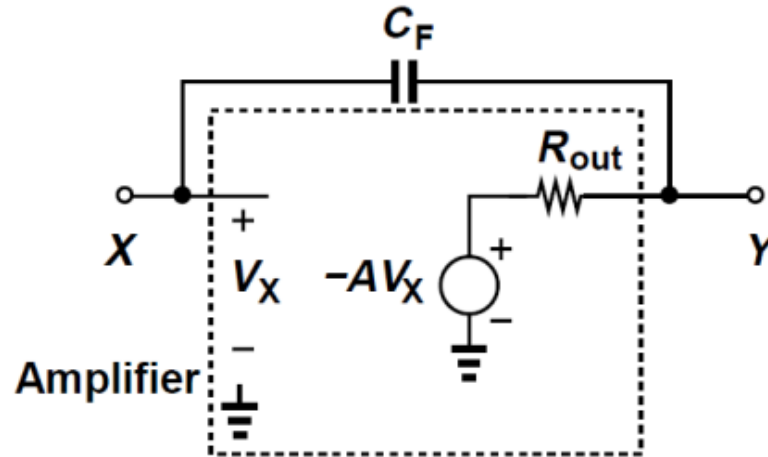


- The value of  $A_v = V_Y / V_X$  must be calculated at the frequency of interest.
- In the figure, the equivalent circuit reveals that  $V_Y \neq -AV_X$  at high frequencies.
- In many cases we use the low-frequency value of  $V_Y / V_X$  to gain insight.
- We call this approach “Miller’s approximation.”
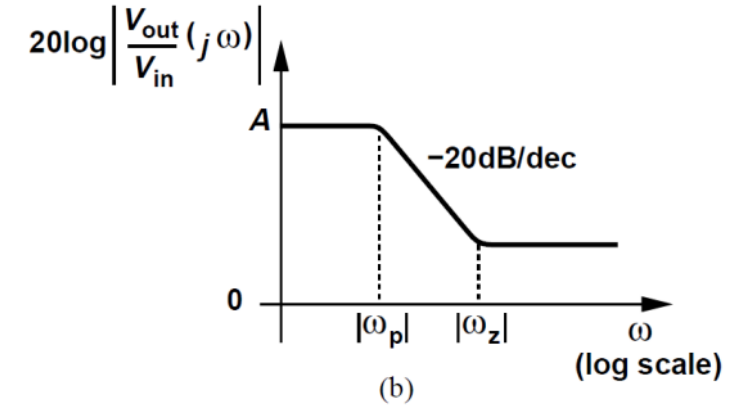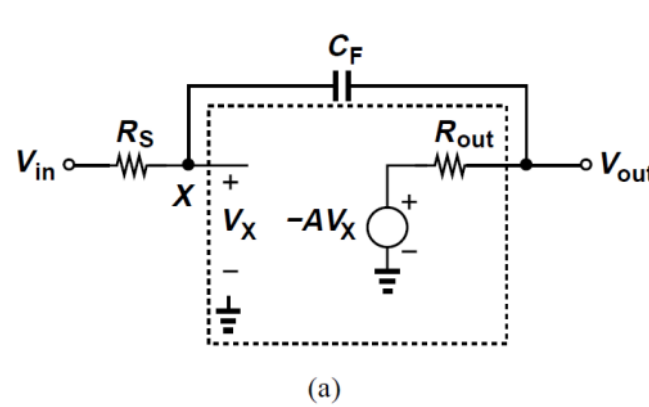
# Example


- Direct Calculation:

$$\frac{V_{out}}{V_{in}}(s) = \frac{R_{out}C_F s - A}{[(A + 1)R_S + R_{out}]C_F s + 1}$$



- Miller Approximation:
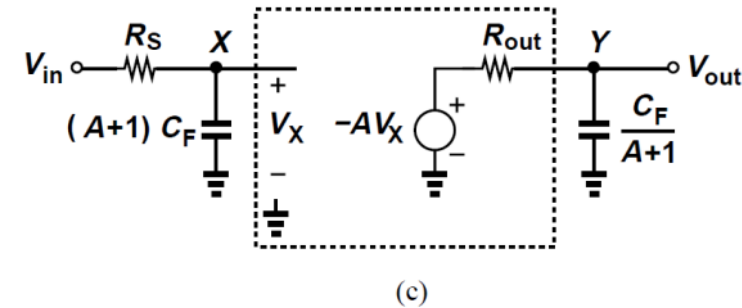
$$\frac{V_{out}}{V_{in}}(s) = \frac{-A}{[(1 + A)R_S C_F s + 1] \left( \frac{1}{1 + A^{-1}} C_F R_{out} s + 1 \right)}$$





- Miller's approximation has eliminated the zero and predicted two poles for the circuit!

# Miller's approximation

- Miller's approximation:
  - (1) it may eliminate zeros
  - (2) it may predict additional poles
  - (3) it does not correctly compute the “output” impedance

# Common-Source Stage

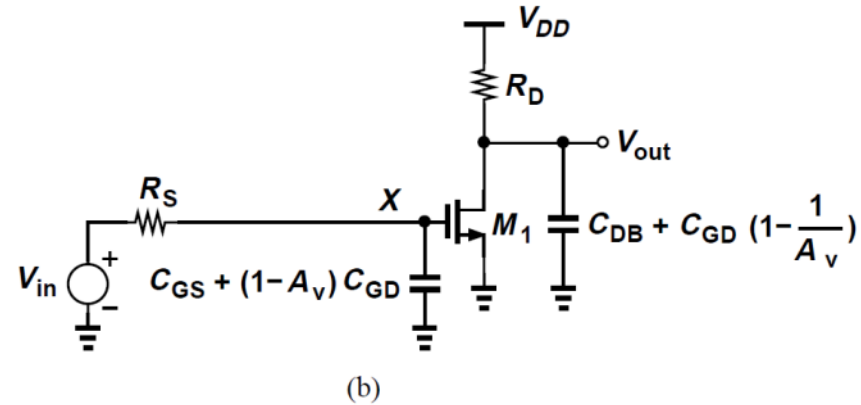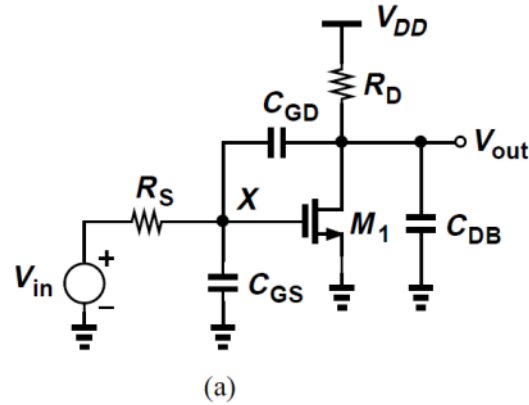

- The magnitude of the “input” pole (using Miller approximation):


$$\omega_{in} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D) C_{GD}]}$$

- At the output node

$$\omega_{out} = \frac{1}{R_D (C_{DB} + C_{GD})}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

# Direct Analysis

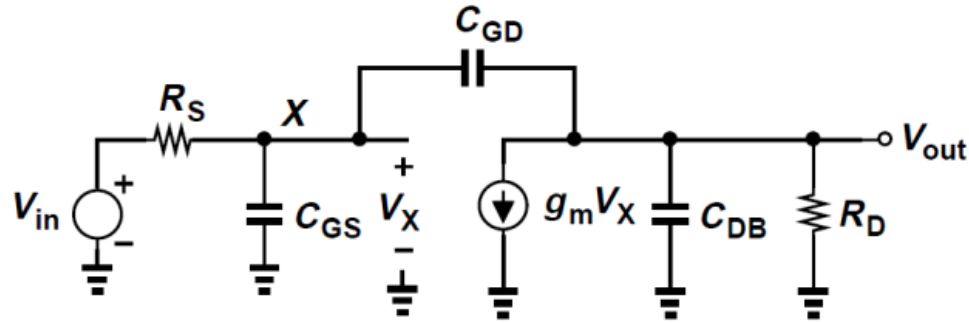

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

- While the denominator appears rather complicated, it can yield intuitive expressions for the two poles.  $|\omega_{p1}| \ll |\omega_{p2}|$
- “Dominant pole” approximation.

$$\omega_{p1} = \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$$

- The intuitive approach provides a rough estimate with much less effort.





# *“Dominant Pole” Approximation*

- Assume a two pole transfer function:

$$\begin{aligned} D &= \left( \frac{s}{\omega_{p1}} + 1 \right) \left( \frac{s}{\omega_{p2}} + 1 \right) \\ &= \frac{s^2}{\omega_{p1}\omega_{p2}} + \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1 \end{aligned}$$

- If one pole will be dominant ( $|\omega_{p1}| \ll |\omega_{p2}|$ ), then:


# Zero in Transfer Function

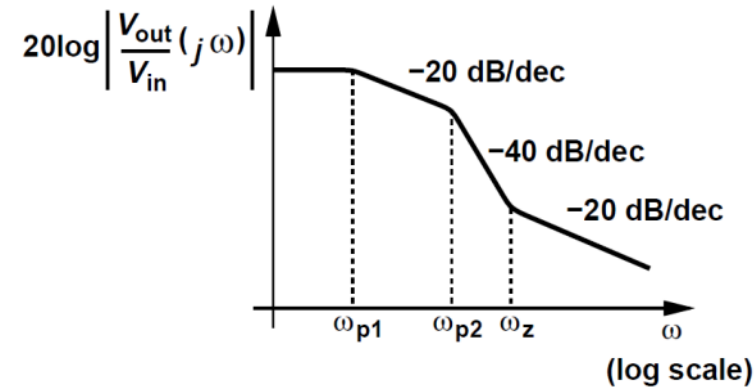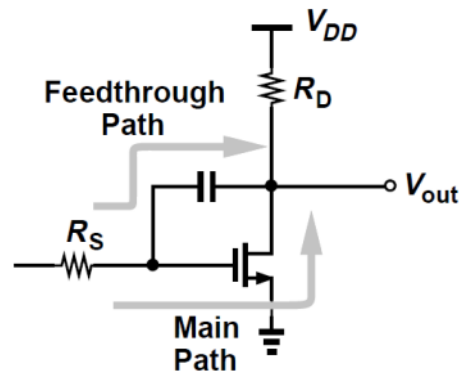


$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

- The transfer function of exhibits a zero given by
 
$$\omega_z = +g_m / C_{GD}$$
- CGD provides a feedthrough path that conducts the input signal to the output at very high frequencies.

# Source Followers

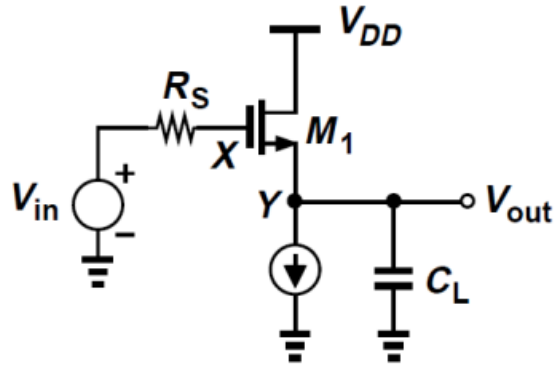

(a)

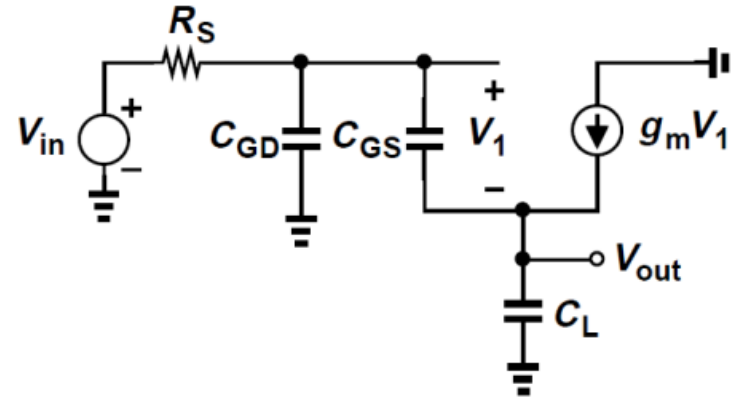

(b)

- The strong interaction between nodes X and Y through  $C_{GS}$  makes it difficult to associate a pole with each node.


$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

- Contains a zero in the left half plane. Why?
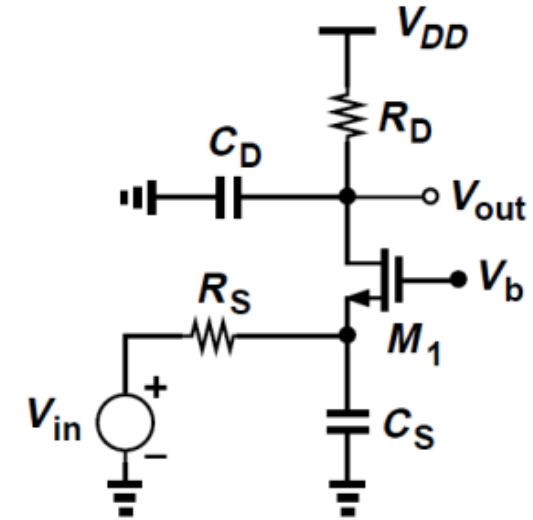
# Common-Gate Stage


- A transfer function (w/o channel length modulation):

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left(1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}}s\right)(1 + R_D C_D s)}$$



- No Miller multiplication of capacitances.
- $R_D$  is typically maximized, so the dc level of the input signal must be quite low.
- As an amplifier in cases where a low input impedance is required in cascode stages.

# Cascode Stage

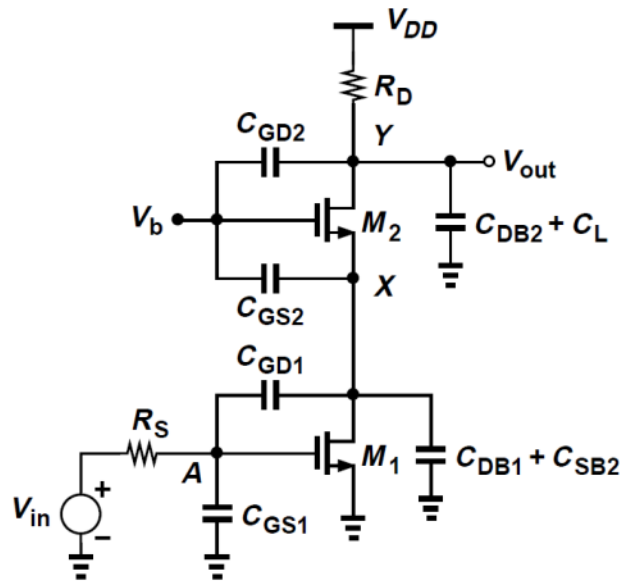

High-frequency model of a cascode stage.


$$\omega_{p,A} = \frac{1}{R_S \left[ C_{GS1} + \left( 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$

$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}}$$

$$\omega_{p,Y} = \frac{1}{R_D (C_{DB2} + C_L + C_{GD2})}$$

- Miller effect is less significant in cascode amplifiers than in common-source stages.
- But  $\omega_{p,X}$  is typically quite higher than the other two.
- What if  $R_D$  is replaced by a current source?
  - Pole at node X may be quite lower, but transfer function will not affect much by this. See example.

# Differential Pair

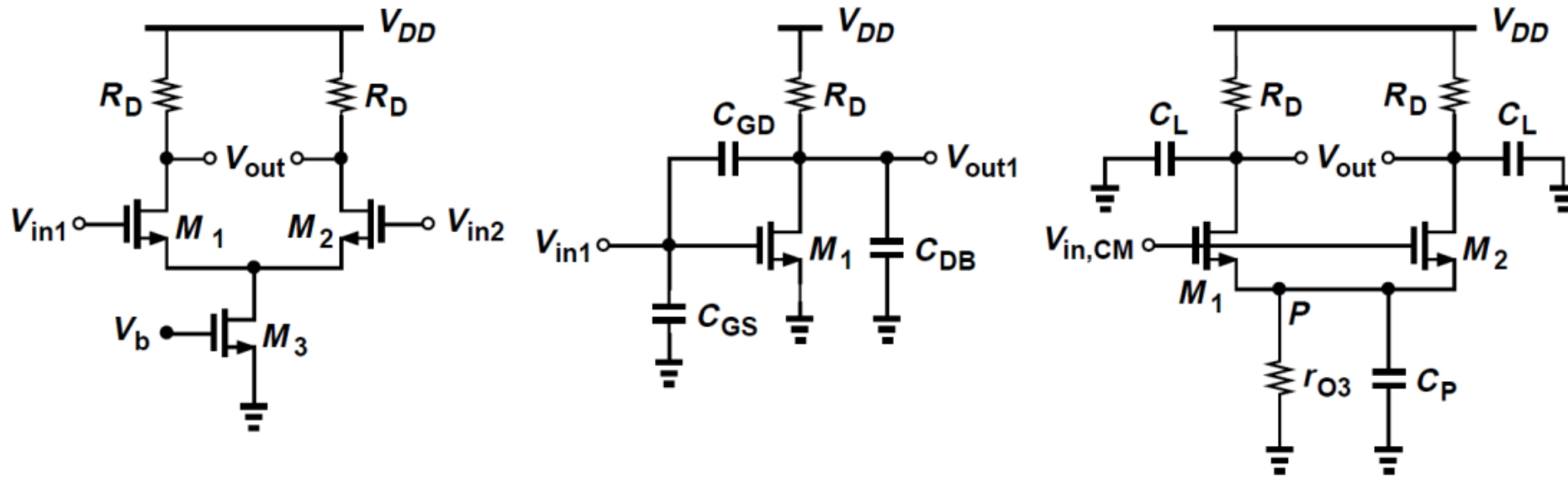


- For differential signals, the response is identical to that of a common-source stage.
- the common-mode rejection of the circuit degrades considerably at high frequencies.

$$A_{v,CM} = - \frac{\Delta g_m \left[ R_D \parallel \left( \frac{1}{C_L s} \right) \right]}{(g_{m1} + g_{m2}) \left[ r_{O3} \parallel \left( \frac{1}{C_P s} \right) \right] + 1}$$


- Channel-length modulation, body effect, and other capacitances are neglected.

# Differential Pair

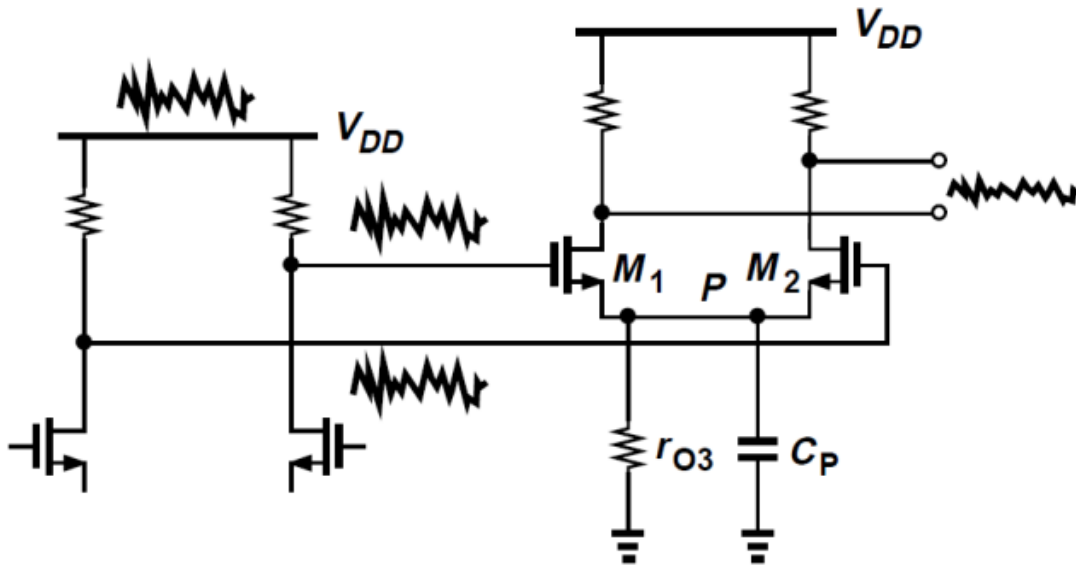




$$\text{CMRR} \approx \frac{g_m}{\Delta g_m} \left[ 1 + 2g_m \left( r_{O3} \parallel \frac{1}{C_P s} \right) \right]$$
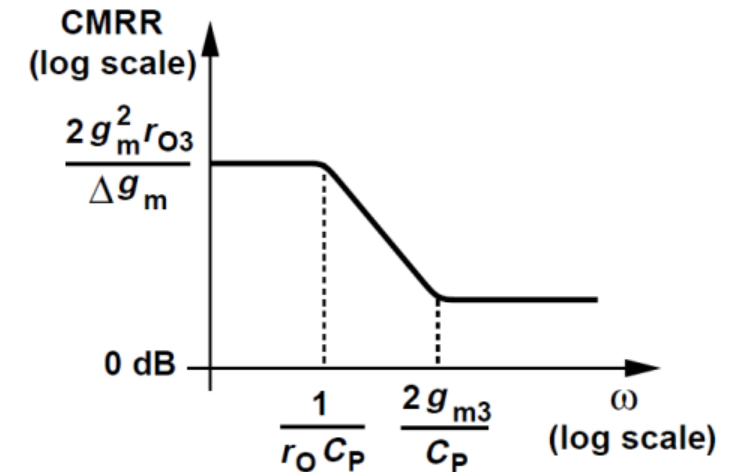
$$\approx \frac{g_m}{\Delta g_m} \frac{r_{O3} C_P s + 1 + 2g_m r_{O3}}{r_{O3} C_P s + 1}$$



- This transfer function contains a zero and a pole.
- The magnitude of the zero is much greater than the pole.


# Differential Pair

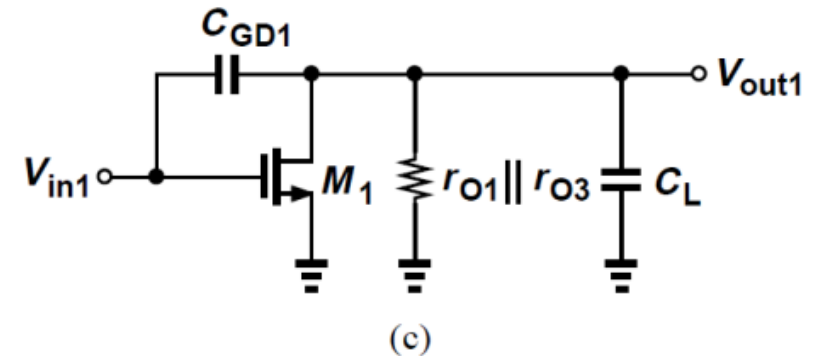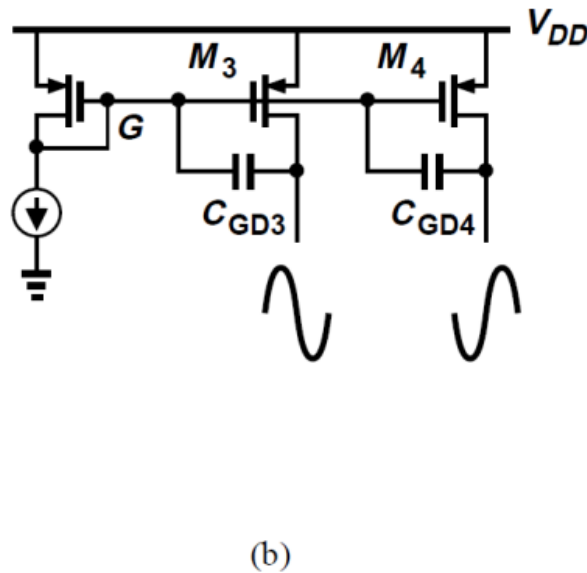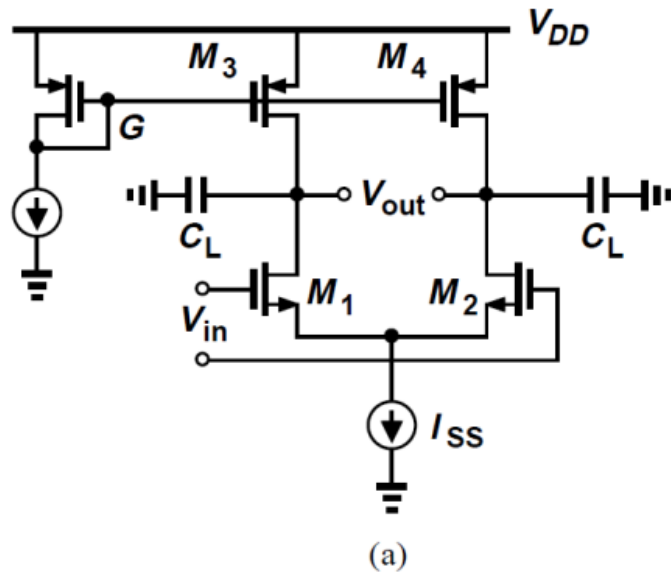

- Frequency response of differential pairs with high-impedance loads.
- Fig (b)  $C_{GD3}$  and  $C_{GD4}$  conduct equal and opposite currents to node G, making this node an ac ground.
- The differential half circuit is depicted in Fig. (c).
- More in chapter 10 ...




# Differential Pair with Active Load

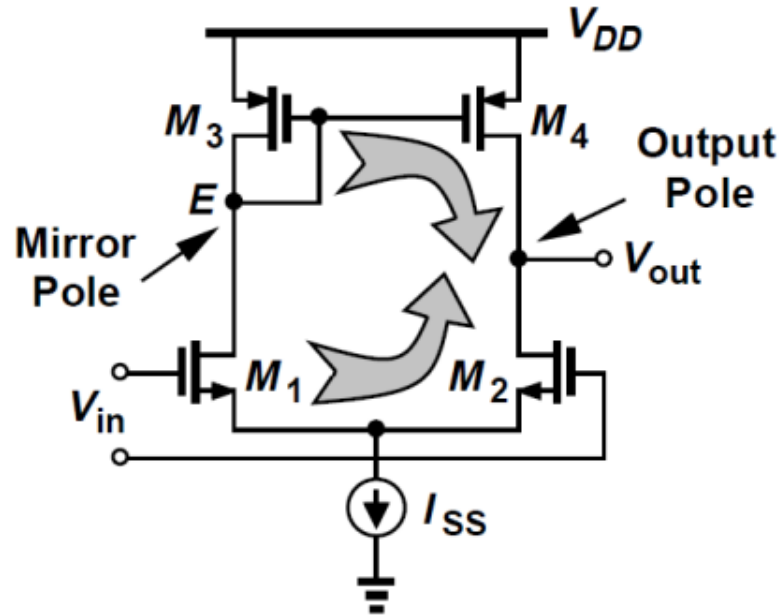

- How many poles does this circuit have?
- The severe trade-off between  $g_m$  and  $C_{GS}$  of PMOS devices results in a pole that impacts the performance of the circuit.
- The pole associated with node  $E$  is called a “mirror pole.”

# Active Load

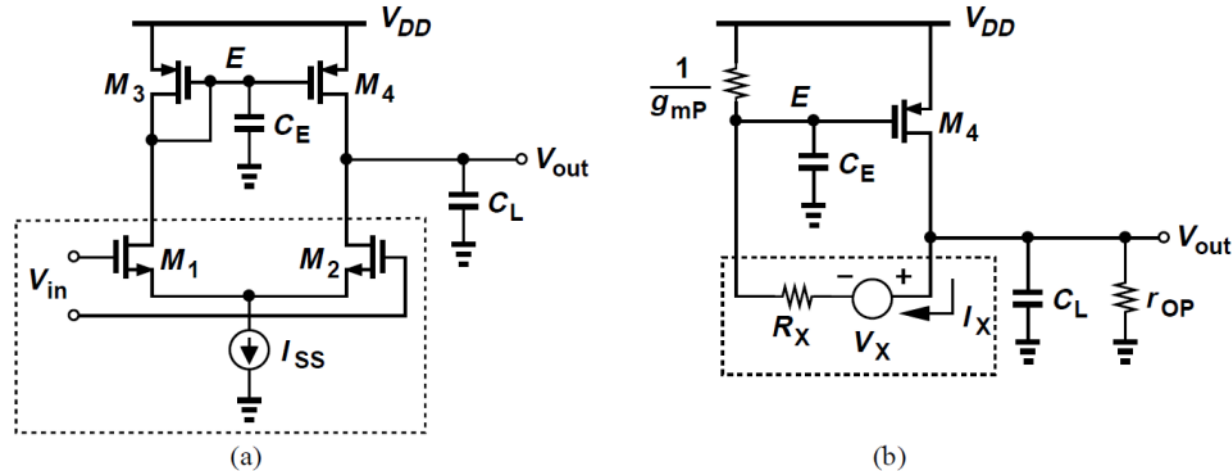


- Replacing  $V_{in}$ ,  $M_1$ , and  $M_2$  by a Thevenin equivalent (Direct calculation method)

$$V_X = g_{mN} r_{ON} V_{in} \quad R_X = 2r_{ON}$$


$$\frac{V_{out}}{V_{in}} = \frac{g_{mN} r_{ON} (2g_{mP} + C_E s) r_{OP}}{2r_{OP} r_{ON} C_E C_L s^2 + [(2r_{ON} + r_{OP}) C_E + r_{OP} (1 + 2g_{mP} r_{ON}) C_L] s + 2g_{mP} (r_{ON} + r_{OP})}$$

$$\omega_{p1} \approx \frac{1}{(r_{ON} \parallel r_{OP}) C_L} \quad \omega_{p2} \approx \frac{g_{mP}}{C_E}$$

# 5T-OTA

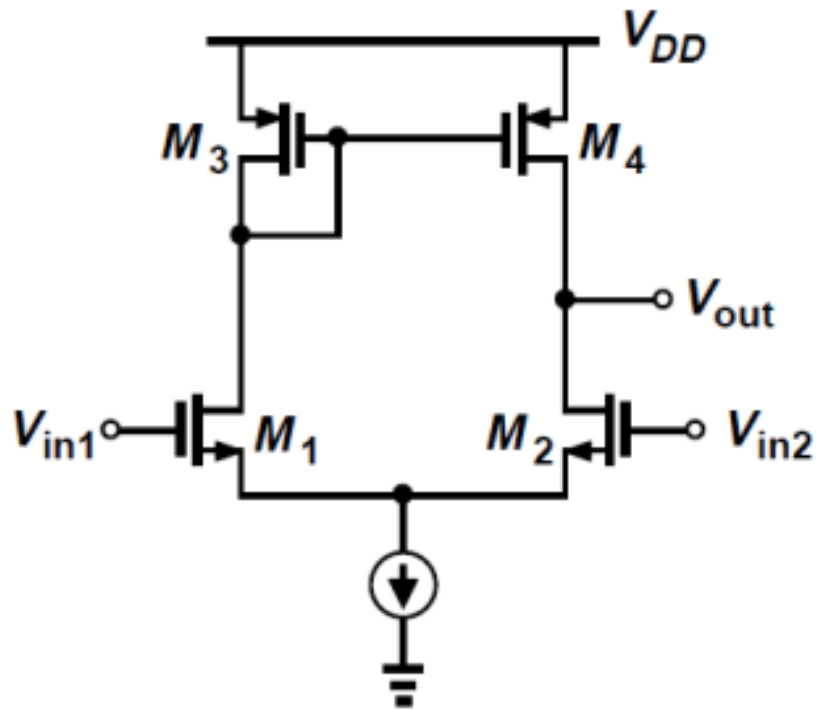

# Example

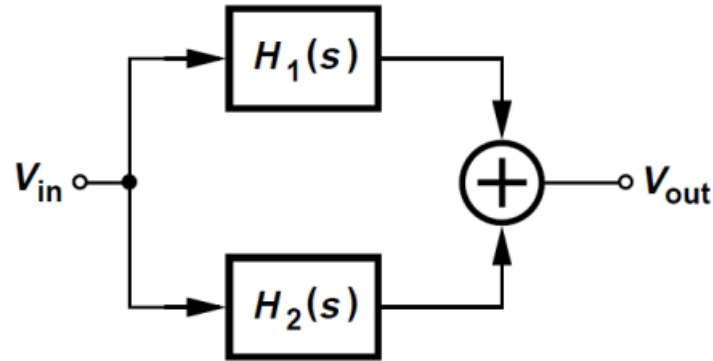

- Can this (the zero) occur if  $H_1(s)$  and  $H_2(s)$  are first-order low-pass circuits?
- $H_1(s) = A_1/(1 + s/\omega_{p1})$  and  $H_2(s) = A_2/(1 + s/\omega_{p2})$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\left(\frac{A_1}{\omega_{p2}} + \frac{A_2}{\omega_{p1}}\right)s + A_1 + A_2}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

- The overall transfer function contains a zero.


# Active Load

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{A_0}{1 + s/\omega_{p1}} \left( \frac{1}{1 + s/\omega_{p2}} + 1 \right) \\ &= \frac{A_0(2 + s/\omega_{p2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}\end{aligned}$$


- A zero with a magnitude of  $2g_{mP}/C_E$  in the left half plane.
- The appearance of this zero can be understood by noting that the circuit consists of:
- a “slow path” (M1,M3 and M4)  $A_0/[(1 + s/\omega_{p1})(1 + s/\omega_{p2})]$  in parallel with
- a “fast path” (M1 and M2) by  $A_0/(1 + s/\omega_{p1})$
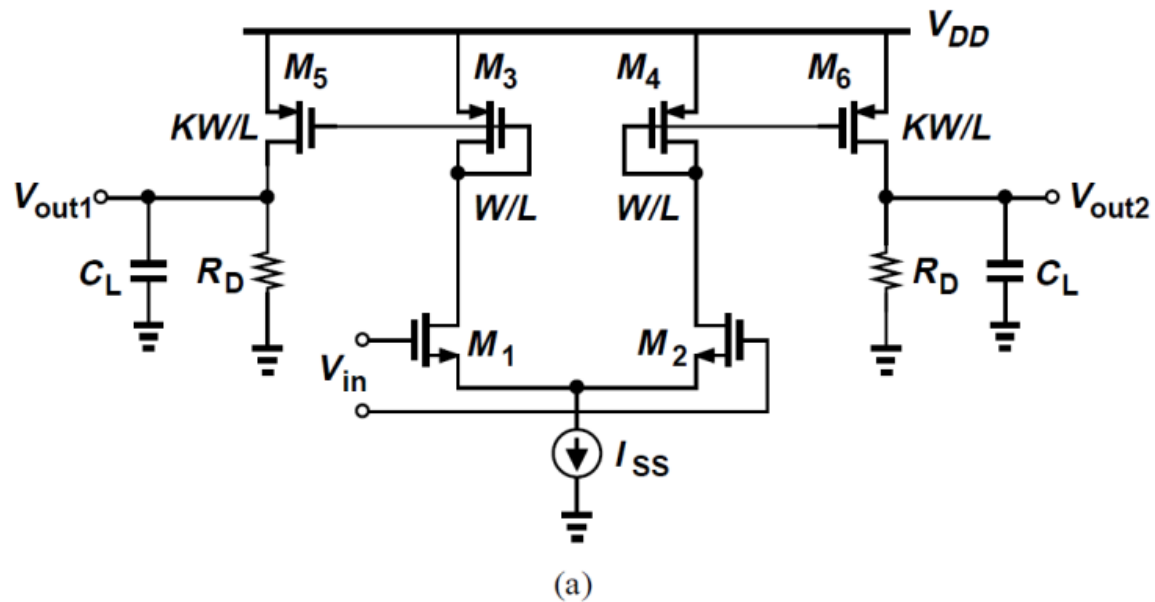
## Example


- Estimate the low-frequency gain and the transfer function of this circuit.




# Example

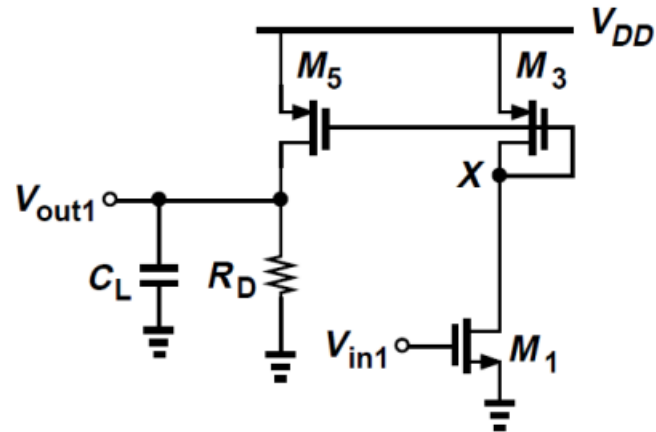

(b)

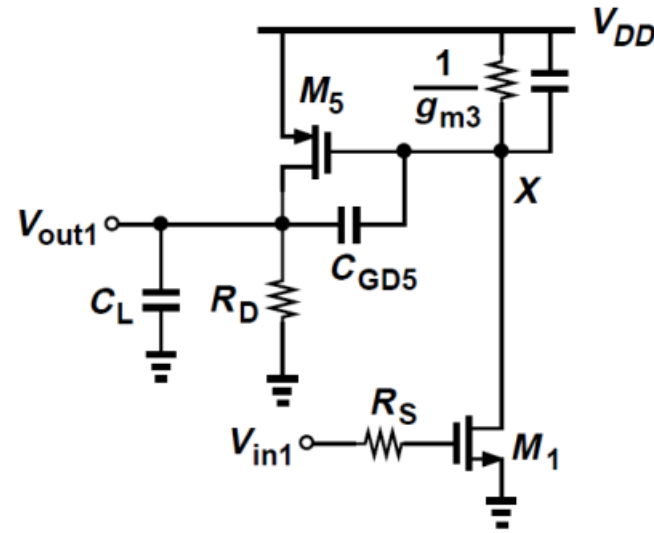


(c)

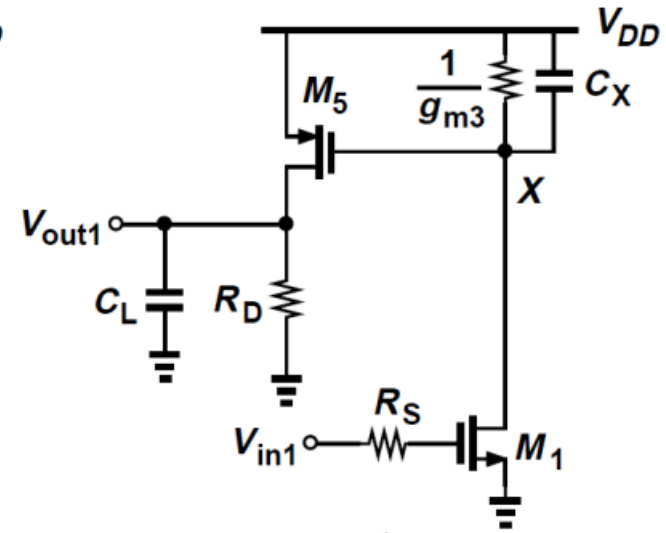

(d)


# Gain-Bandwidth Trade-Offs

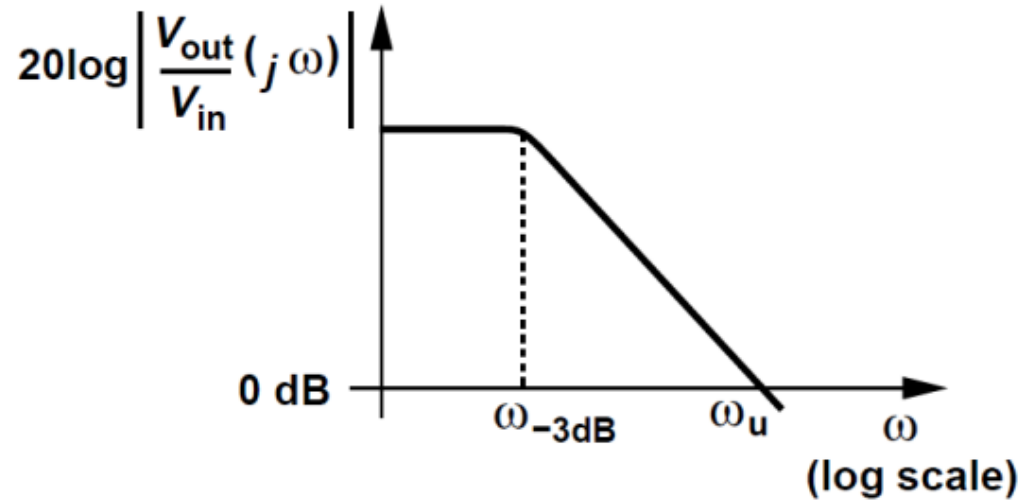

- We wish to maximize both the gain and the bandwidth of amplifiers.
- We are interested in both the 3-dB bandwidth,  $\omega_{-3\text{dB}}$ , and the “unity-gain” bandwidth,  $\omega_u$




# One pole circuit

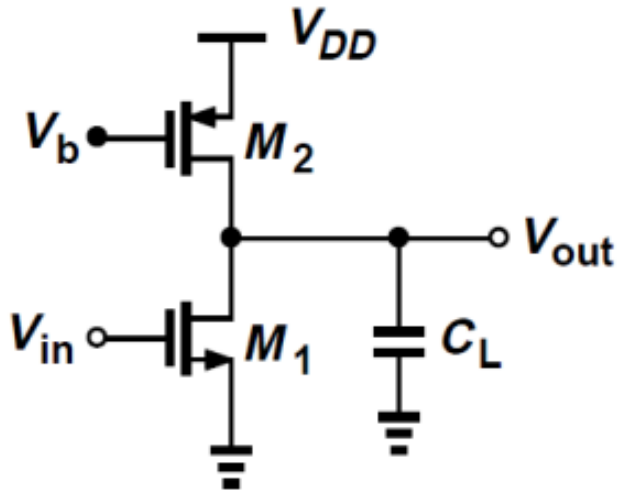

$$\begin{aligned}\text{GBW} &= A_0 \omega_p \\ &= g_{m1}(r_{O1} || r_{O2}) \frac{1}{2\pi(r_{O1} || r_{O2})C_L} \\ &= \frac{g_{m1}}{2\pi C_L}\end{aligned}$$

$$\begin{aligned}\omega_u &= \sqrt{A_0^2 - 1} \omega_p \\ &\approx A_0 \omega_p\end{aligned}$$

# Multi-Pole Circuits

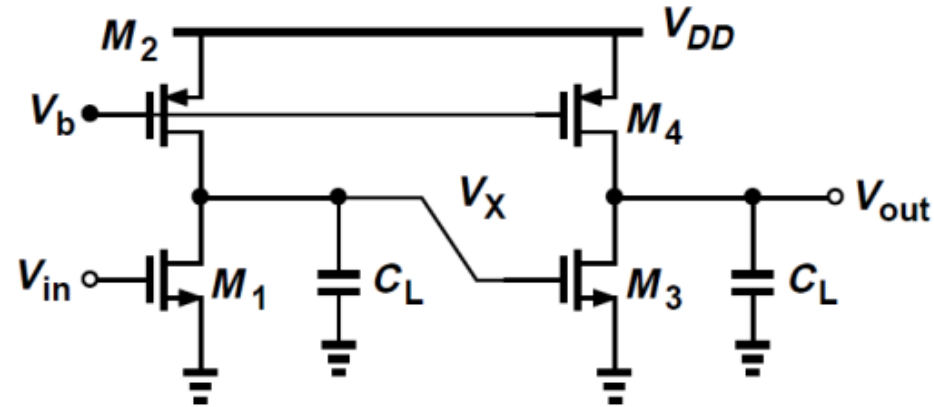

- It is possible to increase the GBW product by cascading two or more gain stages.
- Assume the two stages are identical and neglect other capacitances.

$$\frac{V_{out}}{V_{in}} = \frac{A_0^2}{\left(1 + \frac{s}{\omega_p}\right)^2}$$

$$\omega_{-3dB} = \sqrt{\sqrt{2} - 1} \omega_p \\ \approx 0.64 \omega_p$$

$$\text{GBW} = \sqrt{\sqrt{2} - 1} A_0^2 \omega_p$$

- While raising the GBW product, cascading reduces the bandwidth.