

**EE 332**  
**Homework6**

**Circuits and Devices II**


**Autumn 2022**

**Due: Nov. 18 (11:59pm)**

In this HW assume:  $V_{DD}=1.5V$ ,  $V_{th_{n,p}}=0.3V$ ,  $\mu_n C_{ox} = \frac{500\mu A}{V^2}$ ,  $\mu_n = 2\mu_p$ ,  $\lambda_p = 0.2V^{-1}$ ,  $\lambda_n = 0.1V^{-1}$ , and  $\gamma = 0$  for both NMOS and PMOS devices.

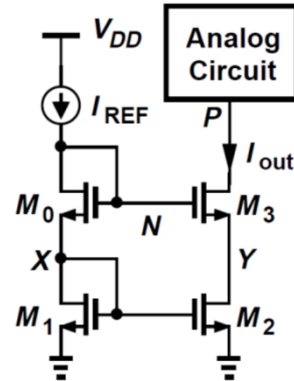
1. For the cascode current-mirror shown below:

- Find minimum output voltage ( $V_p$ ) for the current mirror to work.
- Find output resistance of this current mirror (the resistance looking in from point P).
- If we need to generate a 1mA output current from a 0.1mA reference current, what should be the W/L ratios for  $M_{1,2}$  and  $M_{0,3}$ ? (As in, find  $\frac{(W/L)_2}{(W/L)_1}$  and  $\frac{(W/L)_3}{(W/L)_0}$ )
- To have a minimum working output voltage of 0.5V, what should be the W/L values? Assume  $V_{od}$  is the same for  $M_{0-3}$ .
- To implement  $I_{ref}$  in an easy way we will replace the  $I_{ref}$  ideal current source with a resistor. What should be the value of the resistor to provide 0.1mA reference current?



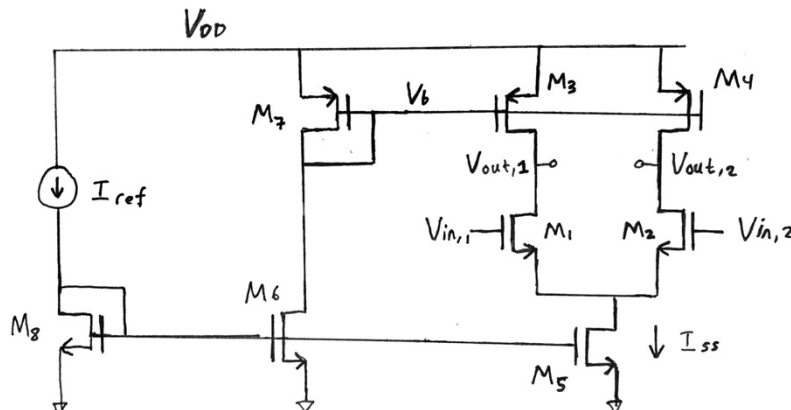2. For the differential amplifier shown below:

- Explain the role of  $M_{3,4}$  and  $M_7$ .
- If  $I_{ref}/I_{ss} = 0.2$ ,  $(W/L)_{7,8} = 50$ , choose W/L of  $M_{3-7}$  to bias the circuit. (You can pick the current flowing through  $M_{6,7}$  as you want). The different W/L ratios do not have to be the same for the different transistors.
- For  $I_{ref} = 125\mu A$  and  $W/L_{1,2} = 125$ , find the peak-to-peak single-ended output swing.
- Find the input CM range (the range of the input voltage DC bias).
- Determine the output nodes' common-mode voltage.



**3.** Consider the 5-Transistor OTA shown here and assume the current in the  $M_5$  current tail will be 1mA.

- Find W/L of  $M_{1,2}$  to have a differential gain of 20.
- Assuming  $V_{od3,4}=0.2V$ , find W/L of  $M_{3,4}$ .
- Find minimum and maximum output swing levels.
- Find the output DC bias and the maximum output swing.
- Find  $M_5$ 's output resistance and the OTA's CMRR.

