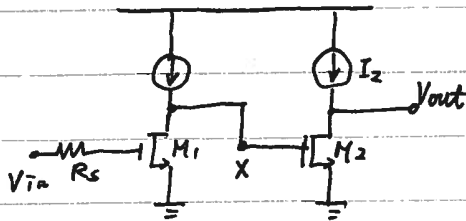


6.7

(a)



There are three poles associated with this circuit.

The first pole @ V_{out}

$$\omega_{p,out} = \frac{1}{r_{o2} \cdot (C_{gd2} + C_{db2})}$$

Note that C_{gd2} should technically be multiplied by $(1 + A) / A$ (Miller cap approximation), where A is the gain, $1 + g_m \cdot r_o$. However, in this case, $(1 + A) / A$ is approximately 1

The pole @ the input


$$\omega_{p,in} = \frac{1}{R_s \cdot [(1 + g_{m1} r_{o1}) C_{gd1} + C_{gs1}]}$$

The pole @ node X


$$\omega_{p,X} = \frac{1}{r_{o1} \cdot [(C_{gd1} + C_{db1} + C_{gs2}) + (1 + g_{m2} r_{o2}) \cdot C_{gd2}]}$$

Please note that the above approximation is based on Miller effect. In order to get more accuracy approximation, transfer function has to be derived.

(b) Small signal model

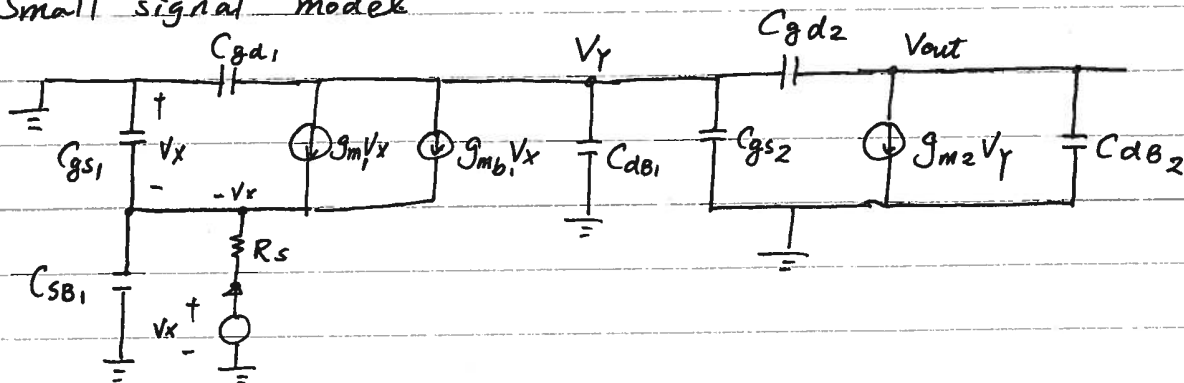

Redraw small signal model

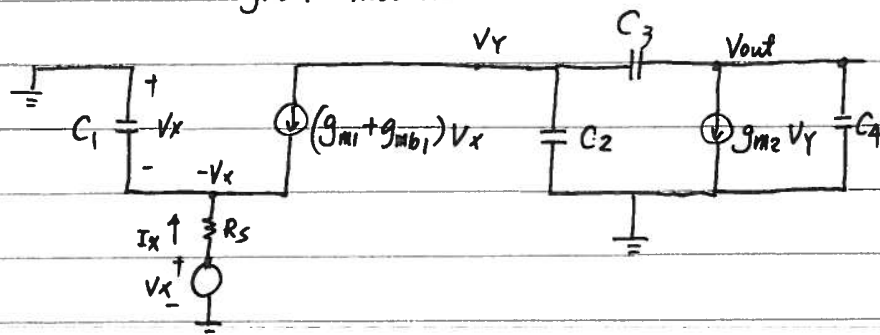

where,

$$C_1 = C_{gs1} + C_{sb1}$$

$$C_2 = C_{gs2} + C_{db1} + C_{ga1}$$

$$C_3 = C_{gd2}$$

$$C_4 = C_{db2}$$

$$\text{KCL @ } V_{out} : S C_3 (V_Y - V_{out}) = g_{m2} V_Y + S C_4 V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_Y} = \frac{-g_{m2} + S C_3}{S (C_3 + C_4)}$$

$$\text{KCL @ } V_Y : (g_{m1} + g_{mb1}) V_X + S C_2 V_Y + S C_3 (V_Y - V_{out}) = 0$$

$$(g_{m1} + g_{mb1}) V_X = -V_Y \left(S C_2 + \frac{S^2 C_3 C_4 + S C_3 g_{m2}}{S (C_3 + C_4)} \right)$$

$$\frac{V_Y}{V_X} = - \frac{g_{m1} + g_{mb1}}{\left[S (C_2 C_3 + C_2 C_4 + C_3 C_4) + C_3 g_{m2} \right] / (C_3 + C_4)}$$

$$\text{KCL @ } V_X : \frac{V_{in} + V_X}{R_S} + S C_1 V_X + (g_{m1} + g_{mb1}) V_X = 0$$

$$\frac{V_X}{V_{in}} = - \frac{1}{S C_1 R_S + (1 + (g_{m1} + g_{mb1}) \cdot R_S)}$$

Thus, there are three poles


$$\omega_{p0} = 0$$

$$\omega_{p1} = \frac{-C_3 g_{m2}}{C_2 C_3 + C_2 C_4 + C_3 C_4} \quad *$$

$$\omega_{p2} = \frac{-(1 + (g_{m1} + g_{mb1}) \cdot R_S)}{C_1 R_S} \quad *$$

Problem 2

(a) Half circuit:

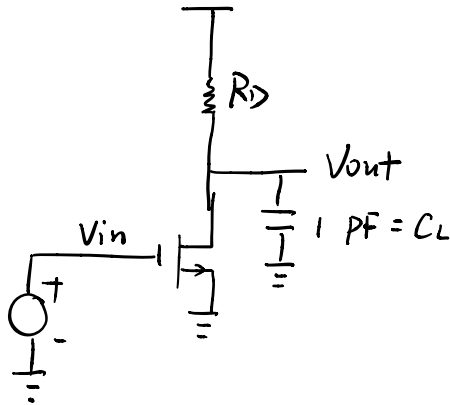

According to Eq 6.30

$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{R_D C_L s + 1} \quad \text{— single pole circuit.}$$

The 3-dB bandwidth is the pole frequency:

$$f_{3-dB} = \frac{1}{2\pi R_D C_L} = 100 \text{ MHz}$$

$$R_D = \frac{1}{2\pi C_L f_{3-dB}} = \frac{1}{2\pi \times 1 \times 10^{-12} \times 100 \times 10^6} = 1.6 \text{ k}\Omega$$

$$(b) \quad A_v = -R_D g_m = -20$$

$$g_m = \frac{20}{1.6 \times 10^3} = \frac{2}{160} = 0.013 \text{ S}$$

$$(c) \quad g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) V_{od}$$



$$\Rightarrow W = \frac{g_m L}{\mu_n C_{ox} V_{od}} = \frac{0.013 \times 65 \times 10^{-9}}{2 \times 10^{-4} \times 0.2} = 21 \mu\text{m.}$$

$$(d) \quad \omega_{in} = \frac{1}{R_S \cdot C_{GS}}$$

$$= \frac{1}{100 \times 1 \times 10^{-15} \times 21} = 4.8 \times 10^{11} \text{ Hz}$$

$$\Rightarrow f_{in} = 7.6 \times 10^{10} \text{ Hz} \\ = 7.6 \times 10^4 \text{ MHz.}$$

(e)

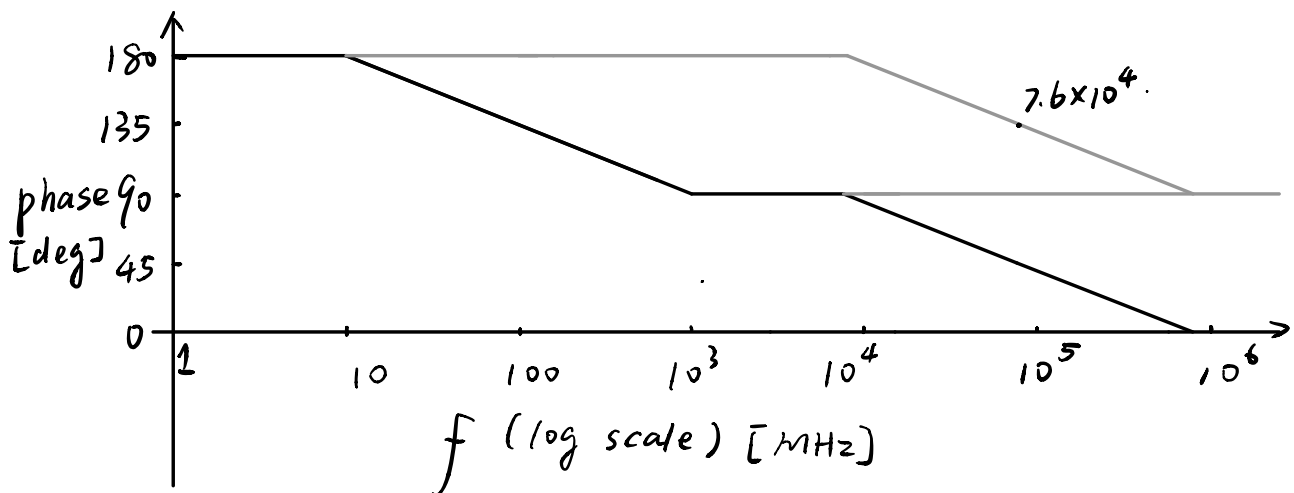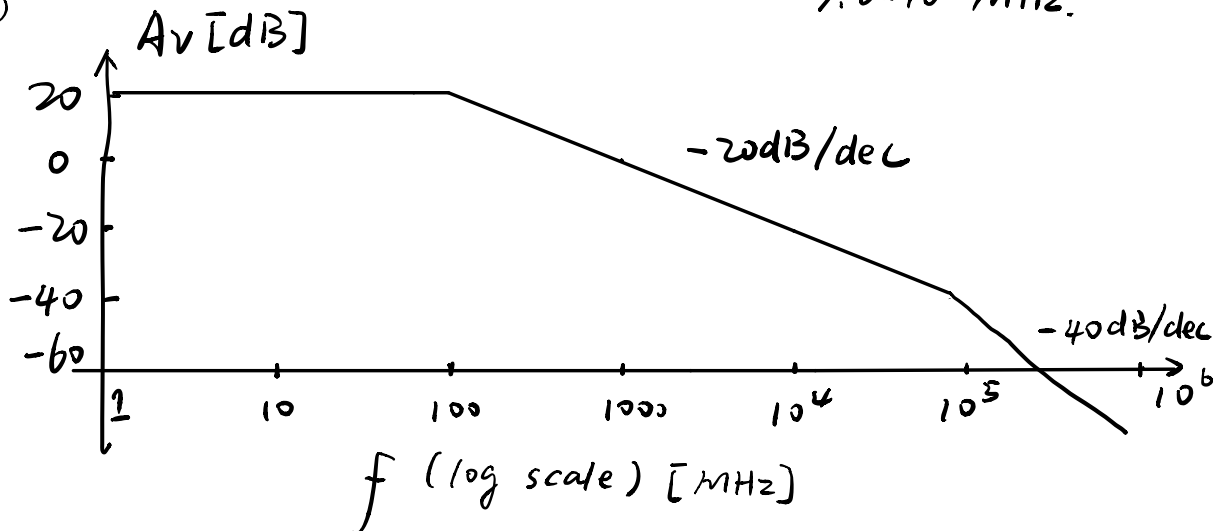

line in black is final
result, gray lines are
Bode plots of each pole