

EE 332: Devices and Circuits II

Course Review & Examples for the Final Exam

Prof. Sajjad Moazeni

smoazeni@uw.edu

Autumn 2022

What did we learn?

- MOS basics and modeling
 - I/V char, parasitics, small-signal, body-effect, channel length mod, ...

- Single-stage Amp (CS, CG, SF + Cascode) *4 types*

- Differential Pair (DM vs. CM, single-ended vs. diff, ...)

- Frequency response (Poles/zeros, Bode Plot, Miller approx., GBW)


- Current Mirrors & Biasing *$1/r_c$*

- Feedback (loop-gain, voltage-voltage fb, ...) & OpAmps *Vs OTA*

- Noise (Definition & Characterization, Thermal Noise, etc.)

PSD,

4WTR

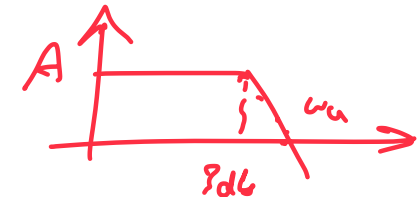


$$A_o \times \omega_{3db} = 1 \times \omega_u$$

Why did we learn?

- Analog circuit is an inevitable part of any electrical system!
 - Remember the world is analog!
- Now you can clearly appreciate the benefit of digital processors
 - You know where the noise is coming from!
- ✱ All the metrics you learned are fundamentals that any IC and embedded system designer should know ...
 - Gain, Noise, Speed, ...
- Techniques and circuit analysis are also essential for any IC designer
- Topics like feedback, noise, ... are useful in Control, Signal processing, communications, etc.

COT Example (CMOS): TI OPAx355



8.2 Functional Block Diagram

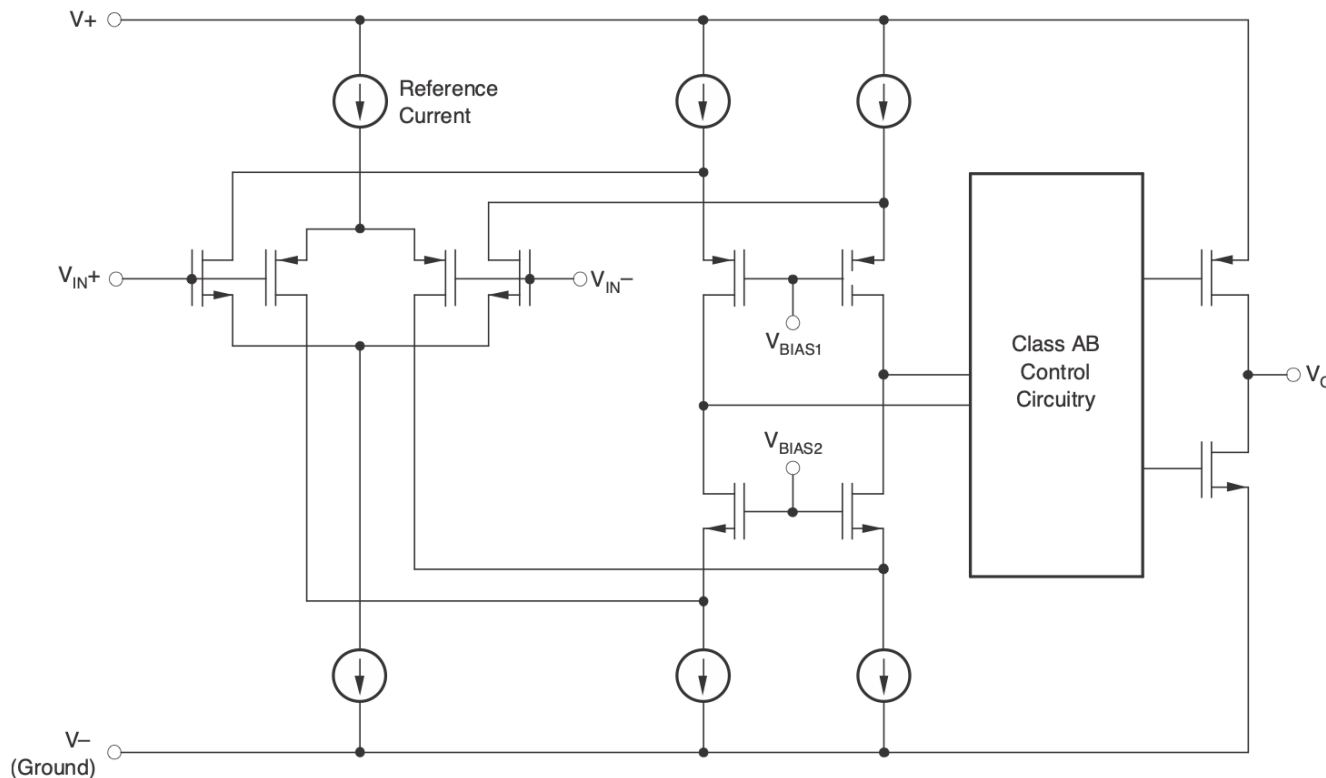

1 Features

- Unity-Gain Bandwidth: 450 MHz
- Wide Bandwidth: 200 MHz GBW
- Low Noise: 5.8 nV/ $\sqrt{\text{Hz}}$
- Excellent Video Performance
 - Differential Gain: 0.02%
 - Differential Phase: 0.05°
 - 0.1-dB Gain Flatness: 75 MHz
- Input Range Includes Ground
- Rail-to-Rail Output (within 100 mV)
- Low Input Bias Current: 3 pA
- Low Shutdown Current: 3.4 μA
- Enable and Disable Time: 100 ns and 30 ns
- Thermal Shutdown
- Single-Supply Operating Range: 2.5 V to 5.5 V
- *MicroSIZE* Packages


Modern Examples: Neuropixel

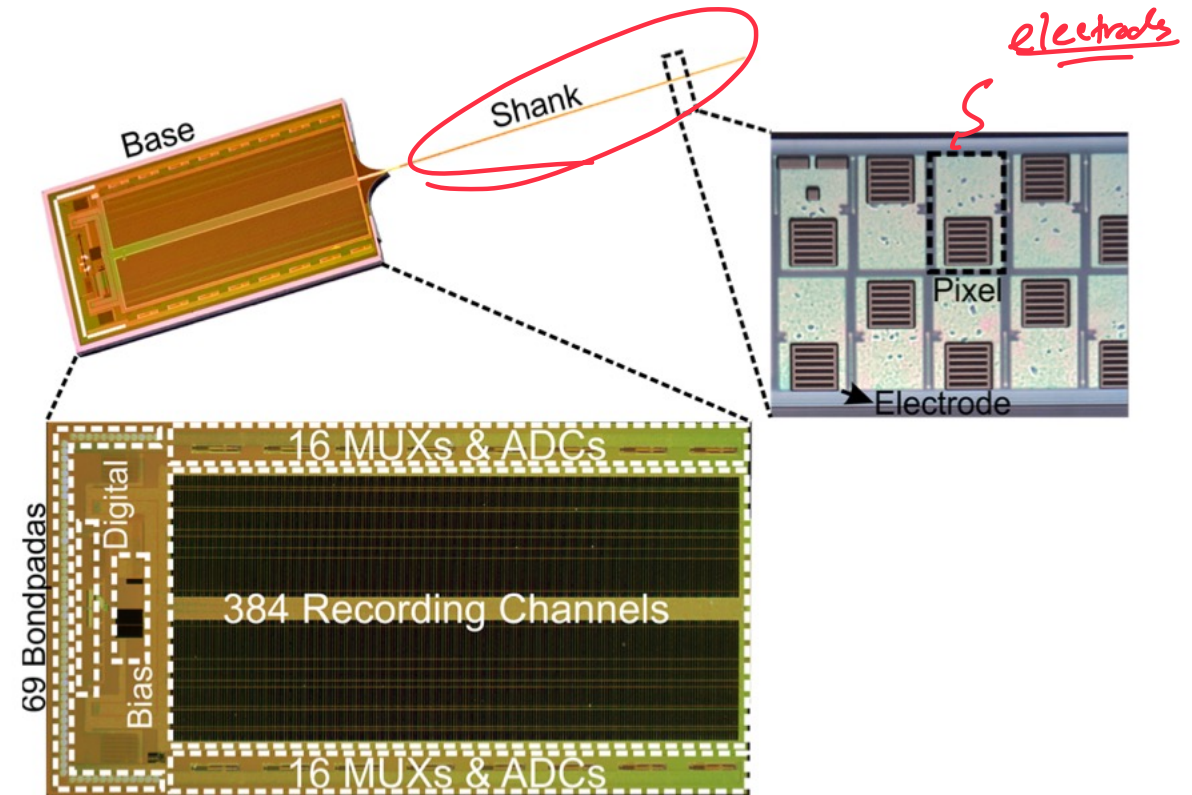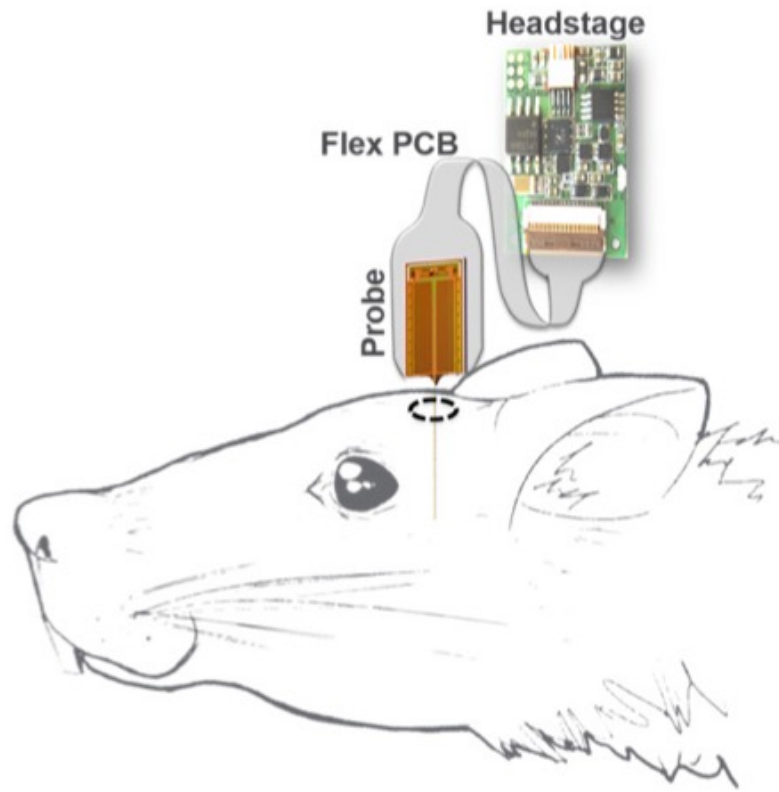

Fully integrated silicon probes for high-density recording of neural activity [Nature 2017]

A Neural Probe with up to 966 Electrodes and up to 384 Configurable Channels in 0.13 μ m SOI CMOS [TBioCAS 2017]


Modern Examples: Neuropixel

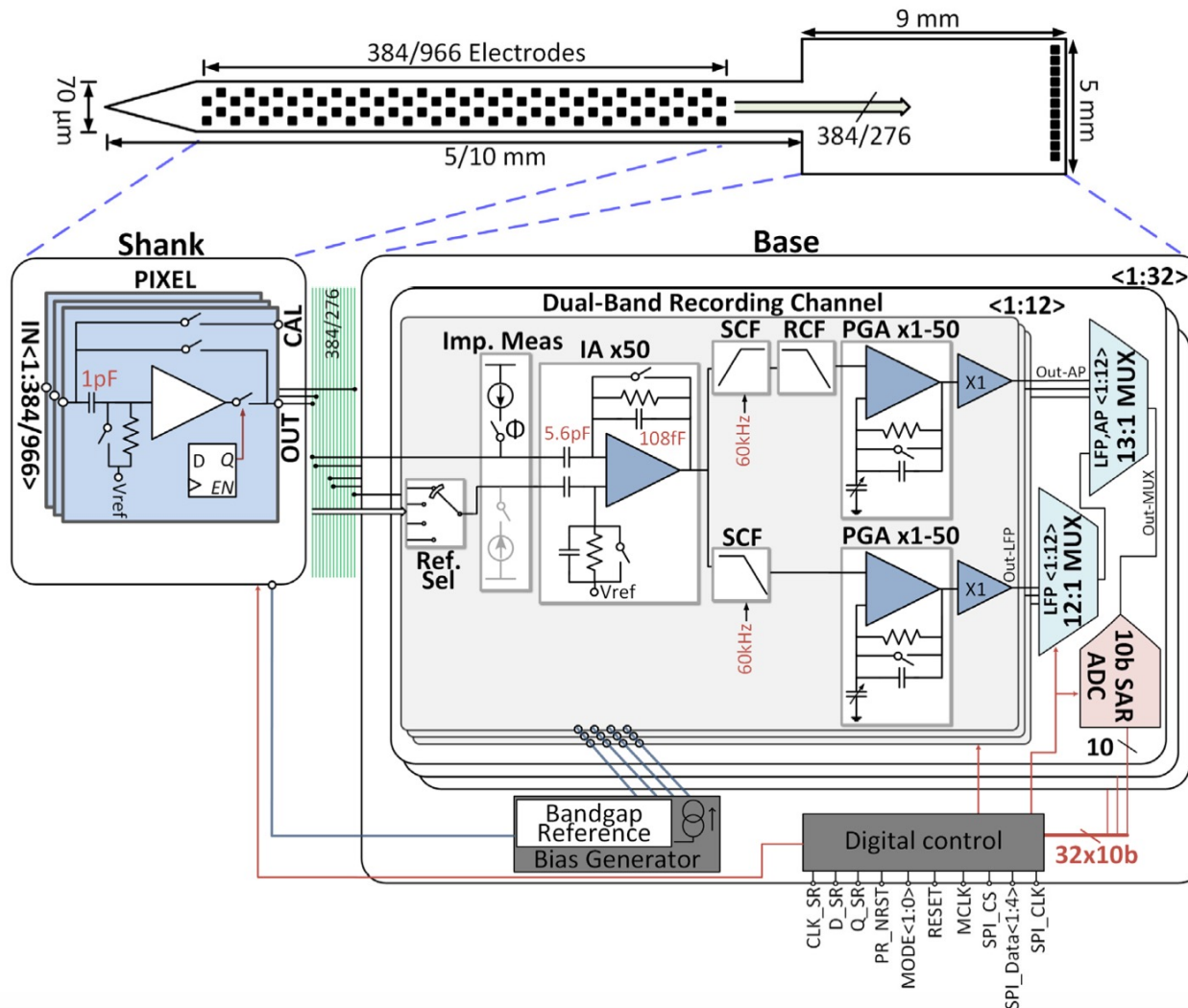

Extended Data Table 1 | Measured operating parameters of the 4 probe types reported (phase 3)

	Option 1	Option 2	Option 3	Option 4
Site Count	384	384	960	966
Channel count	384	384	384	276
Electrode type	Passive	Active	Passive	Active
Shank power (mW)	0	1.31	0	1.31
Base power (mW)		17.5		
Electrode area (μm^2)		144		
Crosstalk (at 1kHz)		< 5%		
Gain		selectable from 50 - 2500		
AP band high-pass corner (kHz)		selectable from 0.3 - 1.0		
AP band low-pass corner (kHz)		10		
LFP band high-pass corner (Hz)		0.5		
LFP band low-pass corner (Hz)		1000		
AP band sampling rate (kHz)		30		
LFP band sampling rate (kHz)		2.5		
AP band noise (μV r.m.s.)	5.7 ± 0.8	6.6 ± 0.8	5.5 ± 0.7	6.6 ± 2.5
LFP band noise (μV r.m.s.)	9.6 ± 5.8	13.0 ± 2.8	8.0 ± 2.5	10.2 ± 1.9

Modern Examples: Neuropixel

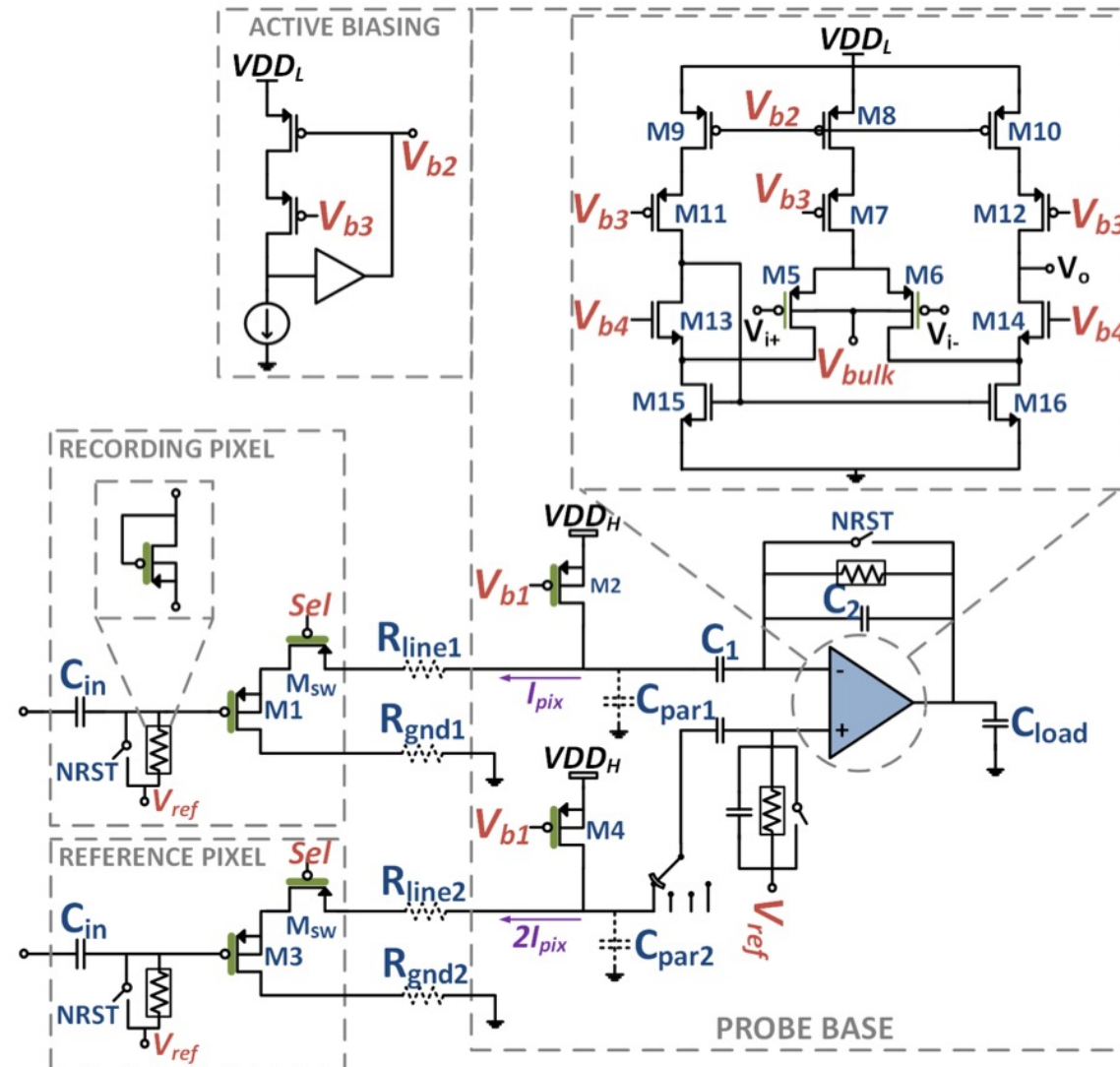

Examples for the Final Exam

$$DM \text{ gain} = \frac{v_x}{v_{in}} \times \frac{v_{out1}}{v_x}$$


Example 1

$$S.E.C.M \text{ gain} = \dots$$


$$\frac{v_x}{v_{in}} = \frac{-g_{m,x}(r_{o1} || r_{o2})}{1 + g_{m,x} 2R_S}$$

- Find/Draw: DM & CM half-circuit & gain, Swing


D.M half-Circuit:

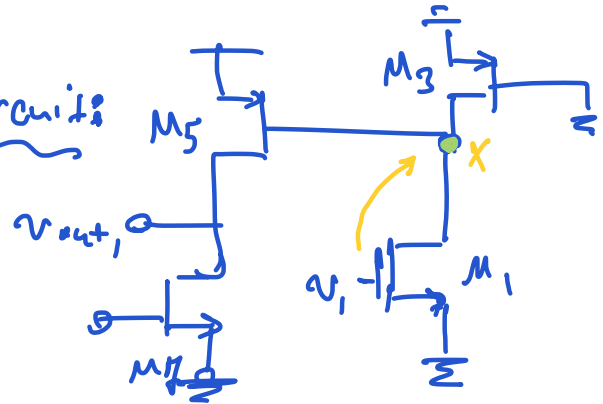

C.M half-circuit:

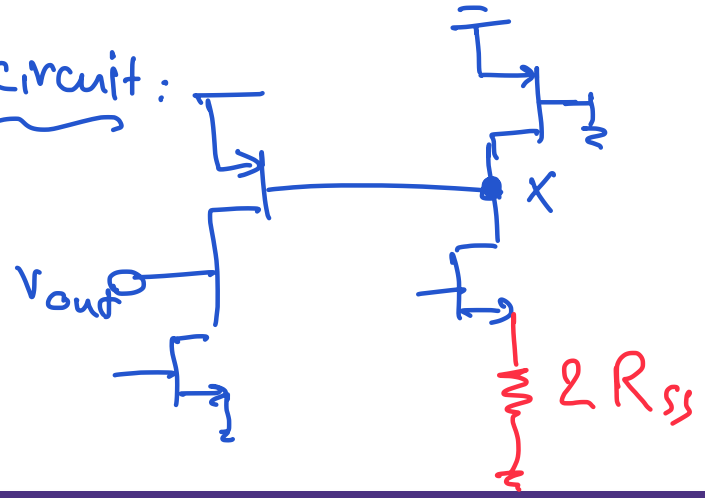

$v_{out M4} \approx V_{DD} - V_{DD5}$
 $v_{out M2} \approx V_{out}$

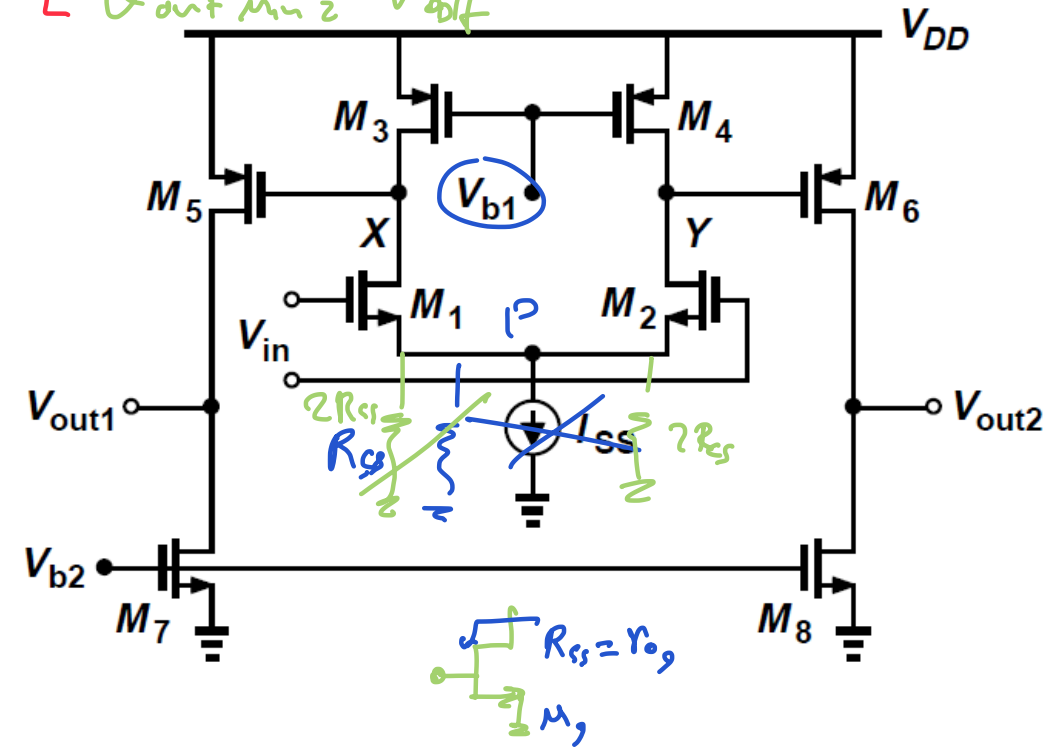

Example 2

* Only assuming a dominant pole


- Find: Poles & Bode plots ($C_L=1\text{pF}$, $C_{gs}=C_{gd}=1\text{fF}/\mu\text{m}$), 3db-bw, unity-gain bw

$$\omega_x = \frac{1}{R_x C_x}, \quad \omega_{out2} = \frac{1}{R_{out} C_{out}}$$

\swarrow $r_{o7} || r_{o1}$ \swarrow $r_{o5} || r_{o7}$

$$C_{out} = C_L + C_{gd7} + C_{gd5}$$


\swarrow $\frac{W}{L} \times L \times \frac{1\text{fF}}{\mu\text{m}}$

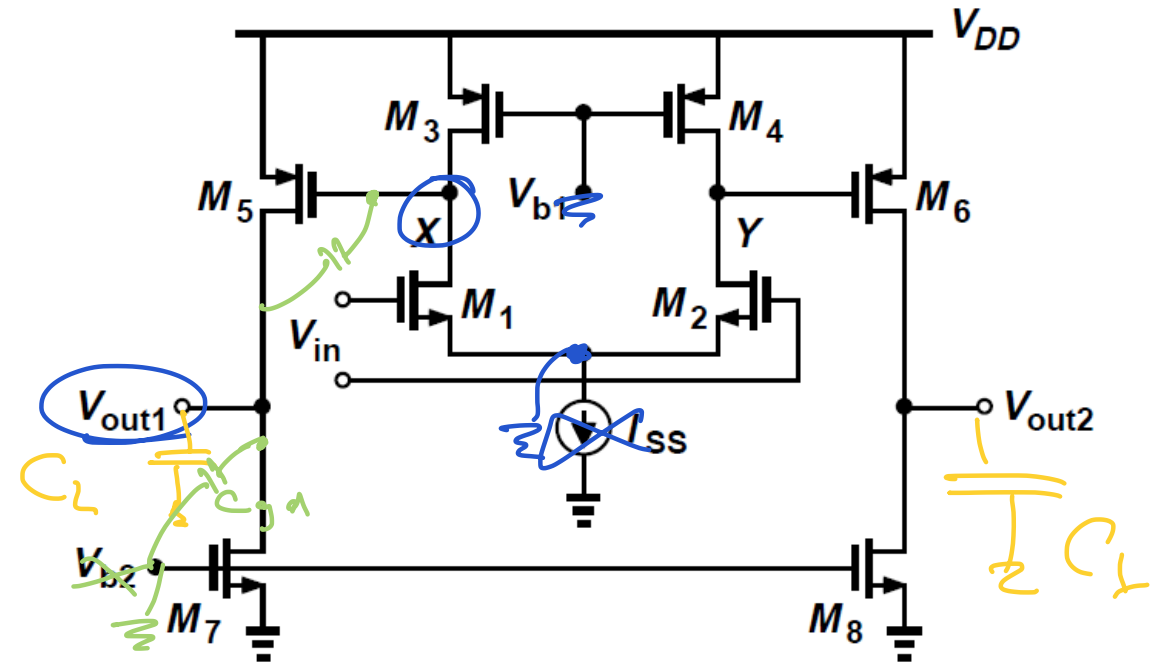

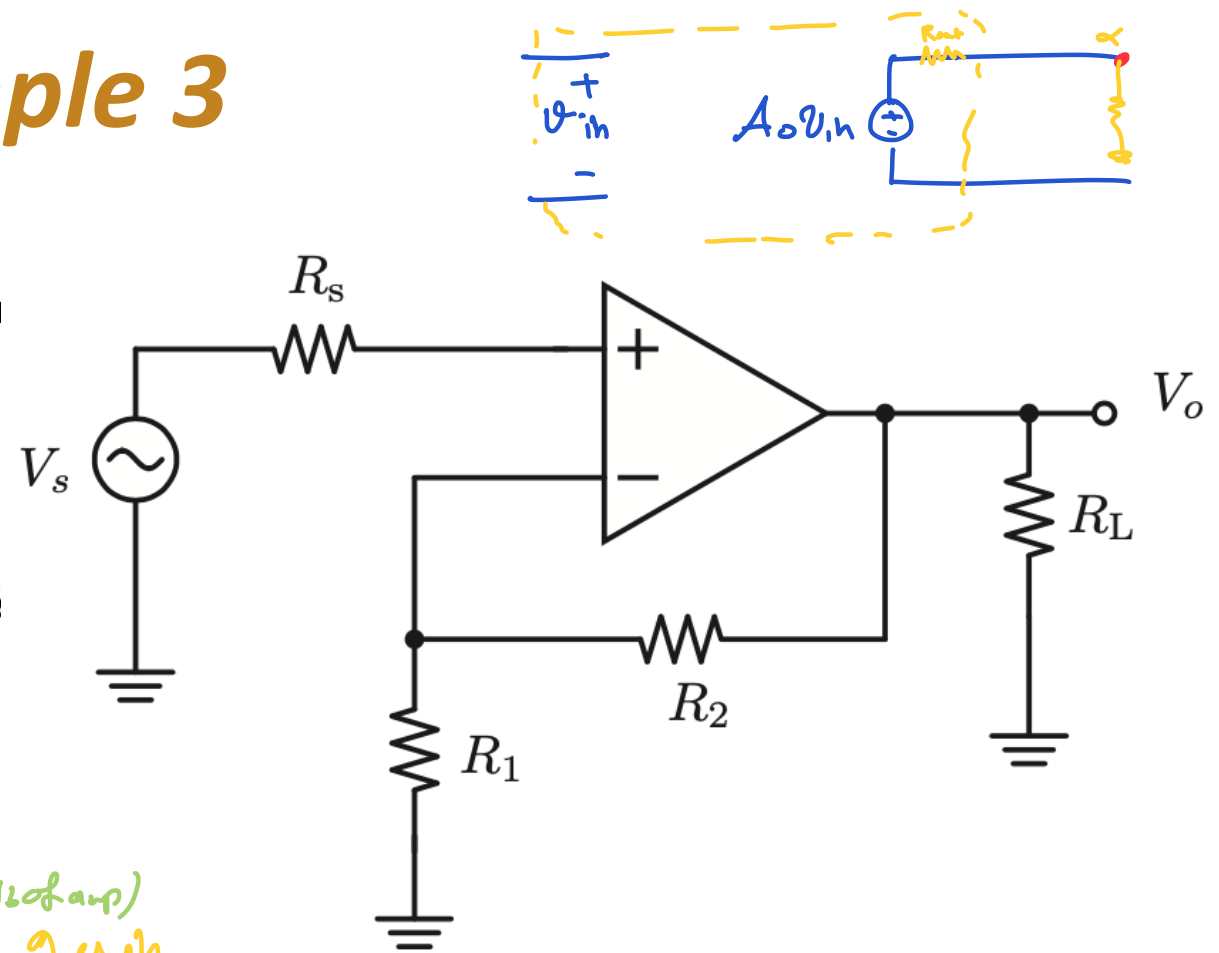Example 3

An op-amp is configured to provide gain (V_O/V_S) of 5V/V a $R_L = 1k\Omega$ load. Model the op-amp with the following parameters:

- $R_{in} = \infty$ (ideal)
- $R_{out} = 0$ (ideal)
- $A_0 = 100$ (not infinite)
- $f_0 = 10MHz$ (not ideal: finite 3dB-bandwidth frequency)



Find:

- R_2/R_1 ?
- Gain error
- Bandwidth & Unity frequency
- If OpAmp's $R_{out} = 100\Omega$ -> find closed loop R_{out} ?

$$\omega_{3dB} = \omega_{3dB \text{ of opAmp}} \times (1 + \beta A)$$

($A \times \omega_{3dB \text{ of opAmp}}$)
gain error

$$R_{out} = 100\Omega / (1 + \beta A)$$

error

$$\frac{A_0}{1 + \beta A_0} \approx \frac{1}{\beta} \left(1 - \frac{1}{\beta A} \right) \rightarrow \text{loop gain}$$

Example 3

Example 4

- Find bias currents, gain, input and output resistance.

$$I_D \rightarrow g_m \& r_o$$

