


EE 332
Homework 2

Circuits and Devices II

Autumn 2022


Due: Oct. 21 (11:59pm)

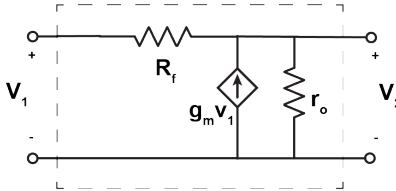1. For the *two-port network* shown below: (All the answers should be in terms of g_m , r_o , R_f , and R_s). In this problem, the two ports at V_1 are the input and the two ports at V_2 are the output.




- Write down KVL/KCL equations to relate V_2 and V_1 and find the gain (V_2/V_1).
- Find the input impedance.
- Assuming that there is a voltage source with source resistance of R_s at the input, find the output impedance.

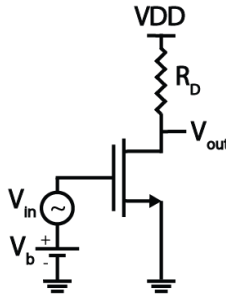2. For the following circuit with an NMOS device assuming $\lambda = 0.1V^{-1}$, $\mu_n C_{ox} = \frac{200\mu A}{V^2}$, $V_{th} = 0.4V$, $\frac{W}{L} = 50$, $L = 65nm$, $R_D = 500\Omega$, $V_{DD} = 1V$, $V_b = 0.8V$:



- Find the bias point and determine the operation region of NMOS device.
- Find small-signal parameters g_m and r_o for the NMOS.
- Draw the small-signal model for the NMOS (you can ignore parasitic capacitances).
- Draw the small-signal model for the full circuit (you can ignore parasitic capacitances).
- Write down KVL/KCL equations to find the small-signal gain ($\frac{V_{out}}{V_{in}}$).
- Find the small-signal gain (questions e and f can be thought of as one question, but make sure to show all your equations and work when finding the small signal gain).

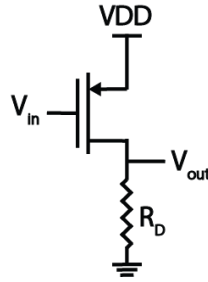3. Assume a basic common-source amplifier with PMOS input (operating in saturation) and R_D as the load.



- Draw the small-signal model, and calculate gain, input, and output impedances. ($\lambda \neq 0$). Do this parametrically (as in, your answer should be a function of variables such as g_m and r_o).
- Suppose $V_{DD} = 1V$, $V_{th} = -0.4V$, V_{IN} (input bias) = $V_{DD}/2$, what's the output voltage swing range ($V_{out,min}$, $V_{out,max}$)?
- With voltages from part (b), if $\lambda = 0.1V^{-1}$, $\mu_p C_{ox} = \frac{50\mu A}{V^2}$, $R_D = 20k\Omega$, what should be W/L to achieve a small signal gain of 20?