 


EE 332
Homework 4

Circuits and Devices II

Autumn 2022
Due: Nov. 4th (11:59pm)

1. For the amplifier circuits below, find gain, input impedance, output impedance, and the voltage swing (peak-to-peak). Assume that all transistors are biased such that: $V_{DD} = 3V$, $V_{th} = 0.5V$, $V_{OD} = 0.2V$, $\gamma = 0$, $\lambda = 0.1V^{-1}$, $I_D = 1mA$, $R_S = 1k\Omega$.



2. Consider a common-source amplifier with $R_S = 100\Omega$ source degeneration (like Fig 3.23a from the book) and $R_D = 10k\Omega$. For NMOS, assume: $V_{DD} = 1V$, $V_{Th} = 0.3V$, $\mu_n C_{ox} = 100\mu A/V^2$, $\lambda = \gamma = 0$.


- Find W/L and V_{in} bias point to achieve $\text{Gain} > 10$ and V_{out} DC bias of $V_{DD}/2$.
- How would the gain change if $\lambda = 0.1V^{-1}$?
- How much is the output voltage swing?
- If we are informed that gate-oxide thickness (t_{ox}) ended up 10% thicker than nominal target value after fabrication, how much this impacts the gain? (*Hint*: what aspect of NMOS device will be influenced by t_{ox} ?)
- Compare your result from part (d) with a simple common-source topology case (w/o source degeneration). Which topology is more robust to process variations?

3. In this problem, we are interested to build an audio amplifier with a gain of 10. Assume the “speaker” that we will drive with our amplifier can be modeled as a load resistor (R_L) of 100Ω . For MOSFETs: $V_{DD} = 1V$, $V_{th} = 0.3V$, $\lambda = 0$, $\mu_n C_{ox} = \frac{100\mu A}{V^2}$

- First, let's design a common-source amplifier with $R_D = 1k\Omega$ and a gain of 10 such that output bias will be at $V_{DD}/2$. Find W/L and V_{GS} bias point.
- Now, include the loading impact of R_L . How much is the gain once you connect the output node to R_L ?
- If you have to adjust your design to achieve the target gain, how do you redesign your amplifier? (Assume the bias point will not be affected by R_L since it can be AC-coupled)
- What's the static power consumption from the supply in this amplifier? (*Hint*: $\text{Supply Power} = V_{DD} * I_D$)

Now, instead of fully redesigning your common-source amplifier from part (a), let's add a source-follower buffer with a gain of 0.5 to drive the load. Assume $R_S = 1k\Omega$, and R_L is AC-coupled.

- First, find the W/L and bias point of the source-follower NMOS (M2) such that V_{out} of that stage will be at $V_{DD}/2$ bias.
- Now modify your CS amplifier such that overall gain will be still 10 and V_{out} is now biased at $V_{DD}/2 + V_{GS2}$. Find new W/L and V_{GS} bias point.
- What's the static power consumption from the supply by both of these stages? Compare the results with part (d).

 

4. *Common-Gate Amp.* Assume $V_{DD}=1V$, $V_{th} = 0.3V$, $\lambda_n = 0.1V^{-1}$, $\gamma = 0$, $\mu_n C_{ox} = \frac{100\mu A}{V^2}$, $I_1 = 0.2mA$, and C_1 will be shorted in small-signal models and open for DC/bias analysis)

- Find R_D , and $V_{GS}-V_{th}$ and W/L of the M1 to achieve a gain of 50 and input impedance of 50Ω (you can assume $\lambda = 0$ for this part).
- If we realize I_1 current-source with a single NMOS device at a fixed gate bias of $0.5V$, draw the new circuit and find W/L of the new NMOS.
- What's the output swing for part (b)?
- How much adding this new NMOS changes the gain?
- Bonus:** if this amplifier is designed for recording neural activities at 300Hz-20kHz frequencies, what should be acceptable C_1 values as a AC-decoupling cap?

