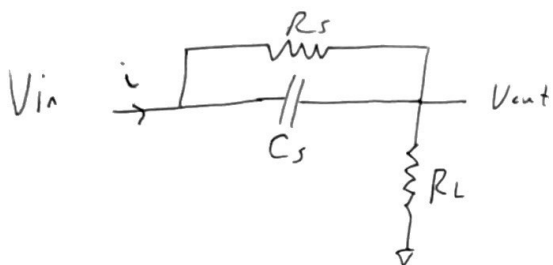


①



①

$$\textcircled{a} \quad \frac{V_{out}(s)}{V_{in}(s)} = i \cdot R_L, \quad i = \frac{V_{in}}{R_s \parallel \frac{1}{C_s s} + R_L}$$

$$= \left(\frac{V_{in}}{\frac{R_s / C_s s}{R_s + \frac{1}{C_s s}} + R_L} \right) \left(\frac{R_s + \frac{1}{C_s s}}{R_s + \frac{1}{C_s s}} \right)$$

$$= \frac{V_{in} \left(R_s + \frac{1}{C_s s} \right)}{R_s / C_s s + R_L \left(R_s + \frac{1}{C_s s} \right)} \cdot \frac{C_s s}{C_s s}$$

$$= \frac{V_{in} (R_s C_s s + 1)}{R_s + R_L (R_s C_s s + 1)}$$

$$= V_{in} \left(\frac{R_s C_s s + 1}{R_s + R_L + R_s R_L C_s s} \right)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_s C_s s + 1}{R_s + R_L + R_s R_L C_s s} \cdot R_L$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(R_s \parallel R_L) C_s s + \frac{R_L}{R_s + R_L}}{(R_s \parallel R_L) C_s s + 1}$$

check

$$\frac{V_{out}(s)}{V_{in}(s)} = \left(\frac{(R_s \parallel R_L) C_s (R_s + R_L)}{R_L} s + 1 \right) \left(\frac{R_L}{R_s + R_L} \right)$$

$$(R_s \parallel R_L) C_s s + 1$$


$$= \frac{\left(\frac{(R_s \cdot R_L) (R_s + R_L)}{(R_s + R_L) R_L} C_s s + 1 \right) \left(\frac{R_L}{R_s + R_L} \right)}{(R_s \parallel R_L) C_s s + 1} =$$

$$\boxed{\frac{R_s C_s s + 1}{(R_s \parallel R_L) C_s s + 1} \cdot \frac{R_L}{R_s + R_L}}$$

Plug in numbers:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{9 \text{ k}\Omega \cdot 1 \text{ nF } s + 1}{(9 \text{ k}\Omega \parallel 1 \text{ k}\Omega) \cdot 1 \text{ nF } s + 1} \cdot \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 9 \text{ k}\Omega}$$
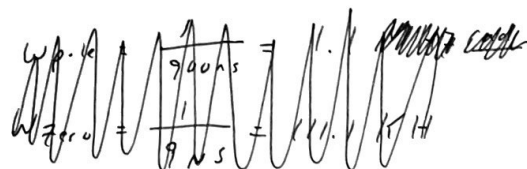
$$= \frac{9 \mu\text{s} \cdot s + 1}{900 \text{ ns} \cdot s + 1} \cdot \frac{1}{10}$$




$$\omega_{pole} = \frac{1}{900 \text{ ns}} = 1.1 \text{ M} \frac{\text{rad}}{\text{sec}}$$

$$\omega_{zero} = \frac{1}{9 \mu\text{s}} = 11.1 \text{ K} \frac{\text{rad}}{\text{sec}}$$

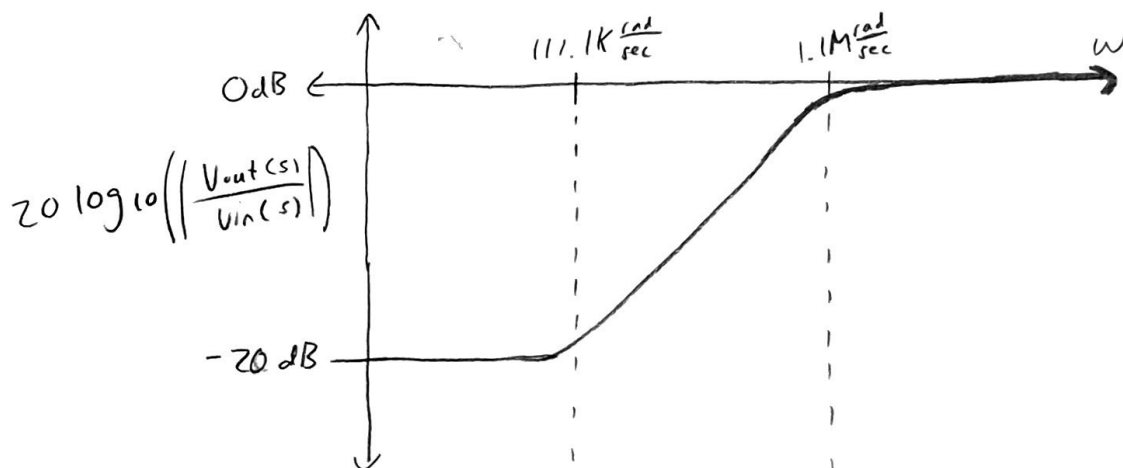(b) Magnitude

At DC, $s=0$, and $\frac{V_{out}}{V_{in}} = \frac{1}{10} = 20 \log_{10}(\frac{1}{10}) = -20 \text{ dB}$

At very high frequency, $\frac{V_{out}}{V_{in}} = 1 \rightarrow = 0 \text{ dB}$



phase

At DC, $\frac{V_{out}}{V_{in}}$ has phase of 0

After the zero "turns on", we will have: $\frac{V_{out}(s)}{V_{in}(s)} = \frac{9 \mu s \cdot s + 1}{1} \cdot \frac{1}{10}$

~~After~~


$= \frac{1}{10} \frac{j+1}{1} \rightarrow \text{phase of } 45^\circ$

After the pole "turns on", we will have:

$\frac{V_{out}(s)}{V_{in}(s)} = \frac{9 \mu s \cdot j\omega}{j+1} \cdot \frac{1}{10} \rightarrow \text{phase of } 45^\circ$

At a high frequency:

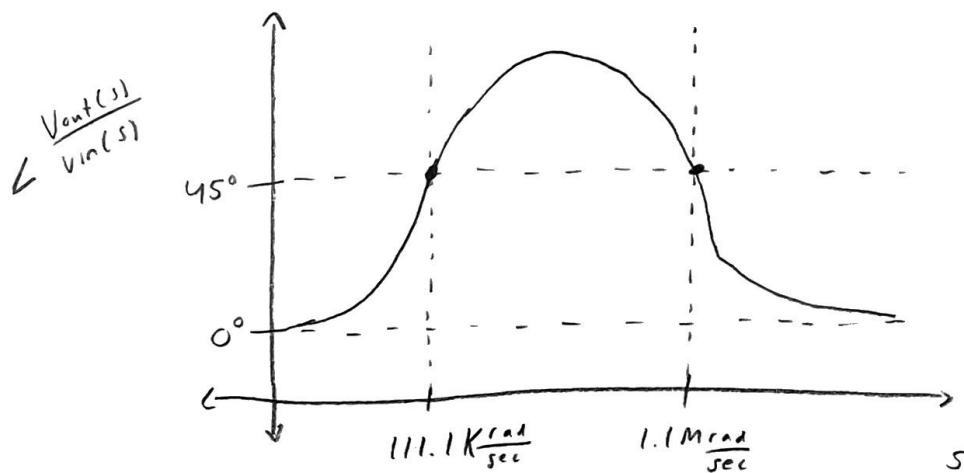$\frac{V_{out}(s)}{V_{in}(s)} = \frac{9 \mu s \cdot j\omega}{500 \mu s \cdot j\omega} \cdot \frac{1}{10} \rightarrow \text{phase of } 0$



③ $V_{in}(t) = 0.2 + \sin(\omega_p t)$

To solve for V_{out} we can consider the DC and non-DC parts of the input ^{separately}

$V_{in,DC}(t) = 0.2$

$V_{out,DC}(t) = 0.2 \cdot \text{DC gain}$
 $= 0.2 \cdot \frac{1}{10}$
 $= 0.02$

~~$V_{in,AC}(t) = \sin(\omega_p t)$~~

$V_{in,AC}(t) = \sin(\omega_p t)$

Solve for $\frac{V_{out}(s)}{V_{in}(s)}$ at $s = \omega_p = 1.1 \text{ M rad/sec}$

$\frac{V_{out}}{V_{in}}(s = 1.1 \text{ M rad/sec}) = \frac{9 \cdot 10^{-6} \cdot 1.1 \cdot 10^6 + 1}{j 900 \cdot 10^{-9} \cdot 1.1 \cdot 10^6 + 1} \cdot \frac{1}{10}$
 $= \frac{10 \cdot j + 1}{j + 1} \cdot \frac{1}{10}$


$\left| \frac{V_{out}}{V_{in}}(\omega_p) \right| = \frac{1}{10} \cdot \frac{\sqrt{10^2 + 1}}{\sqrt{1 + 1}} = \frac{1}{10} \sqrt{\frac{101}{2}} = 0.710$

$\angle \frac{V_{out}}{V_{in}}(\omega_p) = \frac{\tan^{-1}(10)}{\tan^{-1}(1)} = \frac{84.29^\circ}{45^\circ} \rightarrow 39.29^\circ$


$V_{out,AC}(t) = V_{in,AC}(t) \cdot \text{phasor}$

$V_{out,AC}(t) = 0.710 \sin(1.1 \cdot 10^6 \cdot t + 39.29^\circ)$

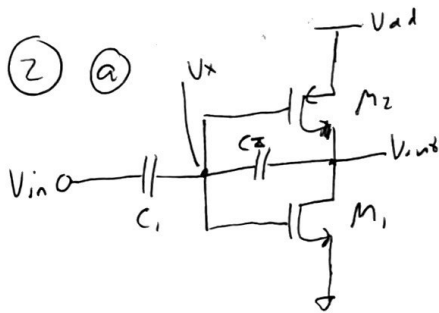
$V_{out}(t) = 0.02 + 0.710 \sin(1.1 \cdot 10^6 t + 39.29^\circ)$



Draw small-signal model

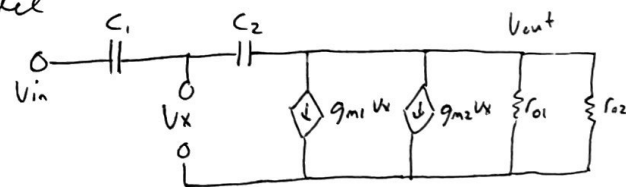

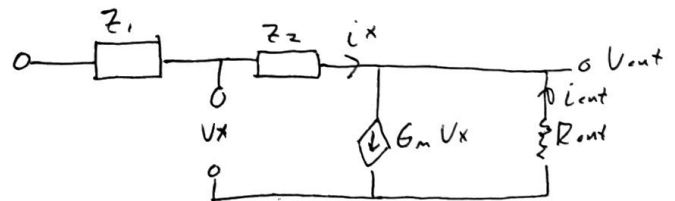I will solve this first by generalizing the capacitors to impedances - can plug in impedance of a capacitor later



$G_m = g_{m1} + g_{m2}$

$R_{out} = r_{o1} \parallel r_{o2}$

$$\frac{V_{in} - V_{out}}{Z_1 + Z_2} - \frac{V_{out}}{R_{out}} = G_m V_x$$

$$V_x = V_{in} - \left(\frac{V_{in} - V_{out}}{Z_1 + Z_2} \right) Z_1$$

$$\frac{V_{in} - V_{out}}{Z_1 + Z_2} - \frac{V_{out}}{R_{out}} = G_m \left[V_{in} - \frac{V_{in} - V_{out}}{Z_1 + Z_2} Z_1 \right]$$

$$\frac{V_{in}}{Z_1 + Z_2} - \frac{V_{out}}{Z_1 + Z_2} - \frac{V_{out}}{R_{out}} = G_m V_{in} - \frac{G_m Z_1 V_{in}}{Z_1 + Z_2} + \frac{G_m V_{out} Z_1}{Z_1 + Z_2}$$

$$\left[V_{in} \left[\frac{1 + G_m Z_1}{Z_1 + Z_2} - G_m \right] = V_{out} \left[\frac{1}{R_{out}} + \frac{1 + G_m Z_1}{Z_1 + Z_2} \right] \right] \rightarrow \times \frac{Z_1 + Z_2}{Z_1 + Z_2}$$

$$V_{in} [1 + G_m Z_1 - G_m Z_1 - G_m Z_2] = V_{out} \left[\frac{Z_1 + Z_2}{R_{out}} + 1 + G_m Z_1 \right]$$

$$V_{in} [1 - G_m Z_2] = V_{out} \left[\frac{Z_1 + Z_2}{R_{out}} + 1 + G_m Z_1 \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{1 - G_m Z_2}{\frac{Z_1 + Z_2}{R_{out}} + 1 + G_m Z_1} \rightarrow \text{now let } Z_1 = \frac{1}{C_1 s}, Z_2 = \frac{1}{C_2 s}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1 - \frac{G_m}{C_2 s}}{\frac{\frac{1}{C_1 s} + \frac{1}{C_2 s}}{R_{out}} + 1 + \frac{G_m}{C_1 s}} = \frac{s - \frac{G_m}{C_2}}{s + \left(\frac{1}{R_{out} C_1} + \frac{1}{R_{out} C_2} + \frac{G_m}{C_1} \right)} \cdot \frac{R_{out} C_1 C_2}{R_{out} C_1 C_2}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{R_{out} C_1 (C_2 s - G_m)}{R_{out} C_1 C_2 s + C_2 + C_1 + G_m R_{out} C_2}$$

Alternatively we can do:

$$\frac{V_{out}}{V_{in}}(s) = \frac{s - \frac{G_m}{C_2}}{s + \left(\frac{1}{R_{out} C_1} + \frac{1}{R_{out} C_2} + \frac{G_m}{C_1} \right)}$$

So we have:

$$\text{Zero: } \omega_z = \frac{G_m}{C_2}$$

$$\text{pole: } \omega_p = \frac{1}{R_{out} C_1} + \frac{1}{R_{out} C_2} + \frac{G_m}{C_1}$$

Let's assume $\omega_z \ll \omega_p$

~~V_{out}(s)~~
~~V_{in}(s)~~

To make the Bode plot
Let's find DC conditions and high freq conditions:
 $\frac{V_{out}}{V_{in}}(0) = \frac{+G_m R_{out} C_1}{C_2 + C_1 + G_m R_{out} C_2}$
 $\frac{V_{out}}{V_{in}}(s = \infty) = 1$
The presence of a negative zero can be a little confusing. What this means is that the zero will already be "on" at DC so the gain will already be rising 20 dB/decade

To make the Bode Plot

(5)

Let's assume that $\omega_s < \omega_p$

Let's find key points & values of $\frac{V_{out}}{V_{in}}(s)$


will assume this $k_v < 1$

$s = 0$
 $\frac{V_{out}}{V_{in}}(s=0) = \frac{-G_m R_{int} C_1}{C_2 + C_1 + G_m R_{int} C_2} \rightarrow \text{mag} = \left| \frac{+G_m R_{int} C_1}{C_2 + C_1 + G_m R_{int} C_2} \right|, \text{phase} = +180^\circ$

$s = \infty$
 $\frac{V_{out}}{V_{in}}(s=\infty) = 1 \rightarrow \text{mag} = 1, \text{phase} = 0$

Mag


$\left| \frac{V_{out}(s)}{V_{in}} \right|$

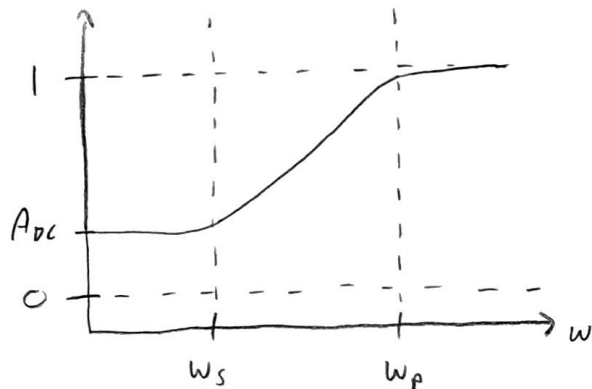


$A_{dc} = \left| \frac{G_m R_{int} C_1}{C_2 + C_1 + G_m R_{int} C_2} \right|$

Phase

$\angle \frac{V_{out}(s)}{V_{in}(s)}$

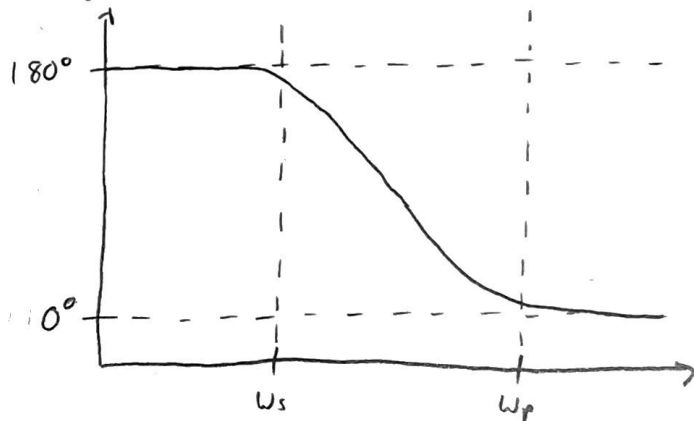

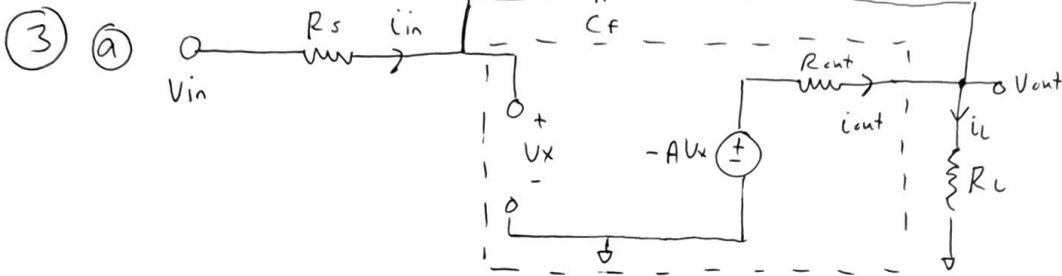

For solving this ~~with~~ I will abstract C_f to a generalised impedance Z_f and will convert to $\frac{1}{C_f s}$ at the end

$$i_{in} + i_{out} = i_L \quad i_{in} = \frac{V_{in} - V_{out}}{R_s + Z_f}, \quad i_L = \frac{V_{out}}{R_L}, \quad i_{out} = \frac{-AV_x - V_{out}}{R_{out}} \rightarrow V_x = V_{in} - \left(\frac{V_{in} - V_{out}}{R_s + Z_f} \right) R_s$$

$$i_{out} = \frac{-A \left(V_{in} - \frac{V_{in} - V_{out}}{R_s + Z_f} R_s \right) - V_{out}}{R_{out}}$$

$$\downarrow$$

$$\frac{V_{in} - V_{out}}{R_s + Z_f} + \frac{-A \left(V_{in} - \frac{V_{in} - V_{out}}{R_s + Z_f} R_s \right) - V_{out}}{R_{out}} = \frac{V_{out}}{R_L}$$

$$\left[\frac{V_{in} - V_{out}}{R_s + Z_f} - \frac{AV_{in}}{R_{out}} + \frac{A(V_{in} - V_{out})R_s}{R_{out}(R_s + Z_f)} - \frac{V_{out}}{R_{out}} \right] (R_s + Z_f) R_{out} = \frac{V_{out}}{R_L} (R_s + Z_f) R_{out}$$

$$R_{out} V_{in} - R_{out} V_{out} - AV_{in}(R_s + Z_f) + AV_{in}R_s - AV_{out}R_s - V_{out}(R_s + Z_f) = V_{out} X, \quad X = \frac{(R_s + Z_f) R_{out}}{R_L}$$

$$\cancel{R_{out} V_{in}} - \cancel{AV_{in}R_s} V_{in} (R_{out} - AZ_f) = V_{out} [X + (R_s + Z_f) + AR_s + R_{out}]$$

$$\frac{V_{out}}{V_{in}} = \frac{R_{out} - AZ_f}{X + (R_s + Z_f) + AR_s + R_{out}} \rightarrow \text{now substitute } Z_f = \frac{1}{C_f s}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_{out} - \frac{A}{C_f s}}{X + \cancel{R_s} + AR_s + R_{out} + \left(R_s + \frac{1}{C_f s} \right)} \cdot \frac{C_f s}{C_f s}$$

$$\frac{V_{out}(s)}{V_{in}} = \frac{R_{out} C_f s - A}{C_f s (X + R_s(A+1) + R_{out}) + 1}, \quad X = \frac{R_s + Z_f}{R_L} R_{out}$$

Continued on next page

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_{out} C_f s - A}{C_f s \left(\frac{R_s + \frac{1}{C_f s}}{R_L} R_{out} + R_s(A+1) + R_{out} \right) + 1}$$

$$= \frac{R_{out} C_f s - A}{C_f s \left(\frac{R_s}{R_L} R_{out} + R_s(A+1) + R_{out} \right) + 1 + \frac{R_{out}}{R_L}}$$


$$= \frac{R_{out} C_f s - A}{C_f s \left[R_s \left(\frac{R_{out}}{R_L} + A + 1 \right) + R_{out} \right] + 1 + \frac{R_{out}}{R_L}}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_L (R_{out} C_f s - A)}{C_f s [R_s (R_{out} + R_L A + R_L) + R_{out} R_L] + R_L + R_{out}}$$

$$= \left(s - \frac{A}{R_{out} C_f} \right) (R_L) (R_{out} C_f)$$

$$\left(s + \frac{R_L + R_{out}}{C_f [R_s (R_{out} + R_L A + R_L) + R_{out} + R_L]} \right) (C_f [R_s (R_{out} + R_L A + R_L) + R_{out} + R_L])$$

6

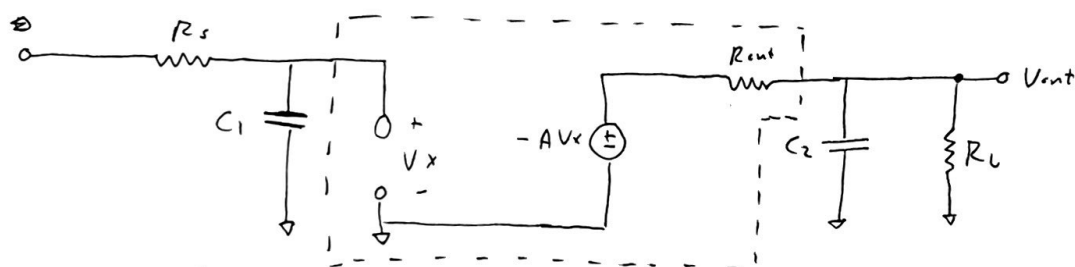

$$C_1 = (1+B) C_f, \quad C_2 = \frac{1+B}{B} C_f$$

B = open loop gain

$$B = \frac{A \cdot R_L}{R_{out} + R_L}$$


③ $V_x = \frac{V_{in}}{R_s + \frac{1}{C_1 s}} \cdot \frac{1}{C_1 s}$ (voltage divider)

⑦

$$\frac{V_x}{V_{in}} = \frac{1}{R_s C_1 s + 1}$$

$$V_{out} = \frac{-A V_x}{R_{out} + R_L \parallel \frac{1}{C_2 s}} \cdot (R_L \parallel \frac{1}{C_2 s}) \text{ (voltage divider)}$$
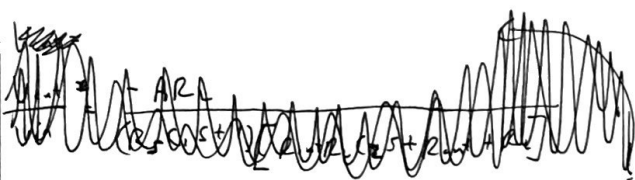
$$\cancel{V_{out}} R_L \parallel \frac{1}{C_2 s} = \frac{R_L \frac{1}{C_2 s}}{R_L + \frac{1}{C_2 s}} \cdot \frac{C_2 s}{C_2 s} = \frac{R_L}{R_L C_2 s + 1}$$



$$V_{out} = \frac{-A V_x}{R_{out} + \frac{R_L}{R_L C_2 s + 1}} \cdot \frac{R_L}{R_L C_2 s + 1}$$

$$\frac{V_{out}}{V_x} = \frac{-A R_L}{R_{out} R_L C_2 s + R_{out} + R_L}$$

$$\boxed{\frac{V_{out}}{V_{in}}(s) = \frac{-A R_L}{(R_s C_1 s + 1)(R_{out} R_L C_2 s + R_{out} + R_L)}}$$

We can also write:

$$\frac{V_{out}}{V_{in}}(s) = \frac{-A R_L}{(R_s C_1 s + 1)(R_{out} R_L C_2 s + R_{out} + R_L)} \cdot \left(\frac{1}{R_{out} R_L C_2} \right) \left(\frac{1}{C_1 R_s} \right)$$

$$\boxed{\frac{V_{out}}{V_{in}}(s) = \left(\frac{-A R_L}{\left(s + \frac{1}{R_s C_1}\right) \left(s + \frac{R_{out} + R_L}{R_{out} R_L C_2}\right)} \right) \left(\frac{1}{R_{out} R_L C_2} \cdot \frac{1}{C_1 R_s} \right)}$$

where $C_1 = (1+B)C_f$, $C_2 = \left(\frac{1+B}{B}\right)C_f$, $B = \frac{A \cdot R_L}{R_{out} + R_L}$

② True Transfer Function

~~One pole and one zero~~

$$\omega_z = \frac{A}{R_{out} C_f}, \quad \omega_p = \frac{R_L + R_{out}}{C_f [R_s (R_{out} + R_L A + R_L) + R_{out} + R_L]}$$

Miller Approx. Transfer function

Two poles

$$\omega_{p1} = \frac{1}{R_s C_1}, \quad \omega_{p2} = \frac{R_{out} + R_L}{R_{out} R_L C_2} = \frac{R_{out} + R_L}{R_{out} R_L \left[1 + \frac{A \cdot R_L}{R_{out} + R_L} \right] C_f} = \frac{R_{out} + R_L}{R_{out} R_L \left[\frac{R_{out} + R_L + A \cdot R_L}{A \cdot R_L} \right] C_f}$$

$$\omega_{p2} = \frac{R_{out} + R_L}{(R_{out} \cdot R_L) \left(\frac{R_{out} + R_L + 1}{A \cdot R_L} \right) C_f}$$

The true transfer function shows one zero and one pole whereas the Miller approximations leads us to two poles.