


EE 332: Devices and Circuits II

Lecture 3: Single-stage Amplifiers (Part 2)

Prof. Sajjad Moazeni




smoazeni@uw.edu

Autumn 2022

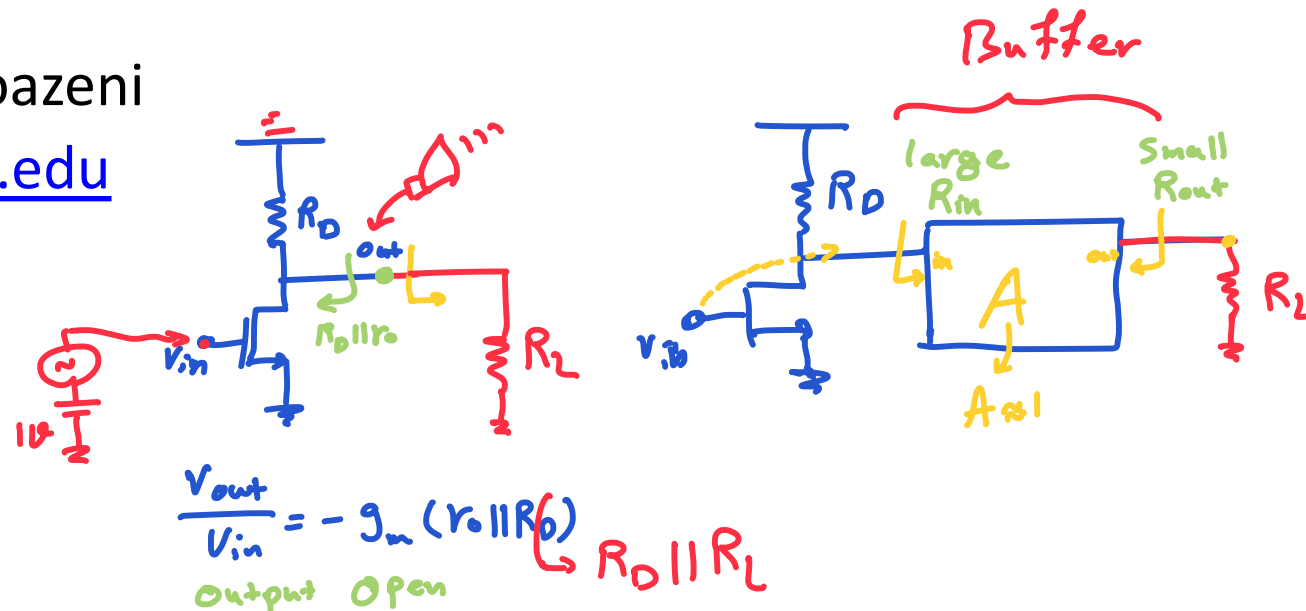


Source Follower

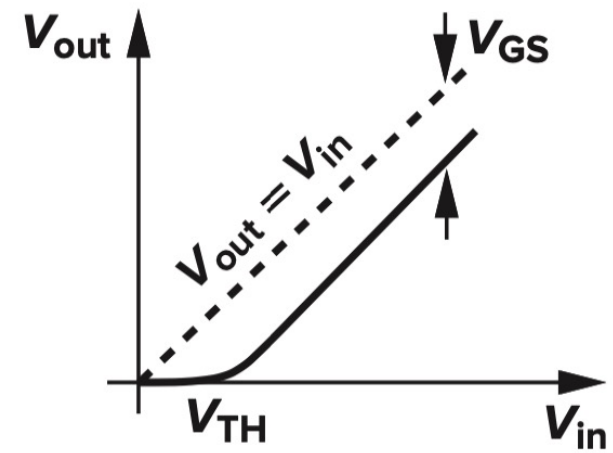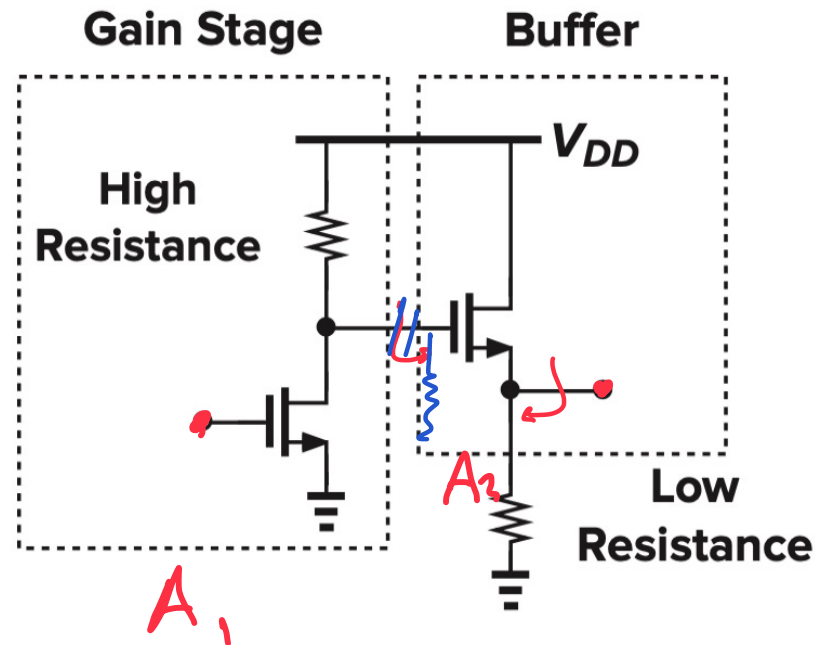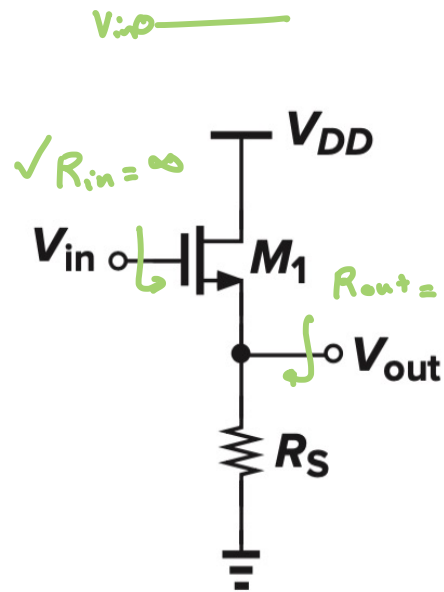- Source follower (also called “common-drain” stage) senses the input at the gate and drives load at the source
- It presents a high input impedance, allowing source potential to “follow” the gate voltage
- Acts as a voltage buffer



Source Follower

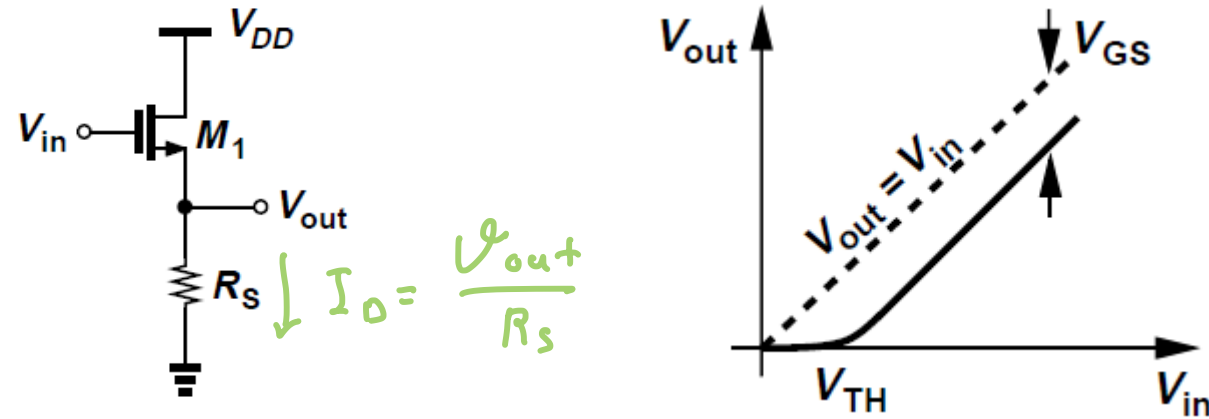


- For $V_{in} < V_{TH}$, M_1 is off and $V_{out} = 0$
- As V_{in} exceeds V_{TH} , M_1 turns on in saturation since $V_{DS} = V_{DD}$ and $V_{GS} - V_{TH} \approx 0$ and I_{D1} flows through R_S
- As V_{in} increases further, V_{out} follows the input with a difference (level shift) equal to V_{GS}
- Input-output characteristic neglecting channel-length modulation can be expressed as

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \overbrace{(V_{in} - V_{TH} - V_{out})^2}^{I_D} R_S = V_{out}$$

Source Follower

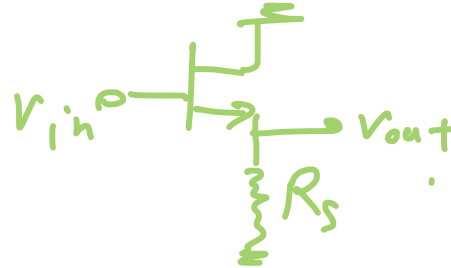- Small-signal gain can be obtained more easily using small-signal equivalent model




- We have,

- KVL: $V_{in} - V_1 = V_{out}, V_{bs} = -V_{out}$

- KCL: $g_m V_1 - g_{mb} V_{out} = V_{out} / R_S$

- Therefore,
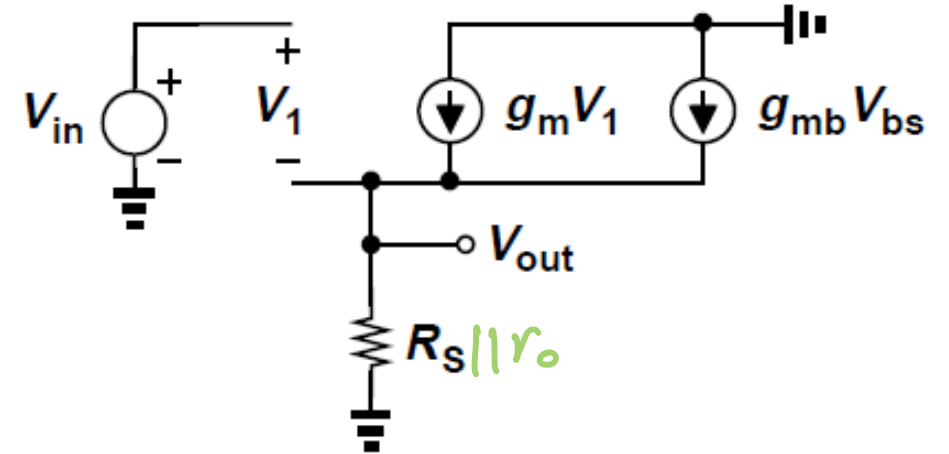
$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$



$$\rightarrow \frac{V_{out}}{V_{in}} = A_v = \dots$$


$$A_v > 0$$

$$A_v < 1$$

Source Follower

large

$$\frac{g_m R_S}{1 + g_m R_S}$$

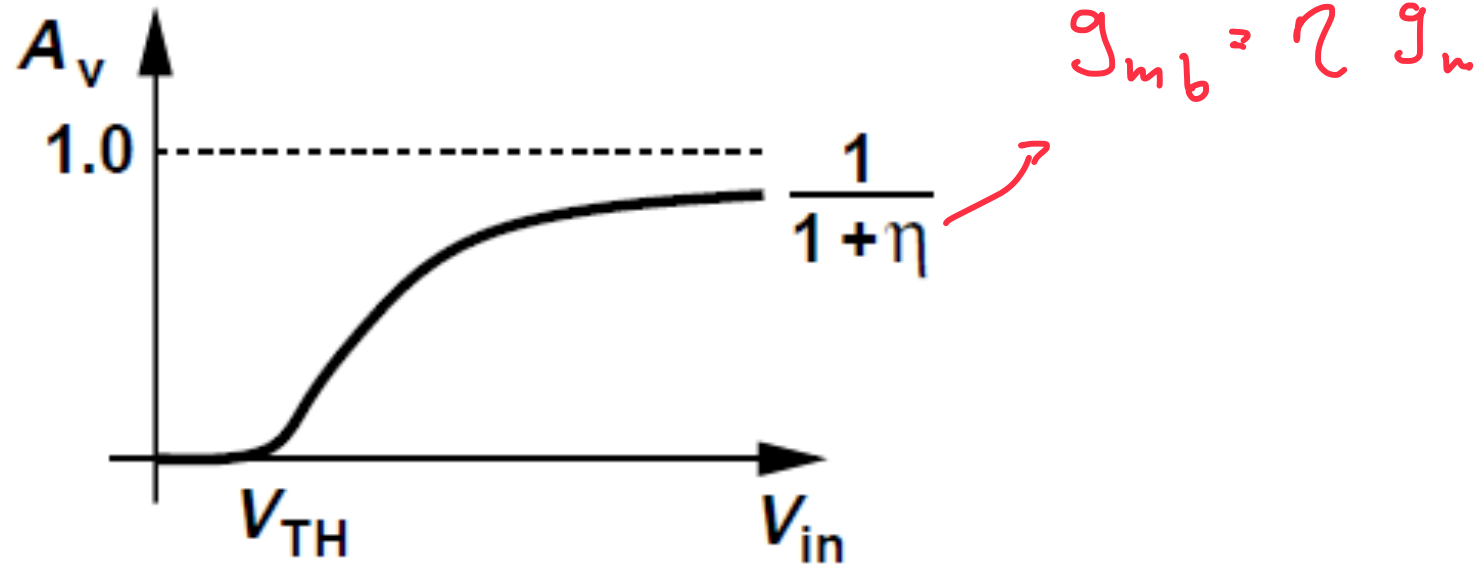



- Voltage gain begins from zero for $V_{in} \approx V_{TH}$ ($g_m \approx 0$), and monotonically increases
- As drain current and g_m increase, A_v approaches

$$g_m / (g_m + g_{mb}) = 1 / (1 + \eta)$$


- Even if $R_S = \infty$, voltage gain of a source follower is not equal to one

Source Follower

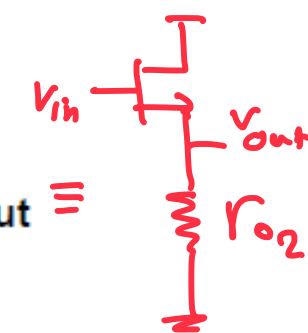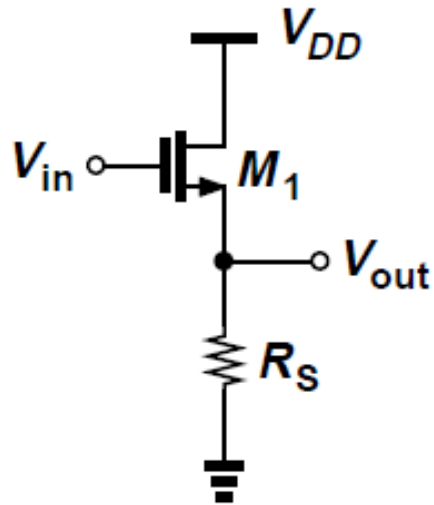
$$A_v = \frac{g_m r_{o2}}{1 + g_m r_{o2}}$$



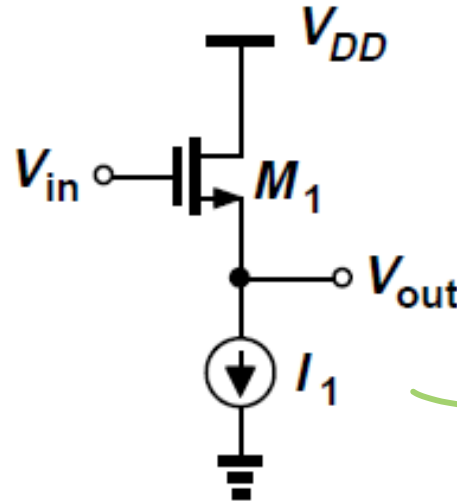
$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH} - V_{out})^2 R_S = V_{out}$$




Source

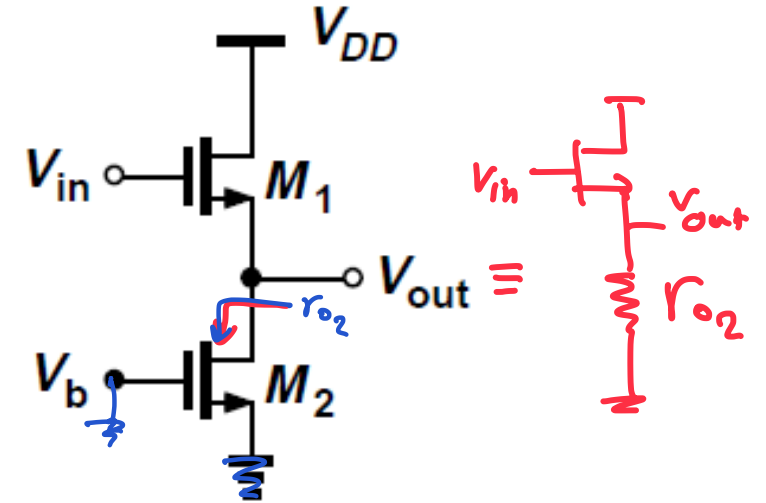

- Drain current of M_1 depends heavily of input dc level
- Even if V_{TH} is relatively constant, the increase in V_{GS} means that $V_{out} (=V_{in}-V_{GS})$ does not follow V_{in} faithfully, incurring nonlinearity
- To alleviate this issue, the resistor can be replaced by a constant current source
- Current source itself is implemented as an NMOS transistor operating in the saturation region

Source Follower: output impedance



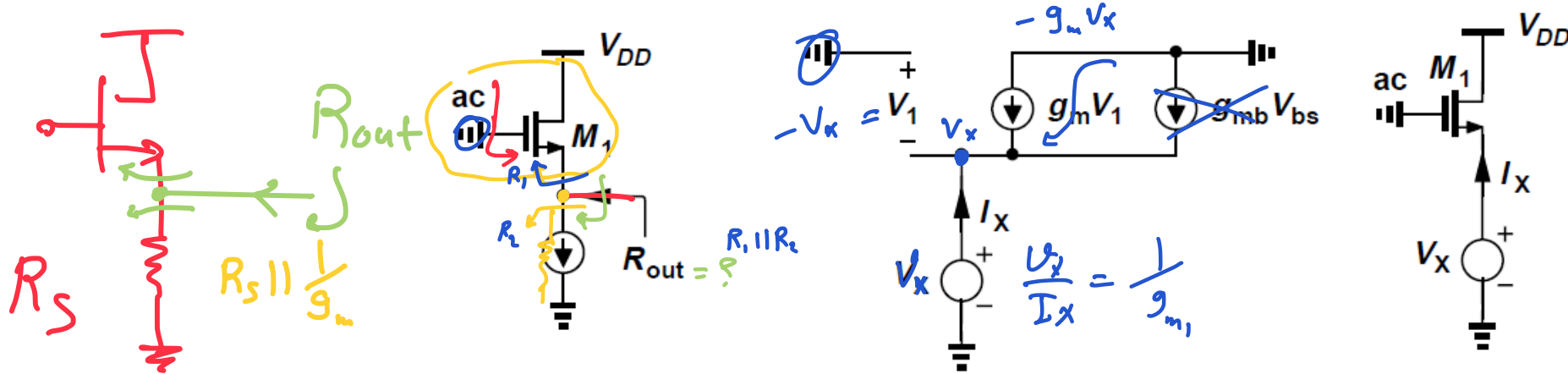


- From small-signal equivalent circuit,
- It follows that $I_X - g_m V_X - g_{mb} V_X = 0$ and $V_X = -V_{bs}$
- Body effect decreases output resistance of source followers
- If V_X decreases by ΔV so the drain current increases
 - w/o body effect, V_{GS} increases by ΔV
 - with body effect, V_{TH} decreases as well, thus $(V_{GS} - V_{TH})^2$ and I_{D1} increase by a greater amount, hence lower output impedance

$$R_{out} = \frac{1}{g_m + \cancel{g_{mb}}}$$


Source Follower

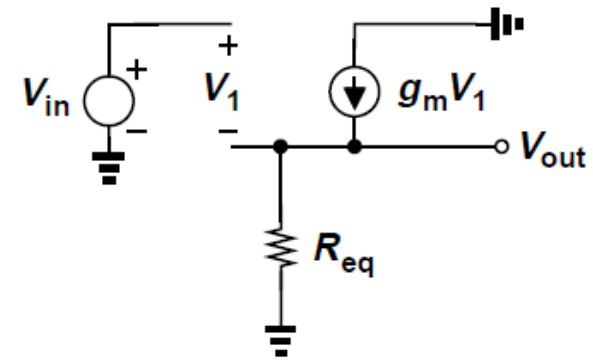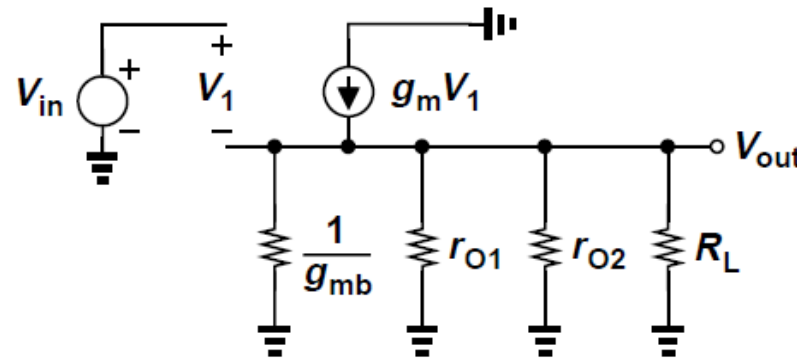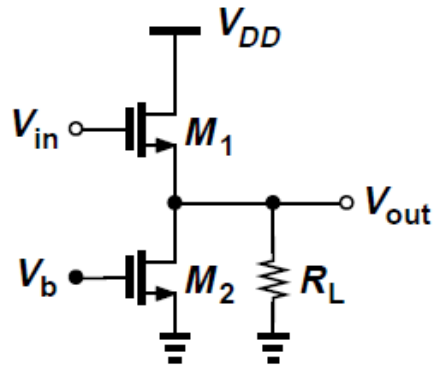- Small-signal equivalent circuit with a finite load resistance and channel-length modulation is shown






- Recall that gain for R_S was
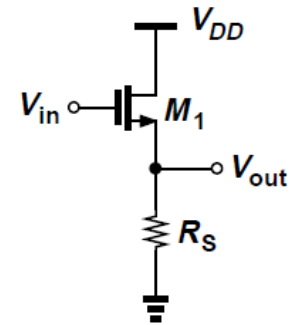
$$A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$



- Gain = ?


Issues with Source Follower

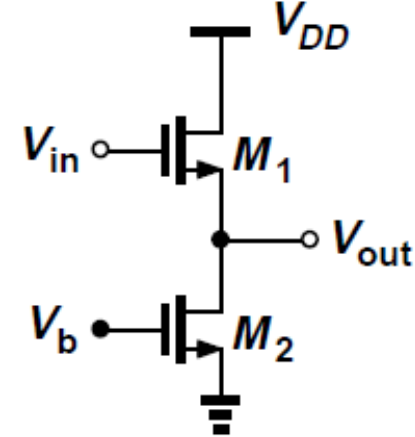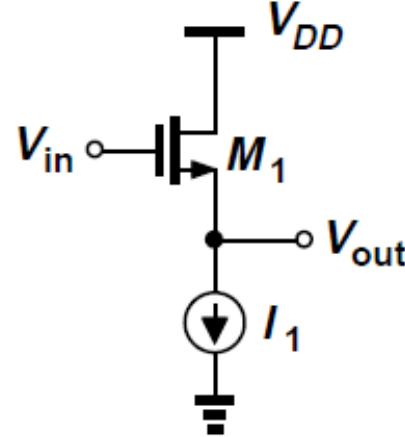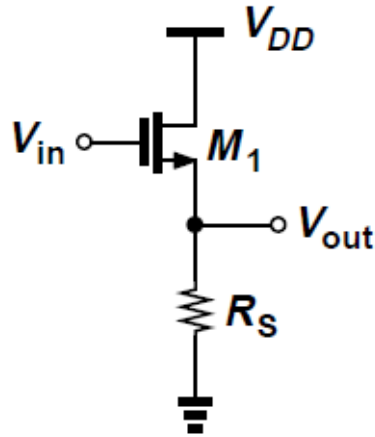

- Source followers exhibit high input impedance and moderate output impedance, but at the cost of
 - Nonlinearity
 - Voltage headroom limitation $\longrightarrow V_{Sw,pp}$ small!
- Even when biased by ideal current source, there is input-output nonlinearity due to nonlinear dependence of V_{TH} on the source potential


Common-Gate Stage

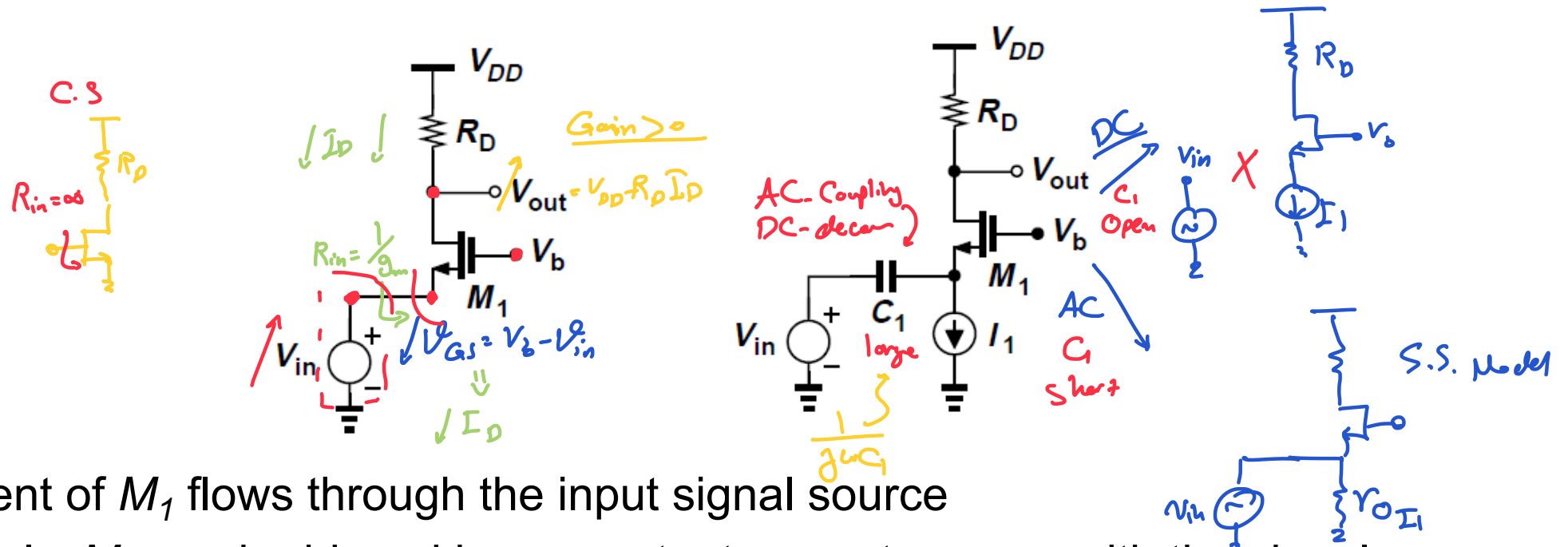- A common-gate (CG) stage senses the input at the source and produces the output at the drain
- Gate is biased to establish proper operating conditions



- Bias current of M_1 flows through the input signal source
- Alternatively, M_1 can be biased by a constant current source, with the signal capacitively coupled to the circuit

Common-Gate Stage: Large-signal behavior

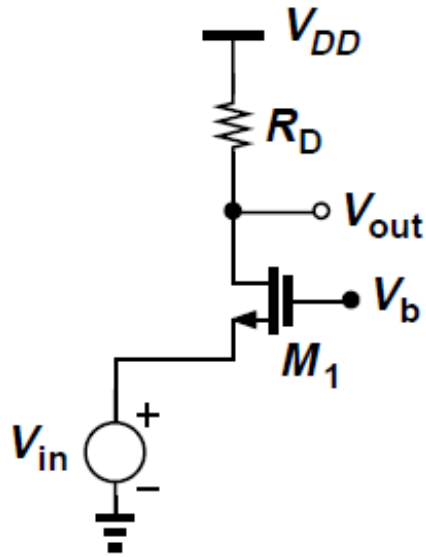

- Assume V_{in} decreases from a large positive value and that $\lambda=0$
- For $V_{in} \geq V_b - V_{TH}$, M_1 is off and $V_{out} = V_{DD}$
- For lower values of V_{in} , if M_1 is in saturation,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \underbrace{(V_b - V_{in} - V_{TH})^2}_{V_{GS}}$$

- As V_{in} decreases further, so does V_{out} driving M_1 into the triode region if


$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D = V_b - V_{TH}$$

- In the region where M_1 is saturated, we can express the output voltage as

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

Common-Gate Stage: Input-output characteristic

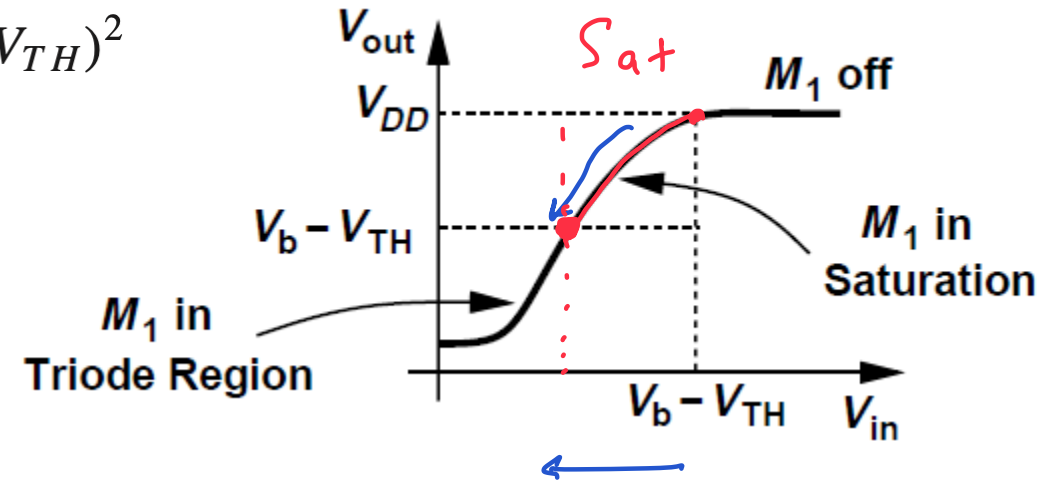
- For M_1 in saturation, $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$
 - $V_{out} = ?$




- Small-signal gain: $g_m(1 + \eta)R_D$

Similar to
C.S. Amp

$$R_{out} = R_D || r_o$$

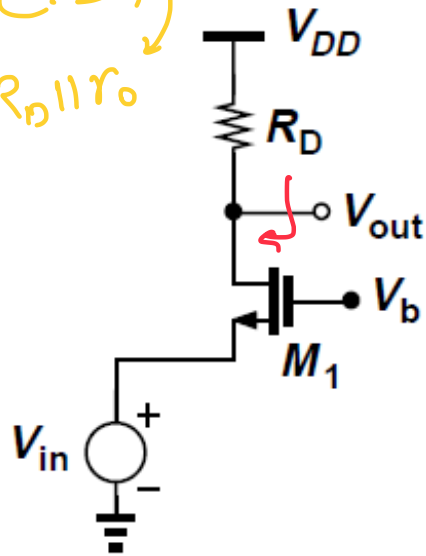


body effect.

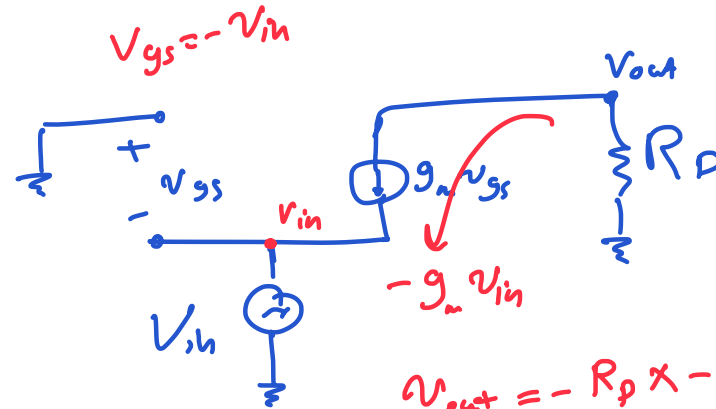

$$v_{out} = -R_D \times -g_m v_{in}$$

$$\Rightarrow A_{vgs} = g_m R_D$$

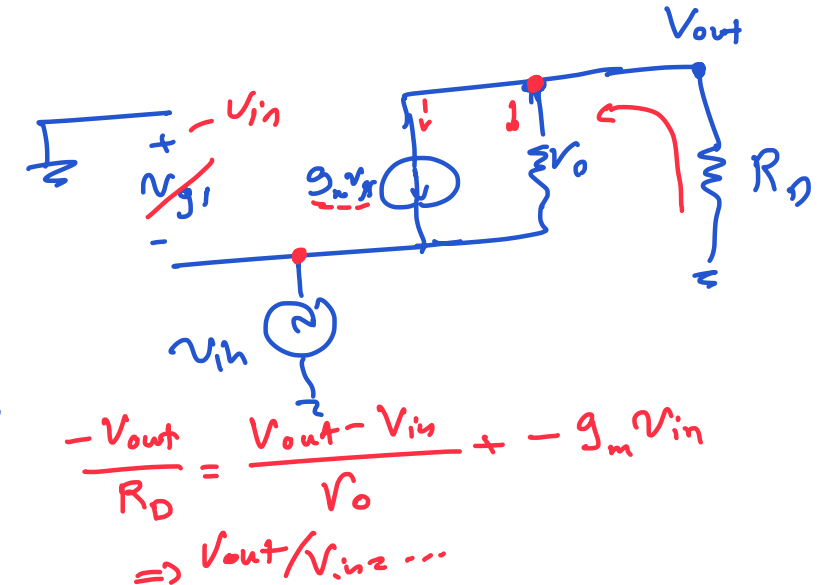


$$\frac{-v_{out}}{R_D} = \frac{v_{out} - v_{in}}{r_o} + -g_m v_{in}$$

$$\Rightarrow v_{out}/v_{in} = \dots$$

Common-Gate Stage


- Gain of the common-gate (CG) stage is positive
- Body effect increases the effective transconductance of the stage
- The minimum allowable value of V_{out} is $V_b - V_{TH}$
 - Min of $V_b = ?$
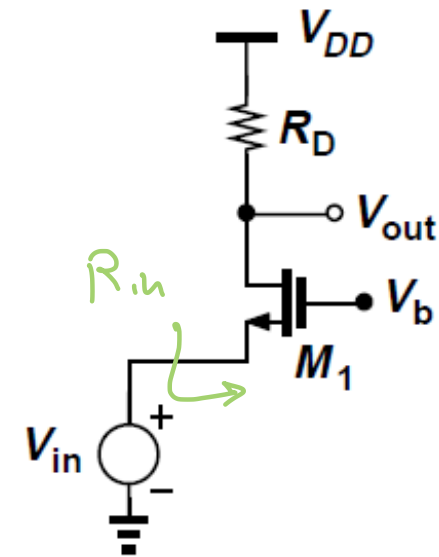
$$\left\{ \begin{array}{l} V_{out, Min} = V_b - V_{th} \\ V_{out, Max} = V_{DD} \end{array} \right.$$



Common-Gate Stage (with r_o & R_S)

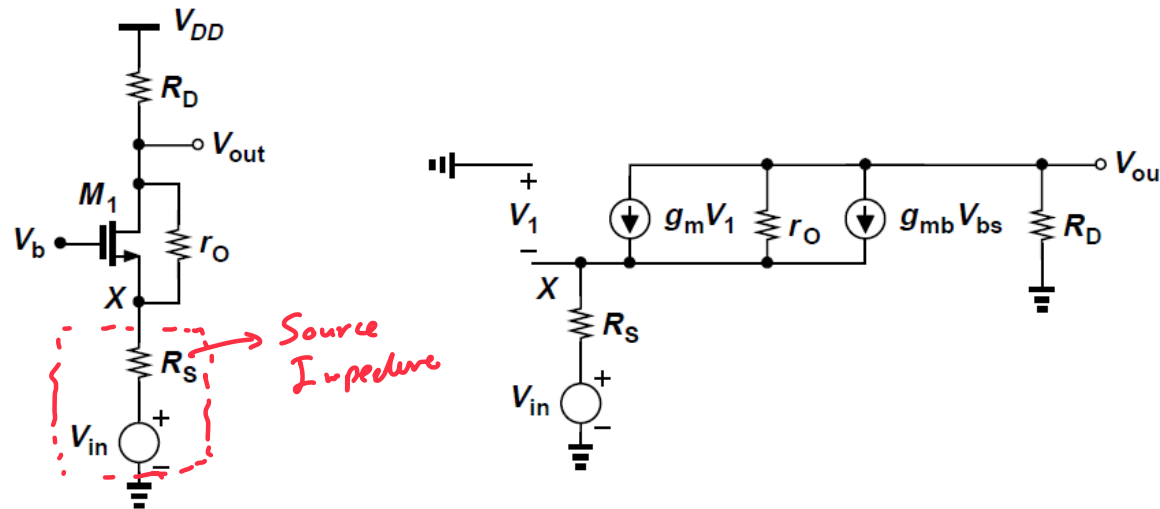- Consider output impedance of transistor (r_o) and impedance of the signal source (R_S):




- In small-signal equivalent circuit, since current flowing R_S is $-V_{out}/R_D$,

$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0 \quad (1)$$

- Moreover, since current through r_o is $-V_{out}/R_D - g_m V_1 - g_{mb} V_1$

$$r_o \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out} \quad (2)$$

Common-Gate Stage

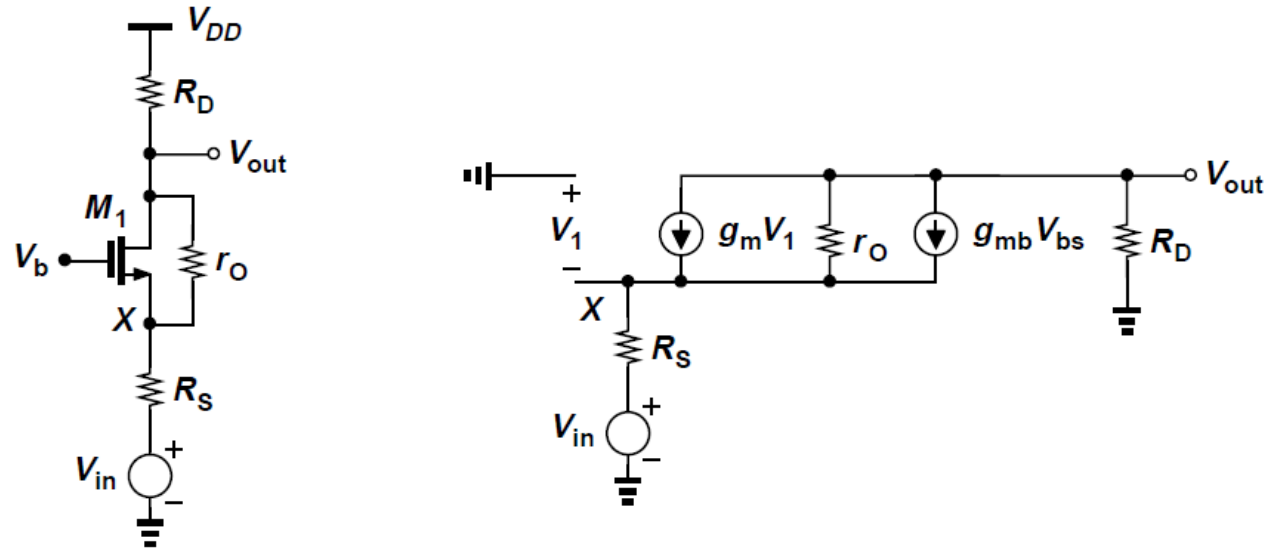

- Substituting V_1 from (1) in (2),

$$r_O \left[\frac{-V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \frac{R_S}{R_D} - V_{in} \right) \right] - \frac{V_{out} R_S}{R_D} + V_{in} = V_{out}$$





- Therefore,

$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D$$

- The voltage gain expression is similar to that of a degenerated CS stage

Cascode Stage

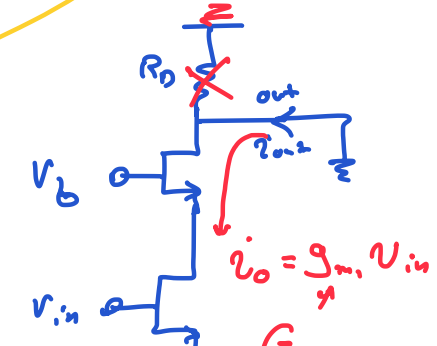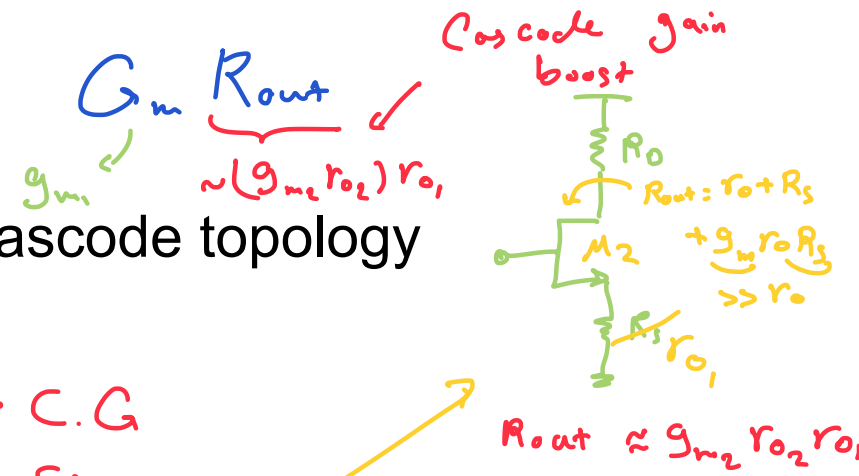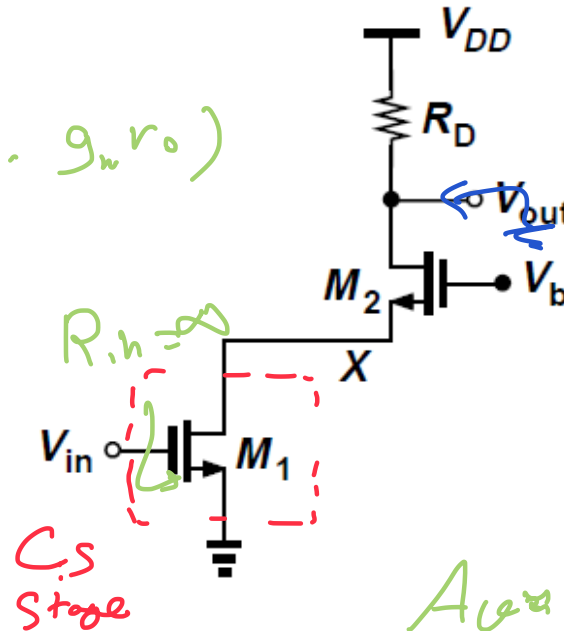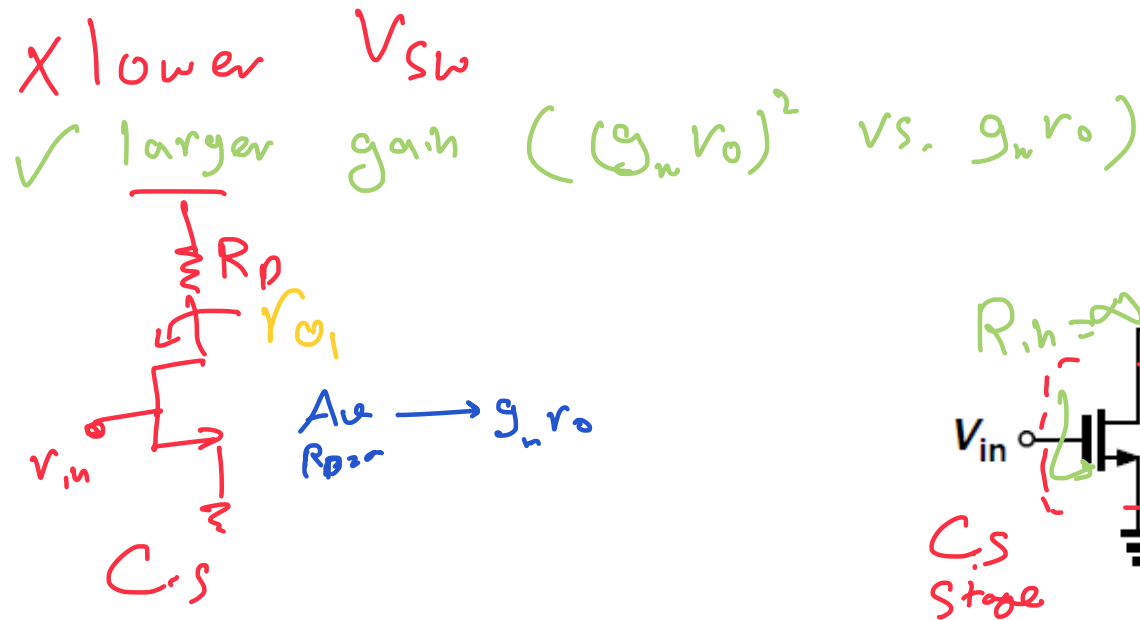
- The cascade of a CS stage and a CG stage is called a cascode topology



- M_1 generates a small-signal drain current proportional to the small-signal input V_{in} and M_2 simply routes the current to R_D
- M_1 is called the input device and M_2 the cascode device
- M_1 and M_2 in this example carry equal bias and signal currents

Cascode Stage: Qualitative Analysis

- Assume both transistors are in saturation and $\lambda = \gamma = 0$
- If V_{in} rises by ΔV , then I_{D1} increases by $g_{m1}\Delta V$
 - This change in current flows through the impedance seen at X, i.e., the impedance seen at the source of M_2 , which is equal to $1/g_{m2}$
 - Thus, V_X falls by an amount given by $g_{m1}\Delta V \cdot (1/g_{m2})$
 - This change in I_{D1} also flows through R_D , producing a drop of $g_{m1}\Delta V R_D$ in V_{out} , just as in a simple CS stage

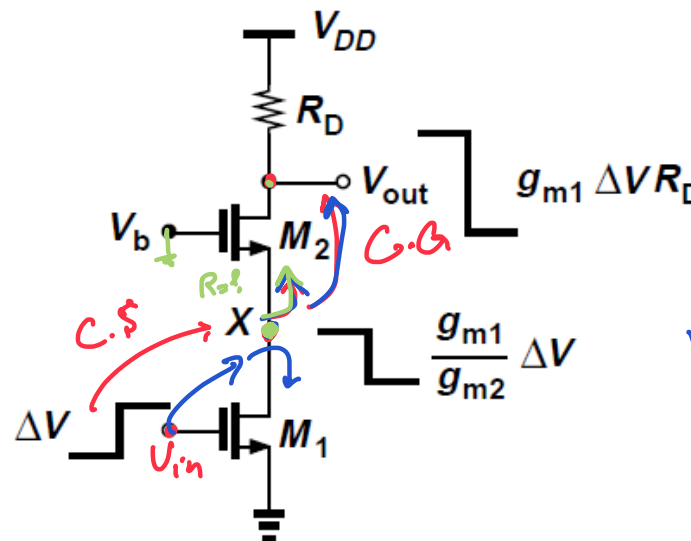

$$A_{ve} = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_X} \times \frac{V_X}{V_{in}}$$

C.G. gain C.S. gain

$$= -g_{m1} (r_{o1} \parallel \frac{1}{g_{m2}})$$

$$= -\frac{g_{m1}}{g_{m2}}$$


\times

$$g_{m2} \times (R_{out} \parallel R_D)$$

\times


$$r_{o1} r_{o2} + g_{m1} r_{o1} r_{o2}$$

Cascode Stage: Bias Conditions

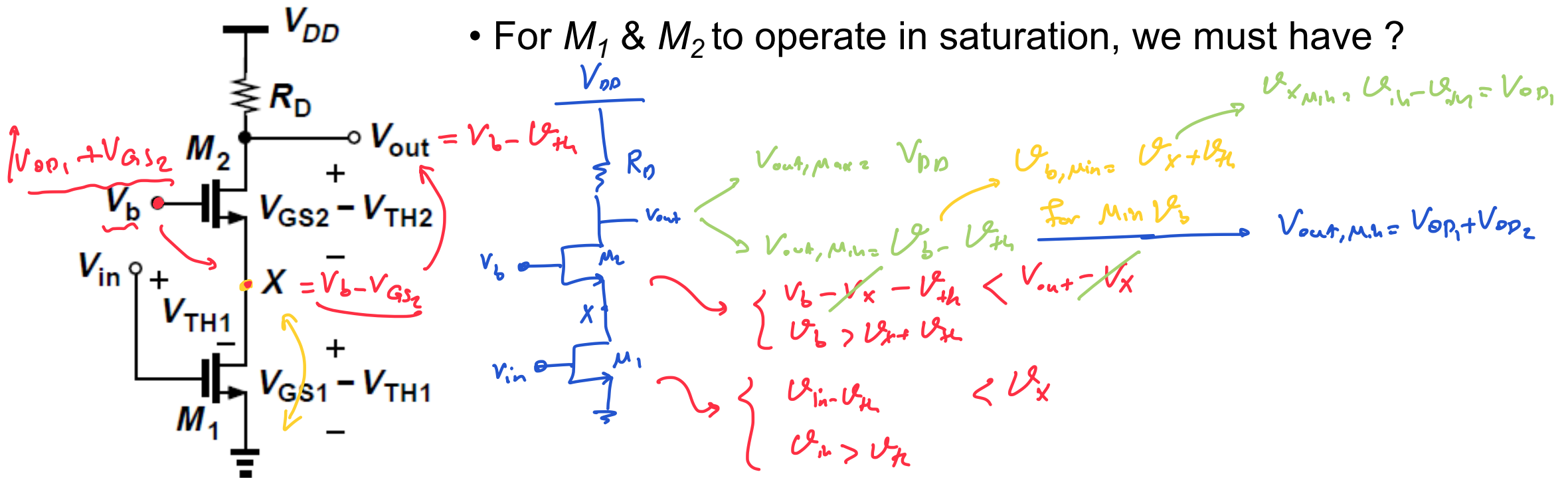

- Minimum output level for which both transistors are in saturation is equal to the sum of overdrives of M_1 and M_2
- Addition of M_2 to the circuit reduces the output voltage swing by at least its overdrive voltage (compared with a basic CS amplifier)

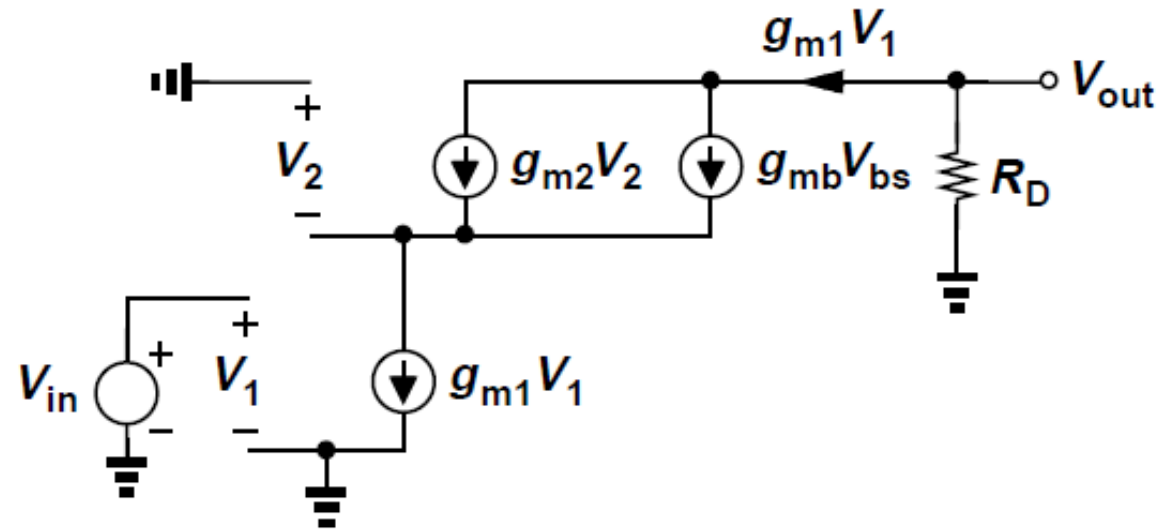
Cascode Stage: Small-signal characteristics




- Assume both transistors operate in saturation and $\lambda=0$
- Voltage gain is equal to that of a common-source stage because the drain current produced by the input device must flow through the cascode device (M_2): ($G_m=g_{m1}$)
- This result is independent of the transconductance and body effect of M_2
- Can be verified using $A_v = -G_m R_{out}$

Cascode Stage: Output Impedance

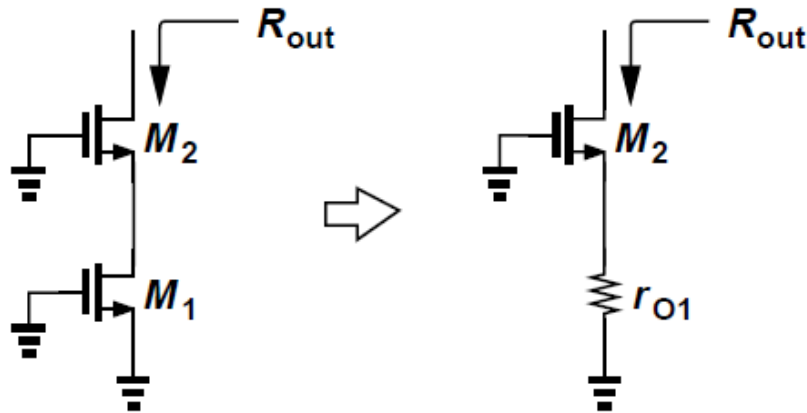- Important property of the cascode structure is its high output impedance


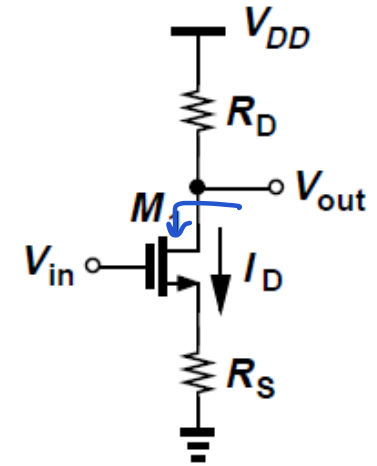
$$\begin{aligned}
 R_{out} &= [1 + (g_m + g_{mb})R_S]r_O + R_S \\
 &= [1 + (g_m + g_{mb})r_O]R_S + r_O \\
 &= r_{O2} + g_{m2}r_{O2}R_S + R_S \\
 &\text{In here if } R_S = r_{O1}
 \end{aligned}$$



- For calculation of R_{out} , the circuit can be viewed as a common-source stage with a degeneration resistor equal to r_{O1}
- Thus, $R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2}$
- Assuming $g_m r_O \gg 1$, we have $R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$
- M2 boosts the output impedance of M1 by a factor of $(g_{m2} + g_{mb2})r_{O2}$

Cascode stage with current source load


- Voltage gain can be maximized by maximizing G_m and/or R_{out}
- Since G_m is typically determined by the transconductance of a transistor and has trade-offs with the bias current and device capacitances, it is desirable to increase voltage gain by maximizing R_{out}

- If both M_1 and M_2 operate in saturation, $G_m \approx g_{m1}$ and yielding

$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$

- Maximum gain is roughly equal to the square of the intrinsic gain of the transistors
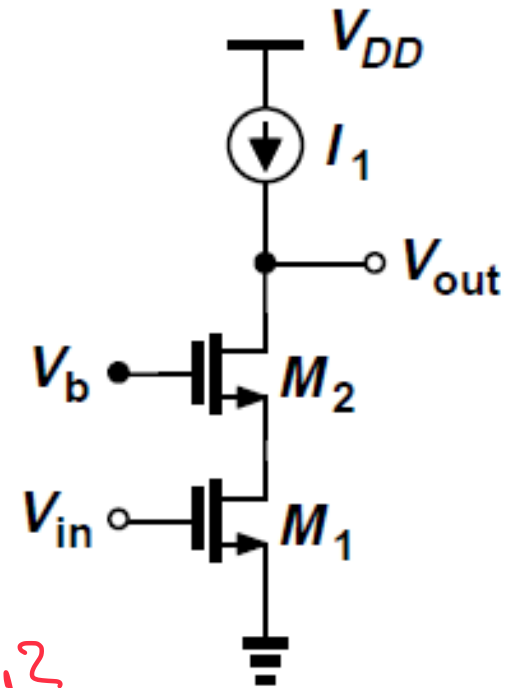
$$\underline{A_v = (g_{m2} + g_{mb2})r_{O2}g_{m1}r_{O1}} \approx (g_m r_o)^2$$



Summary of Amplifier Designs