



Midterm Exam

400 Exam Date: Nov. 13 (5-7pm)

Assume: $V_{DD}=1.5V$, $V_{th,n,p}=0.3V$, $\mu_n C_{ox} = \frac{200\mu A}{V^2}$, $\mu_n = 2\mu_p$, $\lambda_p = 0.2V^{-1}$, $\lambda_n = 0.1V^{-1}$, $\gamma = 0$ for both NMOS and PMOS devices.

1. (15 pts) Suppose that while V_{out} at the beginning is at 5V, V_{G1} and V_{G2} will rise to 1V and 2V respectively and the capacitance starts discharging through $M_{1,2}$. Answer the following questions:

- Find the regions of operation for M_1 and M_2 as C_L discharges. *Also levels!!*
- Plot V_x and V_{out} over time, mark the voltages where M_1 or M_2 transit into another operation region (a qualitative plot is enough, no need to solve the equations!).

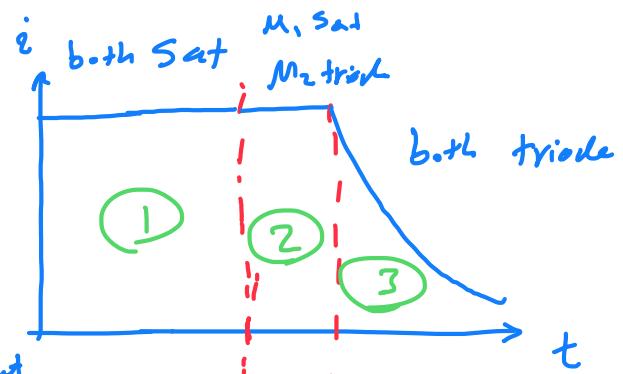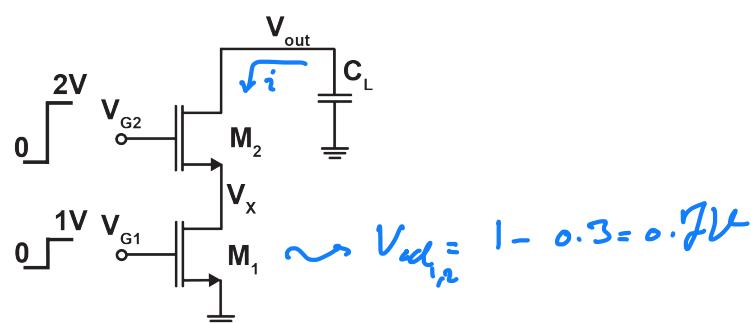Set 10

① Both M_1 & M_2 are in Sat.

i is set by V_{gs} , & since $I_1=I_2$

$$V_{gs,1}=V_{gs,2} \rightarrow V_x = 2 - 1 = 1V$$

V_x stays at 1V to keep $I_2=I_1$, while V_{out}


V_{out} voltage drops linearly.

② Once V_{out} reaches $V_x + V_{od,n} = 1.7V$

M_2 goes into triode, this causes

V_x to start dropping, but the current is

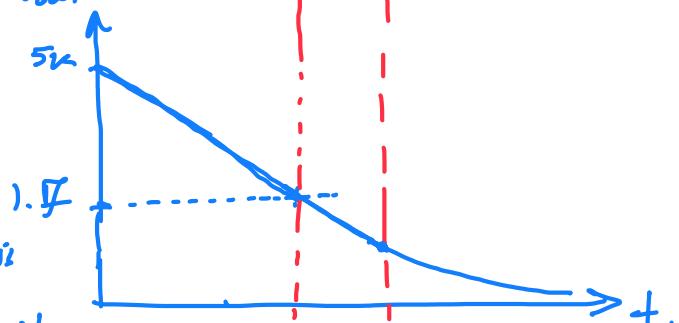still fixed by M_1 since $V_x > V_{od,n}$.




③ when V_x gets smaller than 0.7


M_1 also goes into triode.

Circuit behaves like an RL


circuit until V_x & V_{out} go to 0V.

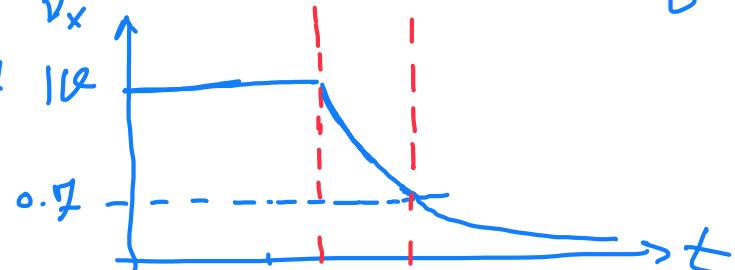

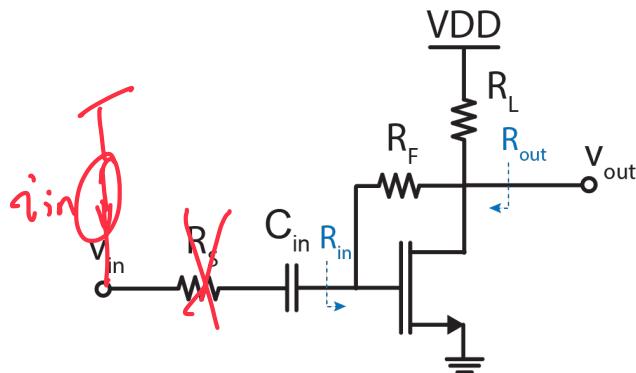2. (25 pts) For the single-stage amplifier given below, answer to the following questions. Assume C_{in} is very large and will be short in small-signal models. Your solution should only depend on g_m , r_o , R_s , R_F , and R_L .



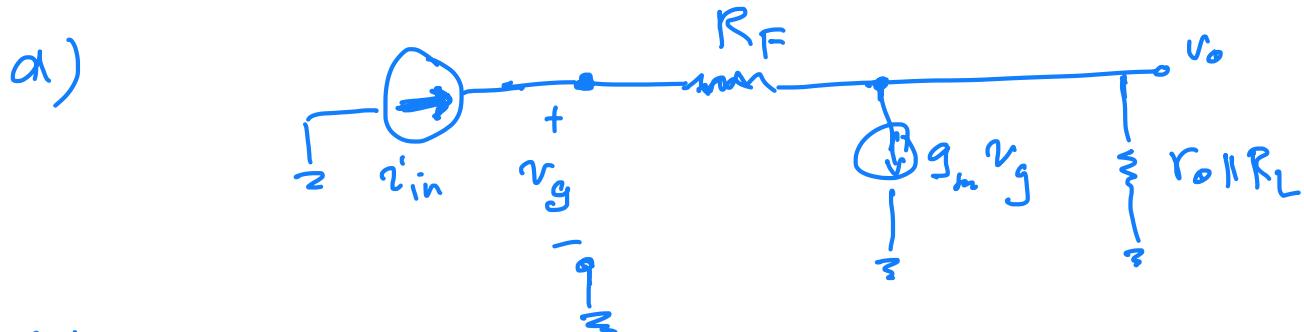- Draw the small-signal model.
- Find the small-signal gain (V_{out}/V_{in}) (V_{out}/i_{in})
- Find R_{out} and R_{in} . $\frac{V_o}{i_{in}}$



b)

$$\left\{ \begin{array}{l} i_{in} = g_m V_g + \frac{V_o}{r_o \parallel R_L} \\ V_g = V_o + i_{in} R_F \end{array} \right. \Rightarrow i_{in} = g_m V_o + i_{in} g_m R_F + \frac{V_o}{r_o \parallel R_L}$$

$$\Rightarrow \boxed{\frac{V_o}{i_{in}} = \frac{1 - g_m R_F}{g_m + \frac{1}{r_o \parallel R_L}}}$$

c)


$$R_{in} = \frac{V_g}{i_{in}} = \frac{V_o}{i_{in}} + R_F = \frac{1 - g_m R_F}{g_m + (r_o \parallel R_L)^{-1}} + R_F$$

$$= \frac{1 + R_F (r_o \parallel R_L)^{-1}}{g_m + (V_o \parallel R_L)^{-1}}$$

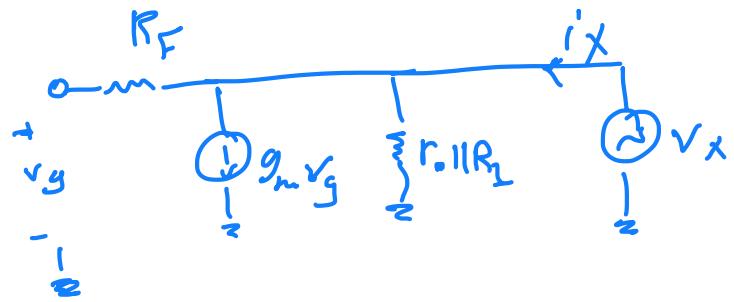d) R_{out} :

$$v_g = v_x$$


$$\dot{i}_x = \frac{v_x}{r_o \parallel R_L} + g_m v_g r_x$$



$$\Rightarrow R_{out} = \frac{v_x}{i_x} = \frac{1}{g_m + r_o \parallel R_L} = \underline{\frac{1}{g_m} \parallel r_o \parallel R_L}$$

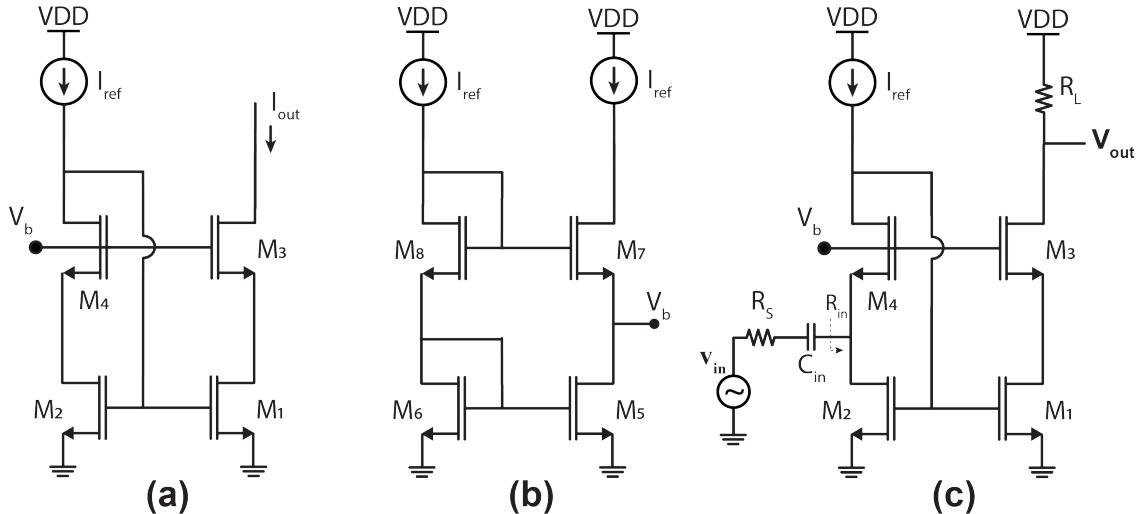3. (30 pts) For the current-mirror circuit shown in Figure a,

- If $(W/L)_1 = (W/L)_3 = k(W/L)_2 = k(W/L)_4$, what is the ratio of I_{out}/I_{ref} ?
- What is the minimum working voltage at the output as a function of V_{od} and V_b ? What should be V_b value to minimize this voltage limit?
- Suppose we want to use the circuit shown in Figure b to generate this V_b . Assuming W/L of M_{5-7} is the same as W/L of M_2 , what should be the ratio of $(W/L)_8/(W/L)_1$?



Now we decided to turn this current mirror into an amplifier shown in Figure c. Assume that C_{in} is a very large decoupling cap (short in small-signal) and the input voltage source has a series resistance of R_s :

- Find the gain (V_{out}/V_{in}) and input and output impedances (assume $\lambda = 0$). Write down your answers in terms of V_{od} voltages of M_{1-4} , R_s , R_L , and I_{ref} .

$$g_{m1-4}, R_{ref}$$

a) $I_{out} / I_{ref} = k$

b) $V_{o,min} = V_b - V_{th}$

$V_{o,min} = 2V_{od}$

$V_{b,min} = V_{od} + V_{gs3}$

Since M_{1-4} have the same V_{od} $\rightarrow V_{b,min} = V_{od} + V_{gs}$

c) We need $V_b = V_{od} + V_{gs}$




from Circuit b: $V_b = V_{gs} + V_{gs8} - V_{gs}$

$\Rightarrow V_{od8} = V_{gs8} - V_{th} = V_{gs} - V_{th} + V_{od} \approx 2V_{od}$

\Rightarrow For the same current of I_{ref} to have

$$V_{OD8} = 2V_{OD}, \text{ we need } \left(\frac{W}{L}\right)_8 = \frac{1}{4} \left(\frac{W}{L}\right)$$

d)

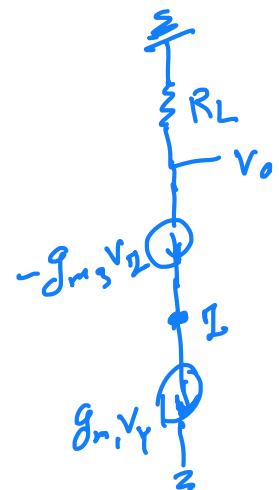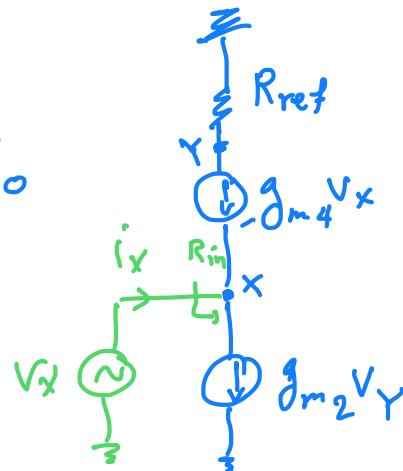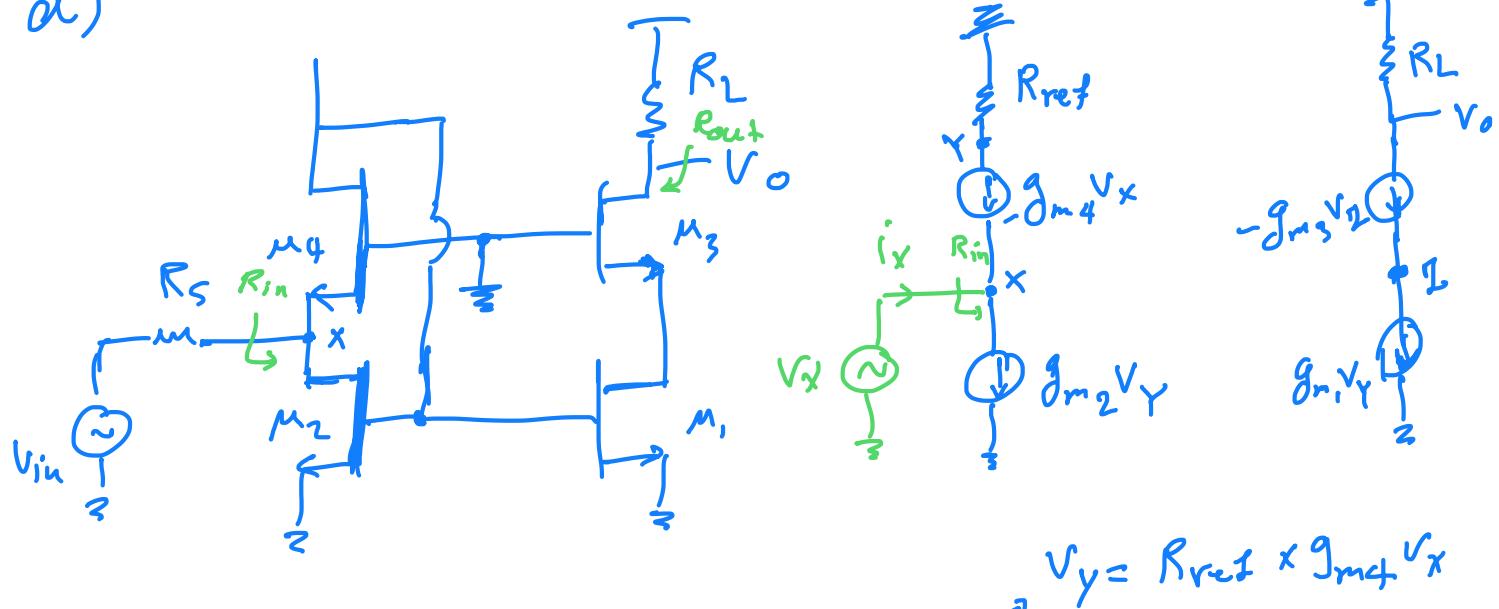

$$V_y = R_{ref} \times g_{m4} V_x$$

$$R_{in}: i_x + (-g_{m4} V_x) = g_{m2} V_y$$

$$\Rightarrow 2i_x = g_{m4} V_x + g_{m4} g_{m2} R_{ref} V_x$$

$$\Rightarrow R_{in} = \frac{V_x}{i_x} = \frac{1}{g_{m4} (1 + g_{m2} R_{ref})}$$


$$R_{out}: R_{out} = R_L \parallel \infty = R_L$$

$$G_m: i_{out+} = g_m, V_y = g_m g_{m4} R_{ref} V_x$$

$$V_x = \frac{R_{in}}{R_{in} + R_s} V_{in} \Rightarrow G_m = \frac{g_m g_{m4} R_{ref} R_{in}}{R_{in} + R_s}$$

$$A_{12} = -G_m R_{out}$$

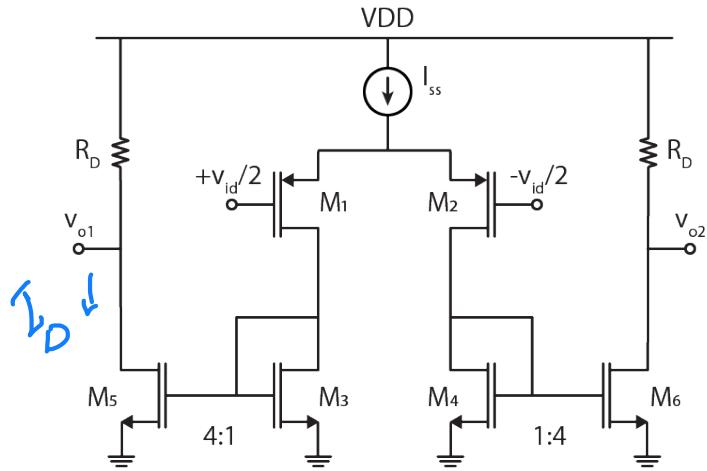4. (30 pts) For the differential amplifier shown below:



$$VDD = 1.2V, R_D = 1.5k\Omega, R_{SS} = 10k\Omega$$

$$\left(\frac{W}{L}\right)_{3,4} = 2 \left(\frac{W}{L}\right)_{1,2} = 200, \left(\frac{W}{L}\right)_5 = 4 \left(\frac{W}{L}\right)_3, \left(\frac{W}{L}\right)_6 = 4 \left(\frac{W}{L}\right)_4$$

- a) What should be the I_{SS} value in order to bias output nodes ($V_{o1/2}$) at $VDD/2=0.6V$?
- b) Based on I_{SS} value from part a, what is the g_m and V_{od} of $M_{1,2}$?
- c) Draw the differential-mode half circuit and calculate the differential gain ($\frac{v_{o2}-v_{o1}}{v_{id}}$)?
- d) Draw the common-mode half circuit and calculate single ended common-mode gain ($\frac{v_{o1/2}}{v_{cm}}$)?
- e) Find differential and single-ended peak-to-peak output swing.
- f) If we implement the tail current with a PMOS with $W/L=400$, what would be the input common-mode range?


a) $V_o = 0.6V \rightarrow I_D = \frac{0.6V}{1.5k\Omega} = 0.4mA$

$$I_D = 4 \times \frac{I_{SS}}{2} = 2 I_{SS} \Rightarrow I_{SS} = 0.2mA$$

b) $0.1mA = \frac{1}{2} \times 100 \times \frac{0.2mA}{V^2} \times V_{od}^2 \Rightarrow V_{od,1,2} = 0.1V$

$$g_m = \frac{25}{V_{od}} = \frac{0.2mA}{0.1} = 2mS$$

c)

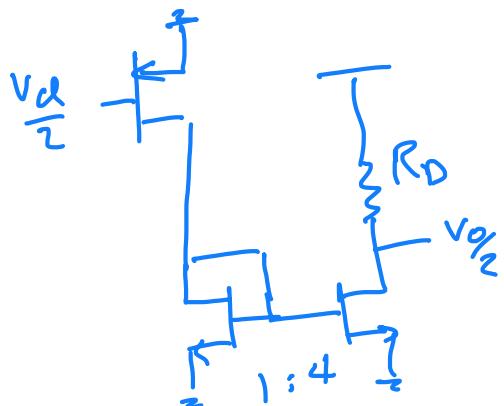


$$A_d = g_m \times 4 \times (R_D || r_{06})$$

$$r_{06} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1 \times 0.4 \text{ mA}} = 25 \text{ k}\Omega \gg R_D$$

$$\Rightarrow A_d = 2 \text{ mS} \times 4 \times 1.5 \text{ k}\Omega = 12$$

d)

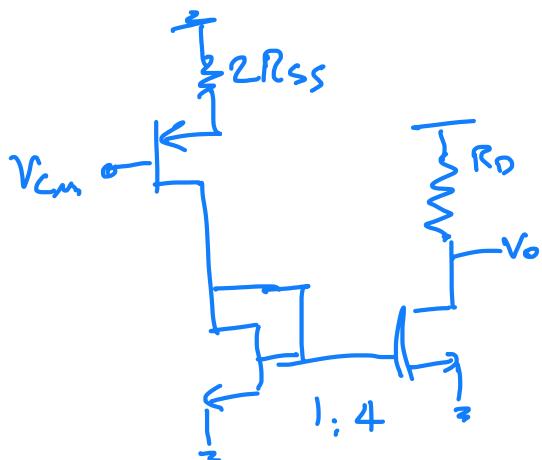

$$A_{CM} = \frac{V_o}{V_{CM}} = \frac{g_m}{1 + 2R_{SS} \times g_{dm}} \times 4 \times (R_D || r_{06})$$

$$= \frac{A_d}{1 + g_m 2R_{SS}} = \frac{12}{1 + 2 \text{ mS} \times 2 \times 10 \text{ k}\Omega} = \frac{12}{40}$$

$$\Rightarrow A_{CM} \approx 0.3$$

e)

$$\left. \begin{array}{l} V_{out, max} = V_{DD} = 1.2 \text{ V} \\ V_{out, min} = V_{OP5,6} = 0.1 \text{ V} \end{array} \right\}$$

$$\rightarrow \overline{V_{swing, pp}} = 1.1 \text{ V}$$

single ended.

$$V_{OD5}: 0.4 \text{ mA} = \frac{1}{2} \times \frac{0.4 \text{ mA}}{\text{V}\text{e}^2} \times 200 \times V_{od}^2 \rightarrow \boxed{V_{od} = 0.1 \text{ V}}$$

Dif. peak-to-peak swing will be $2 \times 0.1 = \underline{2.2 \text{ V}}$

$$f) 0.2 \text{ mA} = \frac{1}{2} \times \frac{0.2 \text{ mA}}{\text{V}\text{e}^2} \times 200 \times V_{od_f}^2$$

$$\Rightarrow V_{od_f} = 0.1 \text{ V}$$

$$V_{in, CM} \leq V_{DD} - (V_{od_f} + V_{gs1,2})$$

$$\Rightarrow \boxed{V_{in, CM} \leq 1.2 - (0.1 + 0.1 + 0.3)} \quad 7$$

Additionally for M_1 & M_2 to stay in Sat:

$$\underbrace{V_{D_{1,2}}}_{-|V_{th}|} \leq V_{in,cm} \Rightarrow V_{DD_3} \leq V_{in,cm}$$

$$V_{GS_3} = V_{DD_3} + V_{th}$$

$$\Rightarrow 0.1V \leq V_{in,cm}$$