 


1. Dennard Scaling: Consider a basic NMOS device with quadratic I/V-relation that we studied in the first week ( $I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$ ). Now suppose that every next generation of this CMOS technology will benefit from scaling down all the dimensions (W, L, thicknesses) by a factor of namely  $s$  ( $s$  is smaller than 1).

- What should be the nominal  $s$  value for Moore's law to be true (i.e. transistor density will be doubled in every new generation)?
- If we want to keep all the electrical fields constant (in particular, the field in gate oxide capacitance), how should the voltages scale? What about threshold voltage?
- Explain how the following parameters change in this type of scaling:  
Density of transistors per  $\text{mm}^2$ , drain-source current (in saturation regime), transconductance ( $g_m$ ), device capacitances ( $C_{GS}$ ,  $C_{GD}$ ,  $C_{DB}$ ), output resistance ( $r_o$ )
- If the speed of circuits can be estimated from charging/discharging time of the device capacitances, how does the speed ( $f$ ) scale up? (*Hint*: you can estimate the time from  $I = \frac{C_{GS} dV}{dt}$  and estimate  $f$  to be linearly proportionate to  $\frac{1}{dt}$ )
- If power consumption for each MOS device can be estimated from charging/discharging energy of gate capacitance ( $C_{GS}$ ) as  $P = C_{GS} V_{DD}^2 f$ . How does a single transistor's dynamic power consumption scale? How about the total power per area?
- What are the obstacles and challenges of this scaling down trend? How far do you think we can benefit from this?

2. Switch Cap: We can sample an analog signal using a simple MOS switch and store the analog value on a capacitor. Circuit diagram below shows a simple "switch cap" circuit during the charging cycle:



- If the cap is discharged initially ( $V_X = 0$ ), describe how  $V_X$  changes after the switch turns on, and identify PMOS working regions (assume  $V_{TH} = -0.4V$ ,  $\mu_p C_{ox} = \frac{100 \mu A}{V^2}$ ,  $W/L = 1 \mu m / 65 \text{nm}$ ,  $C = 100 \text{fF}$ ).
- Write down governing I/V equations for each regime and draw the plot of  $V_X$  over time. (*Hint*: MOS can be modeled as a current source in the saturation region and a resistor in the triode)
- What will happen if the input voltage ( $V_{in}$ ) is at 0.3V instead of 1V? Does the sampling circuit still work? If not, how can we solve this issue by using another circuit? (*Hint*: what if the switch was an NMOS?)

3. Razavi 2.13 (parts a and c): The transit frequency,  $f_T$ , of a MOSFET is defined as the frequency at which the small-signal current gain of the device drops to unity while the source and drain terminals are held at ac ground.

a. Prove that:

$$f_T = \frac{g_m}{2\pi(C_{GD} + C_{GS})}$$

Note that  $f_T$  does not include the effect of the S/D junction capacitance. *Hint*: Small-signal current gain can be derived by calculating drain current using the small-signal model when we have an ac current source at the gate.

c. For a given bias current, the minimum allowable drain-source voltage for operation in saturation can be reduced only by increasing the width and hence the capacitances of the transistor. Using square-law characteristics, prove that

$$f_T = \frac{\mu_n}{2\pi} \frac{V_{GS} - V_{TH}}{L^2}$$

This relation indicates how the speed is limited as a device is designed to operate with lower supply voltages.

4. Razavi 2.2: For  $\frac{W}{L} = \frac{50}{0.5}$  and  $|I_D| = 0.5 \text{ mA}$ , calculate the transconductance and output impedance of both NMOS and PMOS devices. Also, find the “intrinsic gain”, defined as  $g_m r_o$ . Use the device data shown in Table 2.1 from Razavi (copied below) and assume  $V_{DD} = 3V$ .

5. Razavi 2.3: Derive expressions for  $g_m r_o$  in terms of  $I_D$  and  $W/L$ . Plot  $g_m r_o$  as a function of  $I_D$  with  $L$  as a parameter. Note that  $\lambda \propto 1/L$ . Use the device data shown in Table 2.1 from Razavi (copied below) and assume  $V_{DD} = 3V$ .

**Table 2.1** Level 1 SPICE models for NMOS and PMOS devices.

<b>NMOS Model</b>			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
<b>PMOS Model</b>			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8