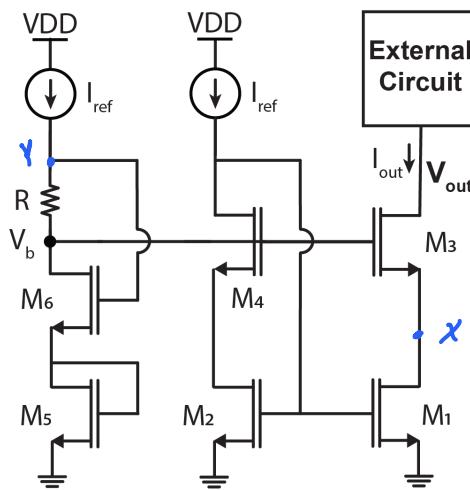


Full Name:
SID :

Grade: /100

Assume for all the problems: $L=65nm$, $VDD=1.2V$, $|V_{th,n,p}|=0.3V$, $\mu_n C_{ox} = \frac{0.5mA}{V^2}$, $\mu_n = 2\mu_p$, $\lambda_p = \lambda_n = 0.1V^{-1}$, $\gamma = 0$ for both NMOS and PMOS devices.

- ~~25~~
1. (20 pts) For the current mirror shown below assume: $I_{Ref} = 100\mu A$ and **all transistors have the V_{od} of 0.2V**.



- a) What should be the ratio of $(W/L)_1/(W/L)_2$ to provide an I_{out} of 1mA?

Since $V_{gs1} = V_{gs2}$ & $V_{ds1} = V_{ds2}$:

$$\frac{(W/L)_1}{(W/L)_2} = \frac{I_{out}}{I_{ref}} = \frac{1mA}{100\mu A} = 10$$

- ~~1 opt.~~ b) What is the minimum V_{out} (as a function of V_b) and also V_b to make sure all devices remain in saturation? What would be minimum acceptable V_{out} for the optimal V_b values?

$$V_{out,Min} = V_b - V_{th} = \underline{\underline{V_b - 0.3V}}$$

$$V_{b,Min} = \underbrace{V_{x,Min}}_{=V_{od}} + V_{S3} = V_{od} + V_{od3} + V_{th} \\ = 0.2 + 0.2 + 0.3 = \underline{\underline{0.7V}}$$

$$\Rightarrow \underline{\underline{V_{out,Min} = 0.4V}}$$

- c) What should be the value of R to ensure V_b will be at the optimal value from part b?

$$V_b = \underbrace{V_T}_{V_{GS5} + V_{GS6}} - R \cdot I_{ref} = 2V_{od} + V_{th}$$

$$\Rightarrow 2V_{od} + 2V_{th} - RI_{ref} = 2V_{od} + V_{th}$$

$$\Rightarrow R = \frac{V_{th}}{I_{ref}} = \frac{0.3V}{0.1mA} = \boxed{3k\Omega}$$

- d) If there will be a fabrication error of 20% increase in the value of the resistor R, will the current mirror be still functional? Why?


if $R \neq 20 \Rightarrow V_b$ will be dropped by $\frac{V_{th} \times 20}{60mV}$

Since M_1 & M_2 were biased by V_b at the

edge of triode saturation, drop in V_b pushes M_1 & M_2 to go to triode & current mirror will not function properly any more.

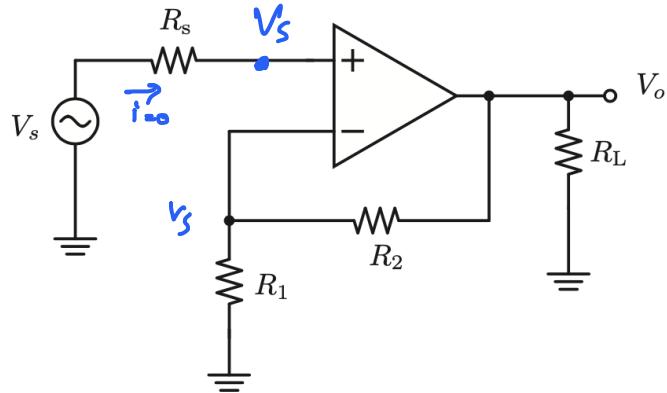2. (35 pts) An op-amp is configured to provide gain (V_o/V_s) of 5V/V to a $R_L = 1k\Omega$ load. Model the op-amp with the following parameters:

- $R_{in} = \infty$ (ideal)
- $R_{out} = 0$ (ideal)
- $A_0 = 100$ (not infinite)
- $f_0 = 10MHz$ (not ideal: finite 3dB-bandwidth frequency)



- e) What should be the ratio of R_2/R_1 to achieve the target close-loop gain assuming amplifier has an infinite gain.

$$A_{cl} = 1 + \frac{R_2}{R_1} = 5 \Rightarrow \boxed{\frac{R_2}{R_1} = 4}$$

- f) How does the closed-loop gain change if R_s or R_L changes?

A_{cl} will not be impacted by either R_s nor R_L .

- g) What's the gain error due to the non-infinite gain of amplifier?

$$A_{cl} = \frac{A_0}{1 + A_0 \beta} \approx \frac{1}{\beta} \left(1 - \underbrace{\frac{1}{A_0 \beta}}_{\text{gain error}} \right) \quad \beta = \frac{R_1}{R_1 + R_2} = \frac{1}{5}$$

$$\Rightarrow \text{gain error} = \frac{1}{\frac{1}{5} \times 100} = \frac{1}{20} = 5\%$$

- h) What's the approximate 3dB bandwidth? Hint: You do not need to derive this result but simply state it from what you know about feedback amplifiers.

$GFBW$ product will remain constant.


$$\Rightarrow A_o \times f_o = A_{CL} \times f_{CL}$$

$$\Rightarrow f_{CL} = \frac{100 \times 10\text{MHz}}{2} = \boxed{200\text{MHz}}$$

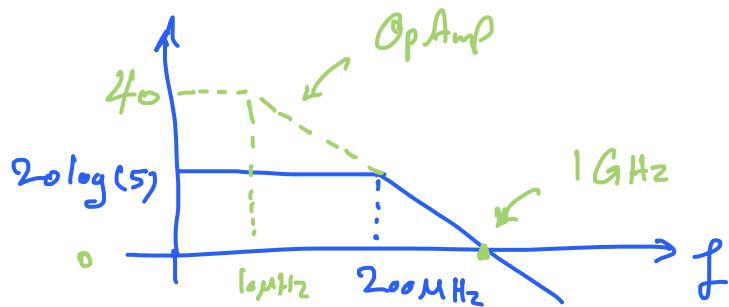- i) What's the unity-gain bandwidth for the closed-loop amplifier?

ω_u remain the same as OpAmp Since $GFBW$ is constant. $\Rightarrow f_u = A_o \times f_{\omega_dB} = 100 \times 10\text{MHz} = \boxed{1\text{GHz}}$

- j) Plot the magnitude Bode plot for closed-loop gain.




- k) if R_{out} of OpAmp is non-zero with a value of 100Ω , calculate the output impedance assuming no loading effect R_1 & R_2 .

$$R_{out,CL} = R_{out} / (1 + \beta A_o)$$

$$= 100 / (1 + \frac{1}{5} \times 100) \approx \boxed{5\Omega}$$

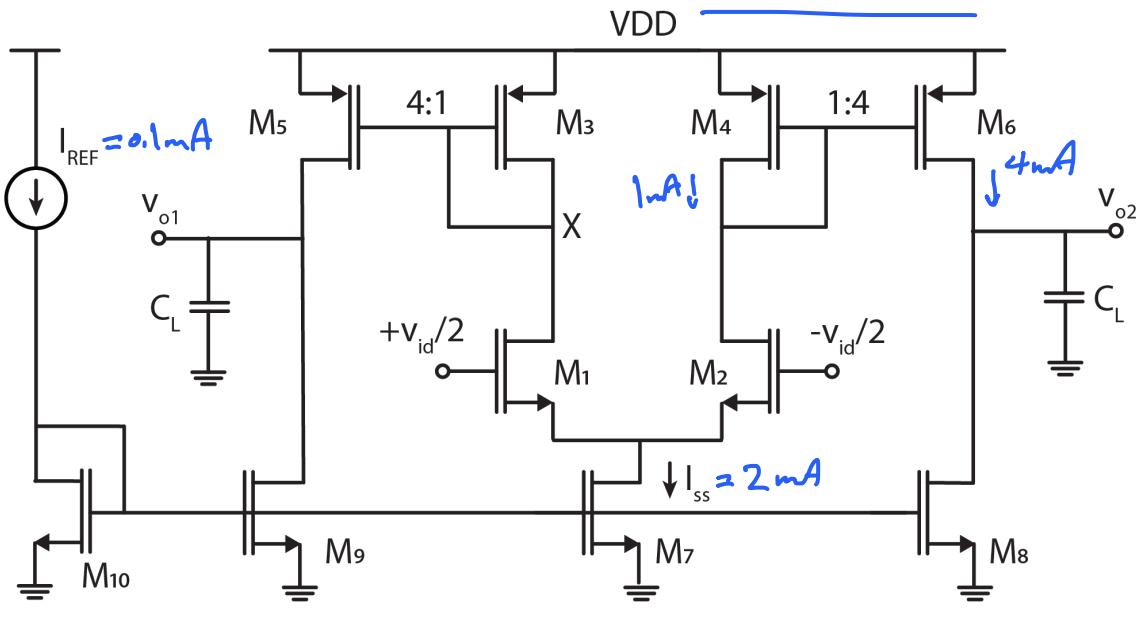3. (40 pts) For the fully differential amplifier shown below all transistors have the nominal channel length of **65nm** and should be biased such that $V_{od} (V_{GS} - V_{th}) = 0.2V$:



$$C_L = \cancel{100fF}, I_{Ref} = 100\mu A$$

a) For I_{ss} to be 2mA, Find W for M₇₋₁₀ transistors.

$$M_{10} : 1.0 \text{ mA} = \frac{1}{2} \times \frac{500 \text{ mN}}{\text{m}^2} \times \left(\frac{W}{L}\right)_{10} \times (0.2)^2 \Rightarrow \left(\frac{W}{L}\right)_{10} = 10 \Rightarrow \underline{W_{10} = 65 \text{ nm}}$$

$$M_F: w_F = w_{10} \times \frac{2}{0.1} = w_{10} \times 20 = \boxed{13 \mu m}$$


$$M_{BB}: \quad w_8 = w_9 = 2 \times \overline{w_7} = 26 \text{ } \mu\text{m}$$

b) Find W for M₃₋₄ transistors.

$$M_{3,4} : 1 \text{ mT} = \frac{1}{2} \times \frac{25 \cdot \mu T}{10^2} \times \frac{W}{L} \times 0.2^2 \Rightarrow \underline{\underline{W_{3,4} = 1 \text{ J/m}}}$$

$$M_{5,6} : \quad w_{5,6} = 4 \times w_{7,4} = \overbrace{52 \mu_m}^{\text{52 } \mu_m}$$

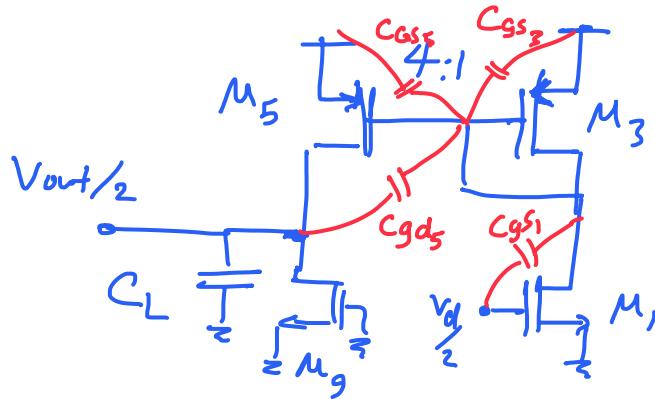c) Draw the half-circuit model for differential mode.



d) Find the small-signal differential gain (V_{out}/V_{id}), where $V_{out} = V_{o1} - V_{o2}$.

$$\begin{aligned}
 A_{de} &= g_m \times 4 \times (V_{o5} \parallel r_{o9}) \\
 &= \frac{2I_1}{V_{od}} \times 4 \times \left(\frac{1}{2I_3} \parallel \frac{1}{2I_9} \right) \\
 &= \frac{2}{0.2} \times 4 \times \frac{1}{2} \times \frac{1}{0.1 \times 4mA} = \boxed{50}
 \end{aligned}$$

e) What's the output differential peak-to-peak output swing?

$$\begin{aligned}
 V_{sw,pp} &= 2 \times \underbrace{V_{sw,pp, \text{single-ended}}}_{V_{DD} - V_{od5} - V_{od9}} = \boxed{1.6V} \\
 V_{DD} - V_{od5} - V_{od9} &= 1.2 - 0.4 = 0.8V
 \end{aligned}$$

f) Estimate output node pole (ω_{out}) location (ignore all other parasitics)

$$\begin{aligned}
 \omega_{out} &= \frac{1}{R_{out} \times C_L} = \frac{10.8G}{125 \times 2 \times 1pF} \\
 \frac{1}{2} \times \frac{1}{0.1 \times 4mA} &= 1.25k\Omega \\
 \Rightarrow \omega_{out} &= 800 \text{ Mrad/s}
 \end{aligned}$$

- g) If M₇₋₆ have $C_{GS} = C_{GD} = 1fF/\mu m$ (per μm unit width), estimate the mirror pole location at node X (ω_X) using the Miller approximation and node-pole associations method. (ignore all other parasitic capacitances)

$$R_X \approx \frac{1}{g_{m_3}} = \frac{V_{od}}{2I_3} = \frac{0.2\text{V}}{2 \times 1\text{mA}} = \frac{100\Omega}{V_X} \frac{V_{out}}{V_X}$$

$$\frac{2I}{V_{od}} = \frac{2 \times 4\text{mA}}{0.2} = 40\text{mS}$$

$$C_X \approx C_{GS_3} + C_{GS_5} + C_{GD_5} \times (1 + A)$$

$$= 1 \frac{fF}{\mu m} (13\mu m + 52\mu m) + 1 \frac{fF}{\mu m} \times 52\mu m \times (1 + g_{m_5} \times R_{out})$$

$$= 65fF + 52fF \times (1 + 40 \times 1.25) = 2.5\text{pF}$$

$$\omega_X = \frac{1}{R_X C_X} = \frac{1}{0.1 \text{ k}\Omega \times 2.5\text{pF}} = \boxed{4 \text{ Grad/s}}$$

- h) Assuming that first pole is dominant in this amplifier, what is the unity-gain bandwidth (ω_u)?

Since $V_{out} \ll \omega_X$, dominant pole will be ω_{out}

$$\Rightarrow \omega_u = A_d \times \omega_{out} = 50 \times 800 \text{ Grad/s}$$

$$\Rightarrow \omega_u = 40 \text{ Grad/s}$$