

EE 332: Devices and Circuits II

Lecture 7: Feedback

Prof. Sajjad Moazeni

smoazeni@uw.edu

Autumn 2022

Feedback Systems


- Feedback Examples?

PID


Oven heating → temp sensor
locks

biological → pacemaker

- Positive vs. Negative Feedback

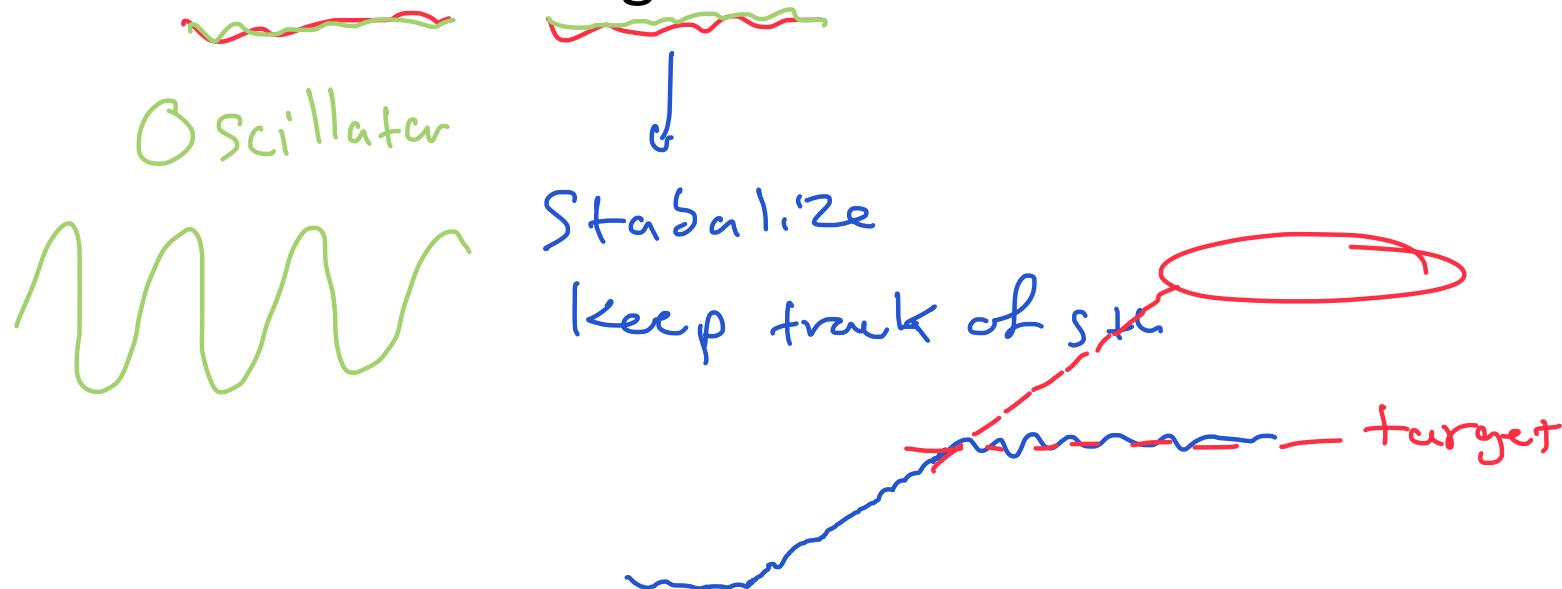

General Considerations

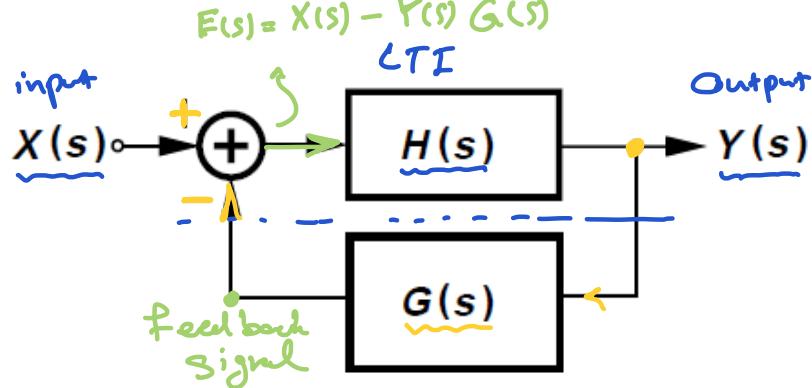

- Above figure shows a negative feedback system
- H : Feedforward network & G : Feedback network
- Feedback error is given by $X(s) - G(s)Y(s)$

$$Y(s) = H(s)[X(s) - G(s)Y(s)]$$


- Thus

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$$

Closed-loop gain $\frac{Y(s)}{X(s)}$ is the *Open-loop gain* $H(s)$ divided by the *loop gain* $1 + G(s)H(s)$.

- $H(s)$ is called the “open-loop” transfer function, $Y(s)/X(s)$ is called the “closed-loop” transfer function, and $G(s)H(s)$ is the “loop-gain”

General Considerations

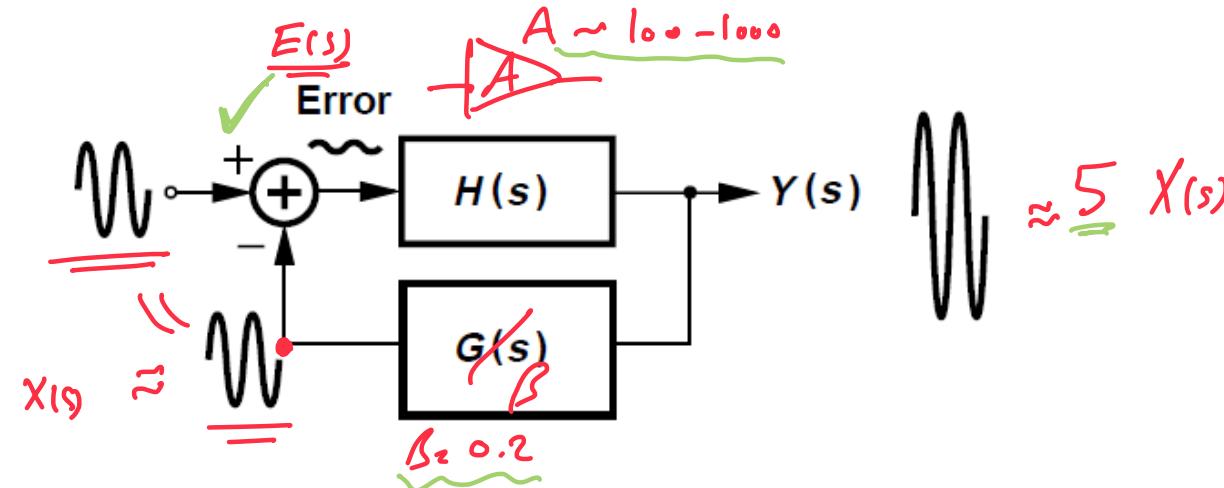


- In most cases, $H(s)$ represents an amplifier and $G(s)$ is a frequency-independent quantity
- In a well-designed negative feedback system, the error term is minimized, making the output of $G(s)$ an “accurate” copy of the input and hence the output of the system a faithful (scaled) replica of the input
- In subsequent developments, $G(s)$ is replaced by a frequency-independent quantity β called the *feedback factor*

4 types of fb circuits


General Considerations

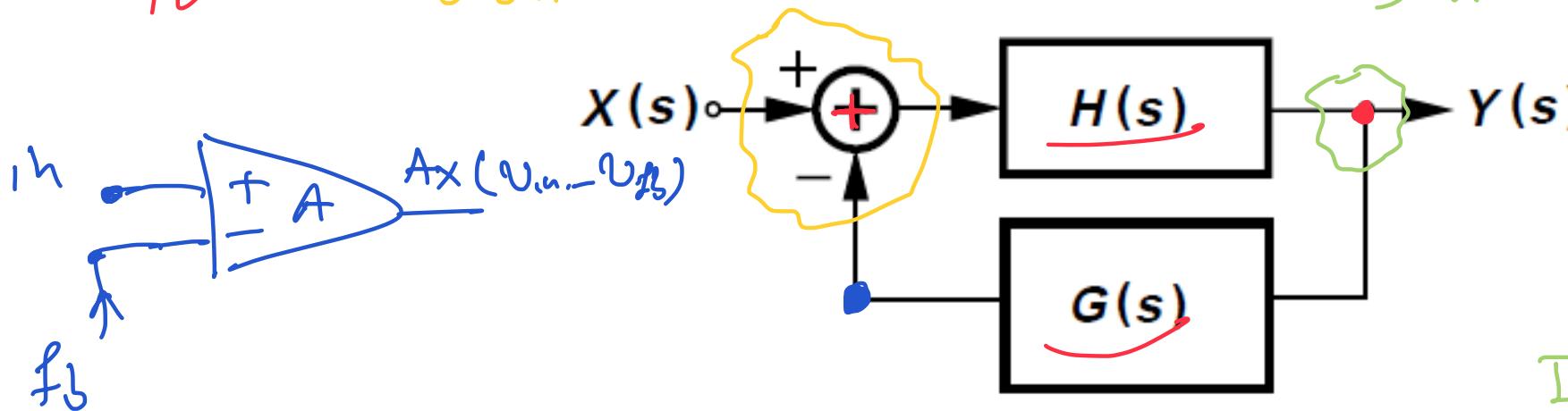* fb circuits Volt or Current domain
Sense : Volt or Current.



- Four elements of a feedback system

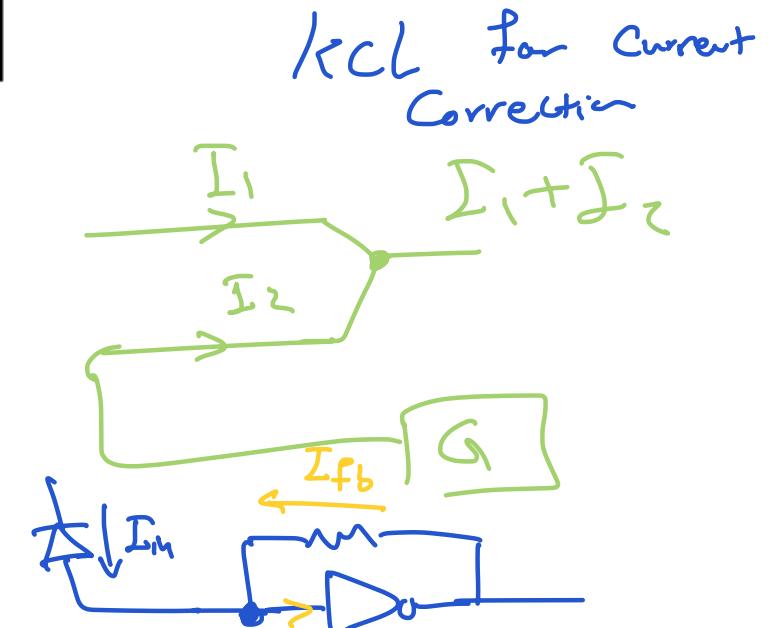- The feedforward amplifier $H(s)$
- A means of sensing the output
- The feedback network $G(s)$
- A means of generating the feedback error, i.e., a subtractor (or an adder)




Properties of Feedback Circuits

$$\beta A = \text{loop gain}$$

$$\beta < 1$$

e.g. $\beta = 0.2$
 $A = 1000$

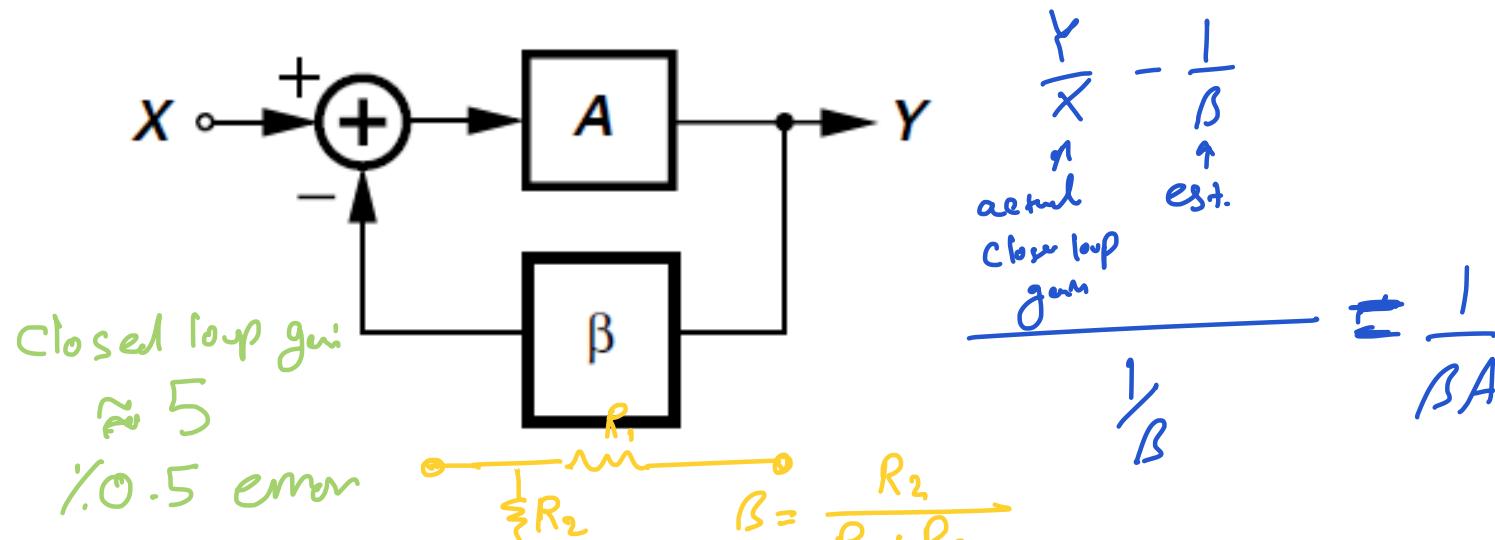

$$\frac{Y}{X} - \frac{1}{\beta}$$

actual
closed loop
gain

est.

$$\frac{1}{\beta} \approx \frac{1}{\beta A}$$

- For a more general case, gain desensitization is quantified by writing


$$\begin{cases} H(s) = A \\ G(s) = \beta \end{cases} \rightarrow \frac{Y}{X} = \frac{A}{1 + \beta A} \approx \frac{1}{\beta} \left(1 - \frac{1}{\beta A} \right)$$

$\frac{1}{\beta A} \approx 0$

$$\boxed{\frac{Y}{X} \approx \frac{1}{\beta}}$$

- It is assumed $\beta A \gg 1$; even if open-loop gain A varies by a factor of 2, Y/X varies by a small percentage since $1/(\beta A) \ll 1$

Properties of Feedback Circuits

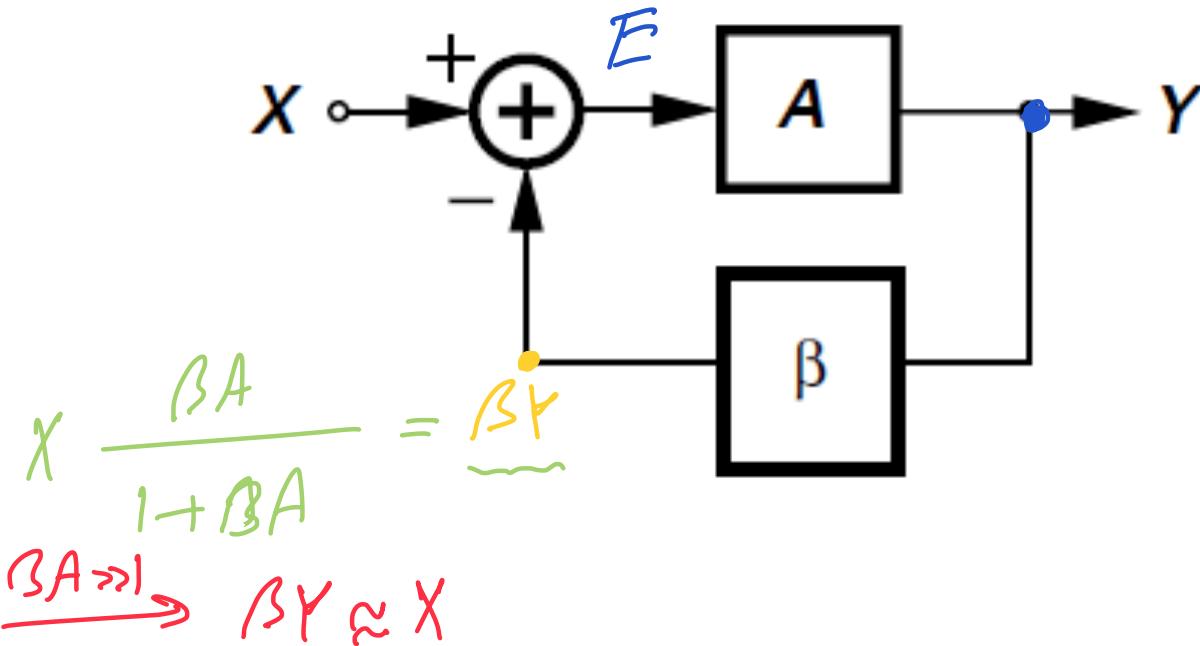

$$\begin{aligned} E &= X - \beta Y \\ &= X - \beta \left(\frac{A}{1 + \beta A} \right) X \\ &= X \left(\frac{1}{1 + \beta A} \right) \end{aligned}$$


if $\beta A \gg 1 \rightarrow E(s) \approx 0$

- The quantity βA is called the “loop gain”
- The output of the feedback network is equal to $\beta Y = X \cdot \beta A / (1 + \beta A)$ approaching X as βA becomes much greater than unity

R_{in} & R_{out}

Types of Amplifiers

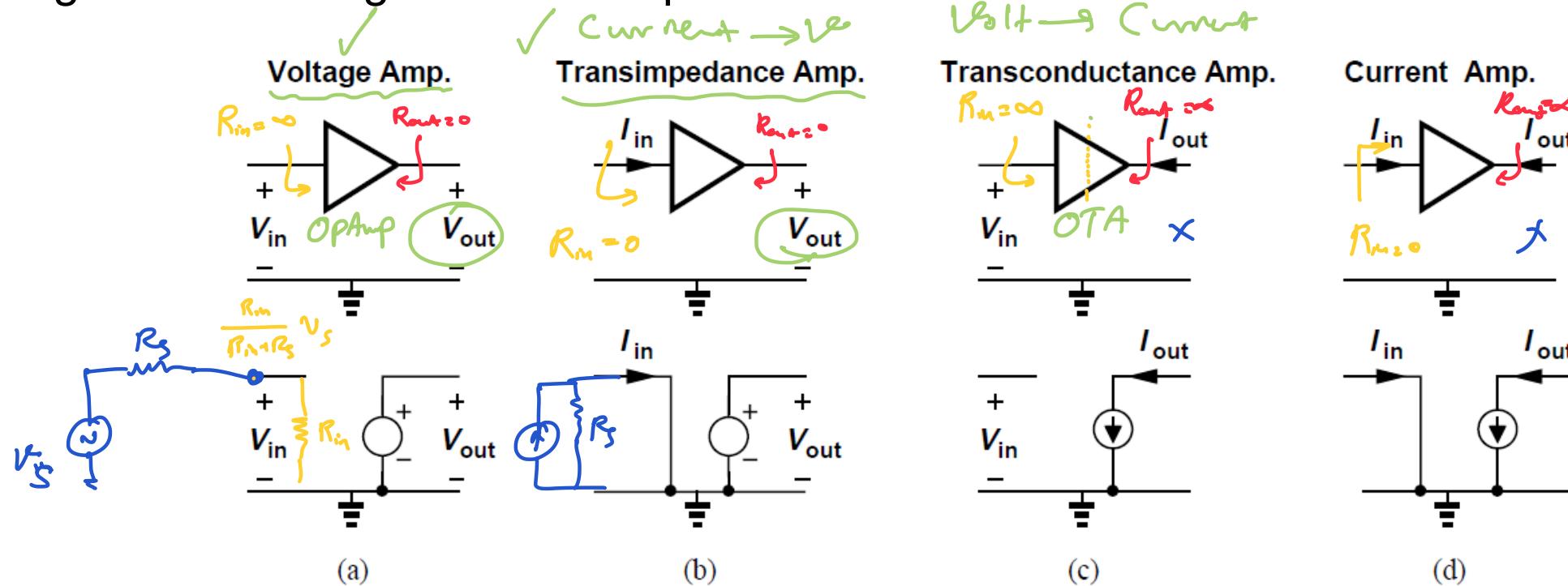
- Four possible amplifier configurations depending on whether the input and output signals are voltage or current quantities



- Figs. (a) – (d) show the four amplifier types with the corresponding idealized models

OpAmp

Volt. Volt.

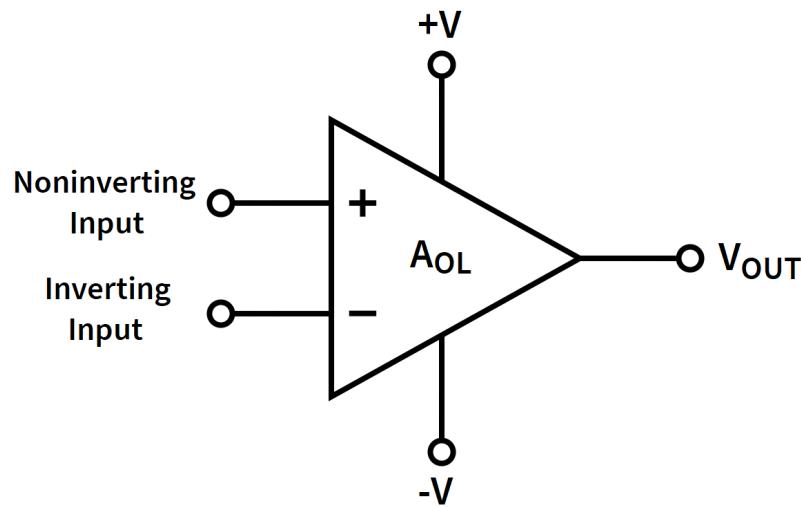


✓ Diff. input

✓ Large gain

OpAmp vs. OTA

V. V

Q. I

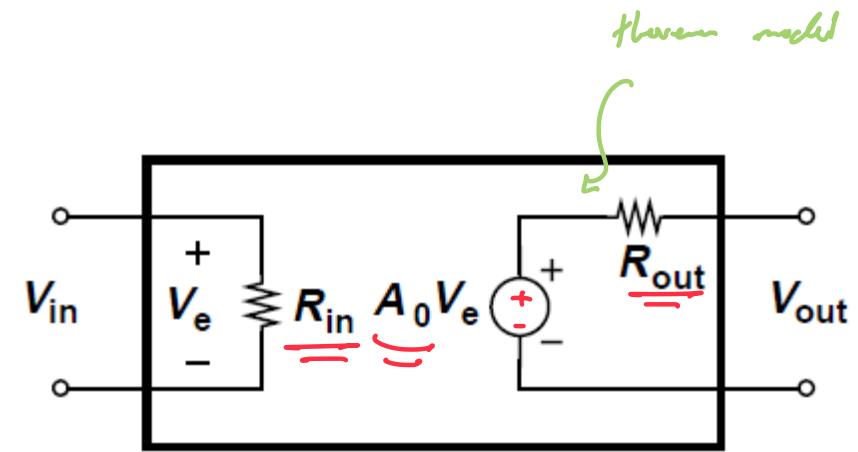


$$A_o(s) = \frac{A_o}{1 + \sum \omega_p}$$




OpAmp

- Providing large-gain by:

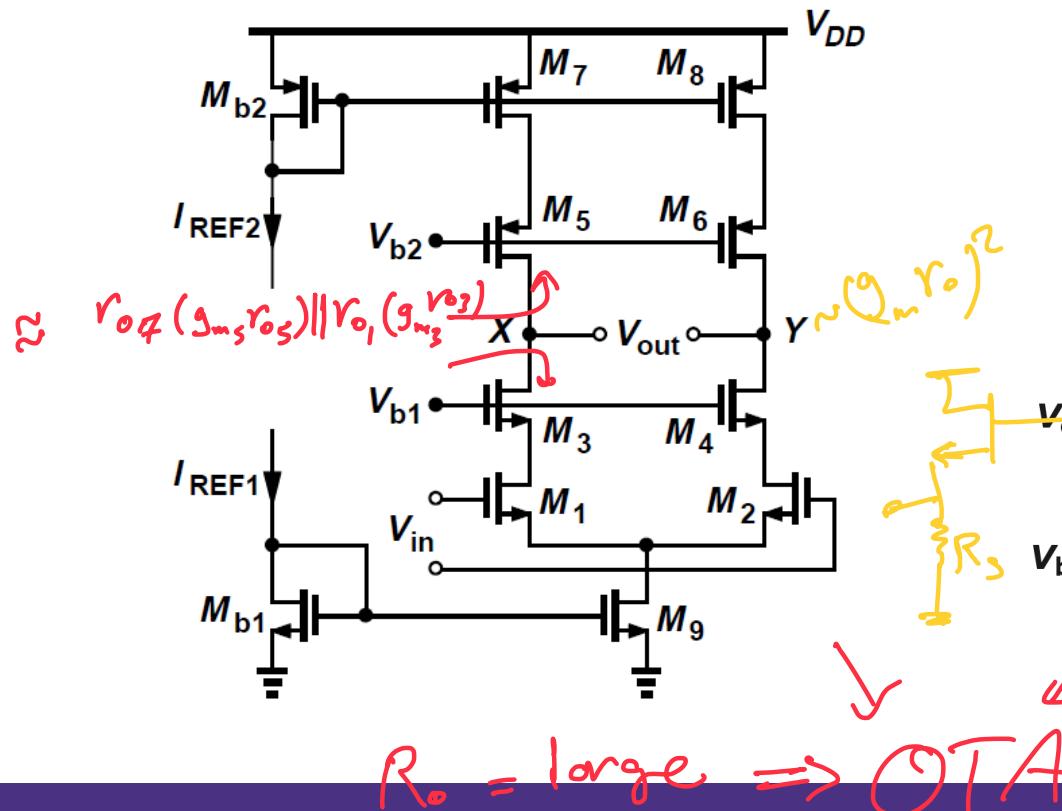- Cascoding technique $\times(g_m r_o)$
- Cascading multiple stages
- etc.




Stability & Compensation

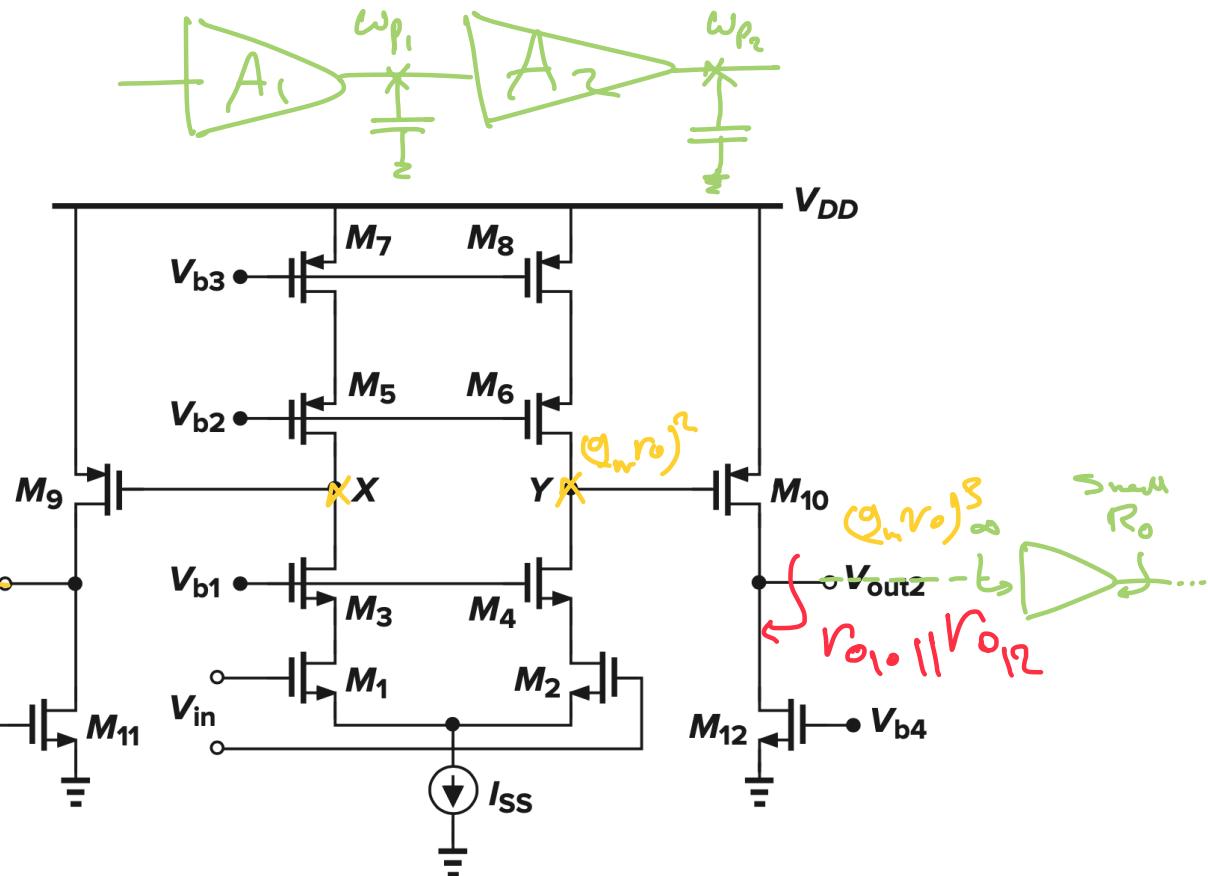

Properties of Feedback Circuits

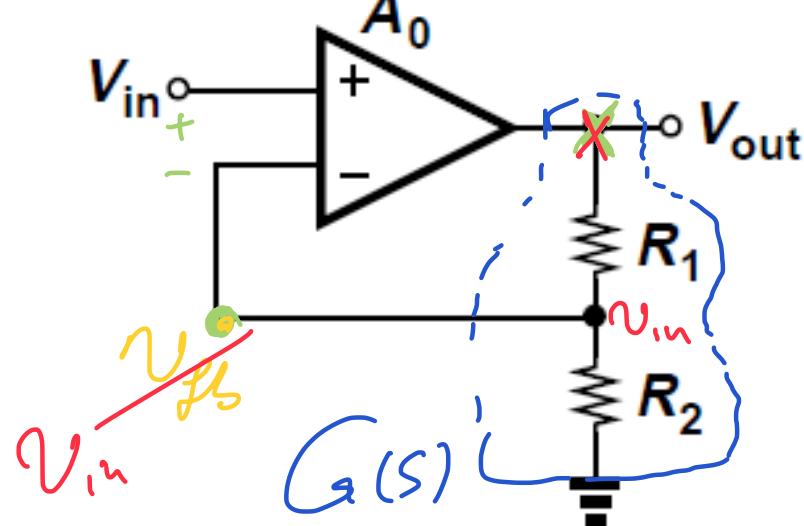- Gain Desensitization: (Non-inverting feedback amplifier example)



Closed-loop gain $\frac{V_{out}}{V_{in}} = ?$

$$\textcircled{A} \quad = \frac{A_0}{1 + \beta A_0}$$

$$\beta A_0 \gg 1 \rightarrow \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

$$\textcircled{B} \quad \frac{R_2}{R_1 + R_2}$$


$$\beta A \gg 1 \Rightarrow E_{eq} = 0 \Rightarrow V_{in} = V_{fb}$$

$$V_{out} \times \frac{R_2}{R_1 + R_2} = V_{in}$$

- Gain can be controlled with higher accuracy unaffected by PVT variations
- Closed-loop gain is less sensitive to device parameters than the open-loop gain, hence called “gain desensitization”


Calculation of Loop Gain
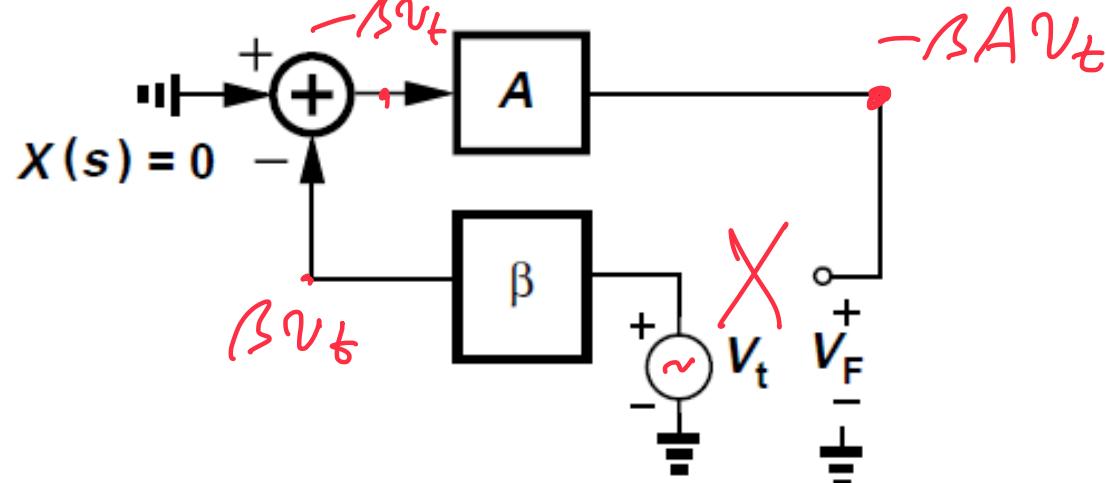
$$\text{Closed loop gain} = \frac{\text{Open loop gain}}{1 + \text{loop gain}}$$



- To calculate the loop gain:
 - Set the main input to (ac) zero
 - Inject a test signal in the “right” direction
 - Follow the signal around the loop and obtain the value that returns to the break point
 - Negative of the transfer function thus obtained is the loop gain
- Loop gain is a dimensionless quantity
- In above figure, $V_t \beta (-1) A = V_F$ and hence $V_F/V_t = \underline{-\beta A}$

Calculation of Loop Gain: Example

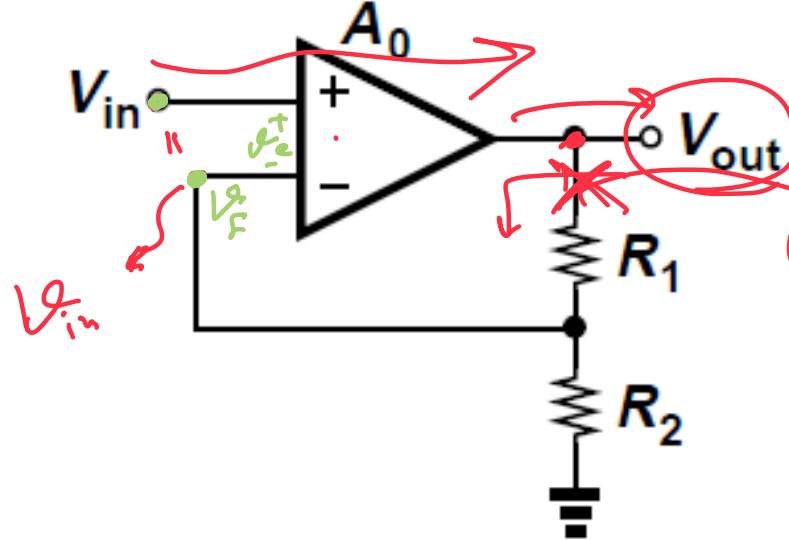

$$\text{Loop gain} = -A_0 \times \frac{R_2}{R_1 + R_2}$$


Open loop = A_0

OpAmp gain
≠

$$\text{Closed-loop gain} = \frac{\text{Open loop gain}}{1 + \text{loop gain}}$$

Calculation of Loop Gain: Example

(inverting feedback amplifier example)

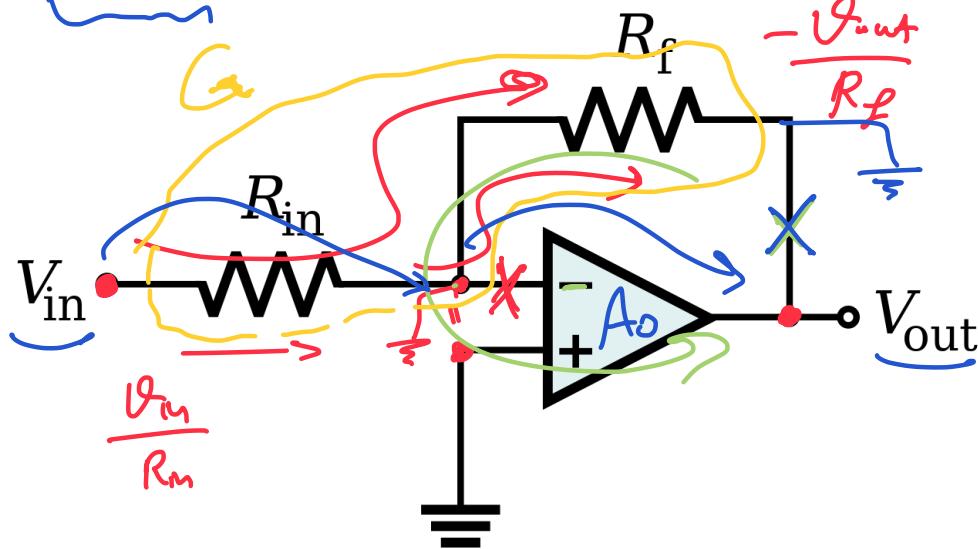

$$\text{input} + \text{Amp} = 0 \Rightarrow V_- = V_+$$

$$\Rightarrow V_- = V_0$$

$$\text{Open loop gain} = \frac{-R_f}{R_{in} + R_f} \times A$$

$$\text{loop gain} = \frac{-R_m}{R_{in} + R_f} A_o \quad \neq \text{open loop gain}$$

$\text{C.L. gain} = ?$

$\text{A} \quad \frac{-R_f}{R_{in} + R_f} A_o \quad \cancel{A_o}$

$\Rightarrow \frac{1 + \frac{R_m}{R_{in} + R_f} A_o}{1 + \cancel{\beta A_o}} \quad \cancel{\text{loop gain}}$

$\Rightarrow \frac{1 + \frac{R_m}{R_{in} + R_f} A_o}{1 + \frac{R_f}{R_m}}$

$\text{C.L. gain} \Rightarrow \frac{V_{in}}{R_m} = \frac{-V_{out}}{R_f}$


$\Rightarrow \boxed{\text{C.L. gain} = -\frac{R_f}{R_m}}$

Sense and Return Mechanisms

Correction

- Placing a circuit in a feedback loop requires sensing an output signal and returning a fraction of it to the summing node at the input
- * • Four types of feedback:
 -  **Voltage-Voltage** (We only cover this type in our lecture, Sec. 8.2.1)
 - Voltage-Current
 - Current-Current
 - Current-Voltage
- **First term is the quantity sensed at the output, and the second term is the type of signal returned to the input**

Voltage-Voltage Feedback

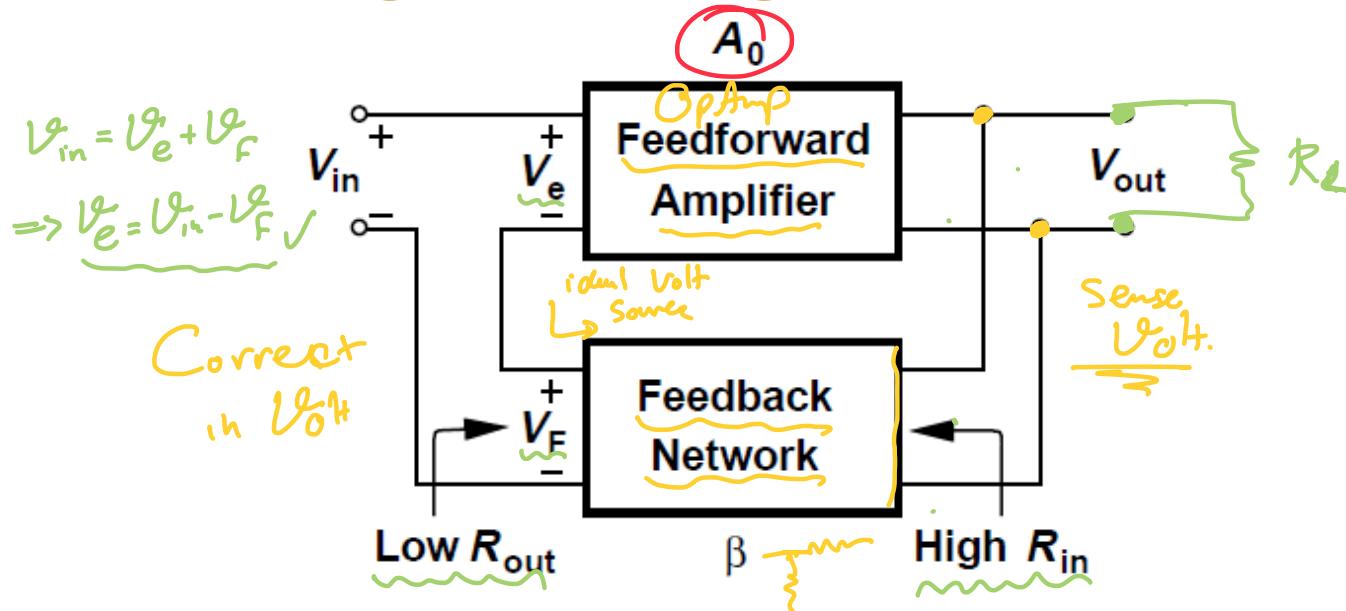

- Also called “series-shunt” feedback; first term refers to the *input* connection and second to the *output* connection



- We can write $V_F = \beta V_{out}$, $V_e = V_{in} - V_F$, $V_{out} = A_0(V_{in} - \beta V_{out})$, and hence

Closed-loop gain

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \beta A_0}$$

- βA_0 is the loop gain and the overall gain has dropped by $\underline{1 + \beta A_0} \gg 1$

Voltage-Voltage Feedback

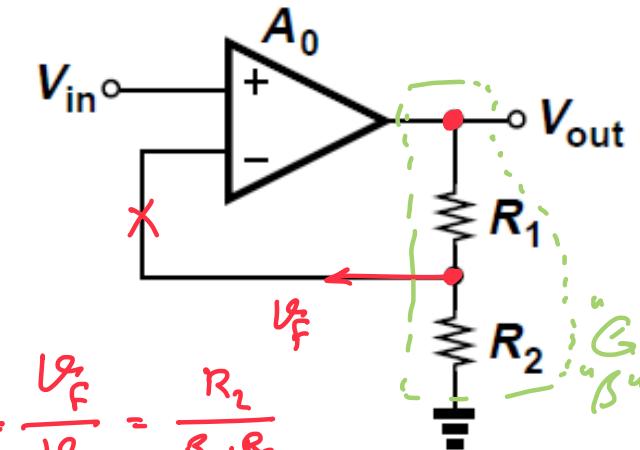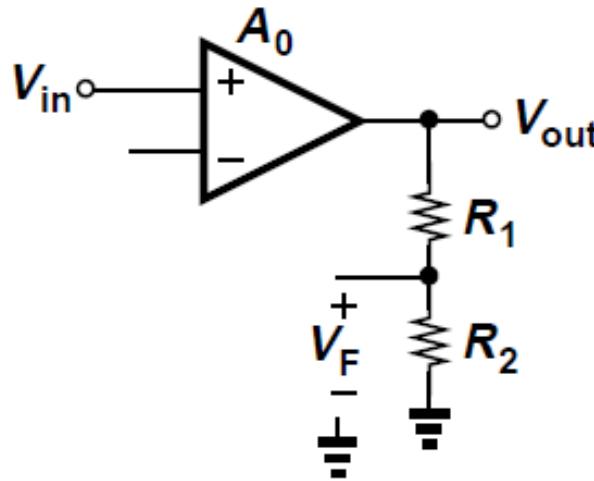


$$\beta = \frac{V_F}{V_{out}} = \frac{R_2}{R_1 + R_2}$$

- As an example of voltage-voltage feedback, a differential voltage amplifier with single-ended output can be used as the forward amplifier and a resistive divider as the feedback network [Fig. (a)]
- The sensed voltage V_F is placed in series with the input to perform subtraction of voltages

Properties of Feedback Circuits


- Terminal Impedance Modification (output impedance)

R_{out} w/o feedback
is R_{out} !

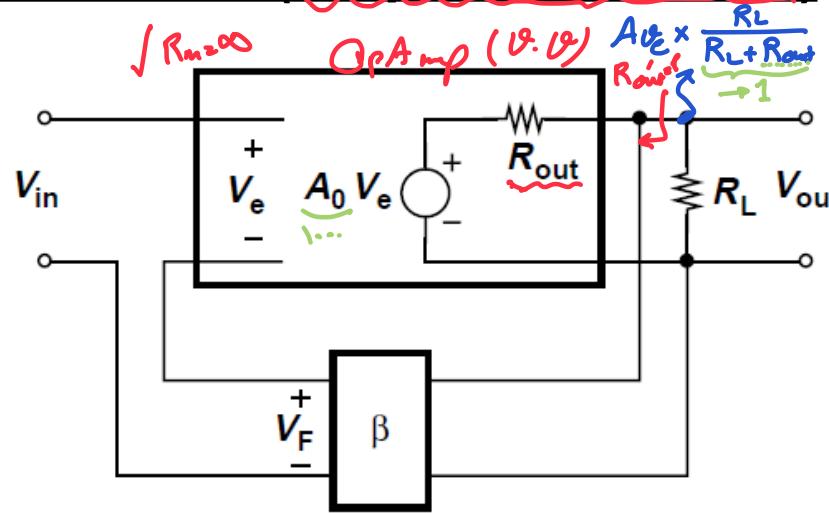

- If output is loaded by resistor R_L , in open-loop configuration, output decreases in proportion to $R_L/(R_L+R_{out})$
- In closed-loop V_{out} is maintained as a constant replica of V_{in} regardless of R_L as long as loop gain is much greater than unity
- Circuit “stabilizes” output voltage despite load variations, behaves as a voltage source and exhibits low output impedance

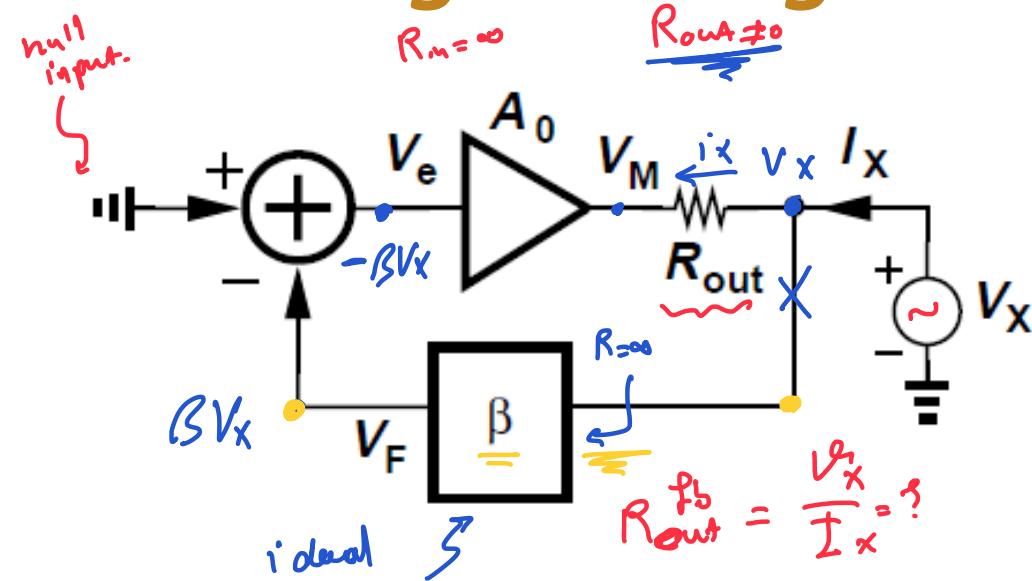Voltage-Voltage Feedback: Output Resistance





$$\begin{aligned} V_F &= A_0 \times -\beta V_x \\ i_x &= \frac{V_x - V_M}{R_{out}} = \frac{V_x - (-A_0 \beta) V_x}{R_{out}} = \frac{(1 + \beta A_0) V_x}{R_{out}} \\ \Rightarrow R_{out}^{\text{fb}} &= \frac{V_x}{i_x} = \frac{R_{out}}{1 + \beta A_0} \end{aligned}$$

↑ + loop gain $\gg 1$

- In the above model, R_{out} represents the output impedance of the amplifier
- Setting input to zero and applying a voltage at the output, we write $V_F = \beta V_x$, $V_e = \beta V_x$, $V_M = \beta A_0 V_x$ and hence $i_x = [V_x - (-\beta A_0 V_x)]/R_{out}$ (*if current drawn by feedback network is neglected)

lowers the R_{out}
 improves R_{out} ✓
 ✓ Output impedance and gain are lowered by the same factor

Calculation of Output Impedance: Example

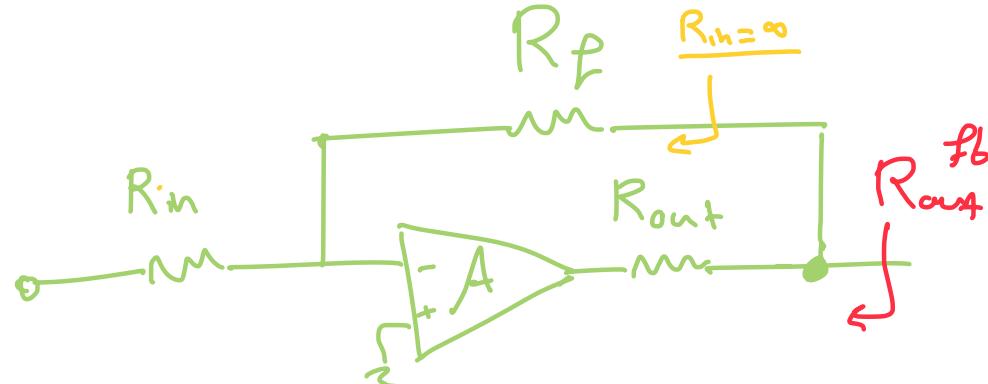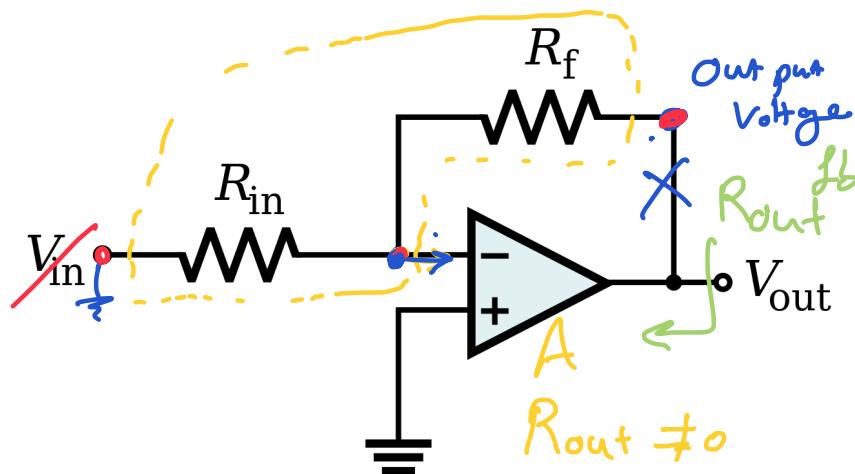

$$\underline{R_{out}} = \frac{R_{out}}{1 + \beta A}$$

$$\beta = \frac{R_{in}}{R_{in} + R_f}$$

KVL & KCL

R_{out}

$\underline{R_{out}}$


$$= (R_{in} + R_f) \ll$$

$$\frac{R_{out}}{1 + \beta A}$$


large
 R_{in} & R_f

Properties of Feedback Circuits

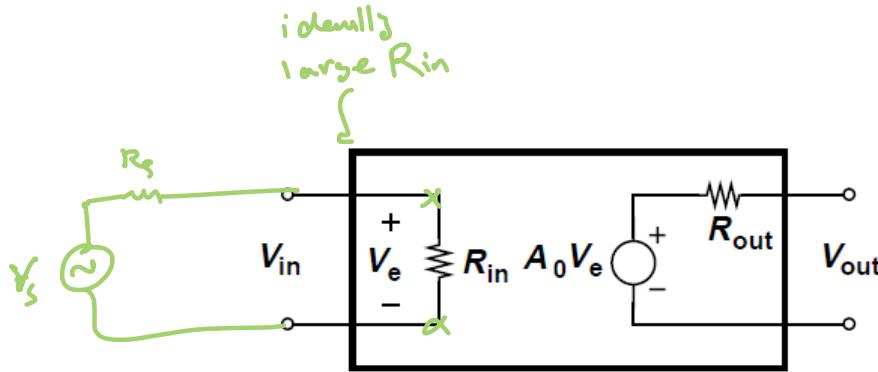- Terminal Impedance Modification (input impedance)




(a)

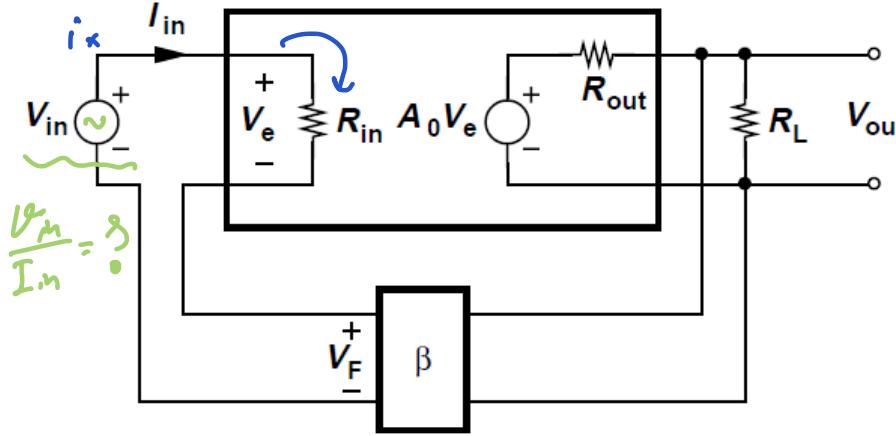

(b)

- Voltage-voltage feedback also modifies input impedance
- In Fig. (a) [open-loop], R_{in} of the forward amplifier sustains the entire V_{in} , whereas only a fraction in Fig. (b) [closed-loop]
- I_{in} is less in the feedback topology compared to open-loop system, suggesting increase in the input impedance

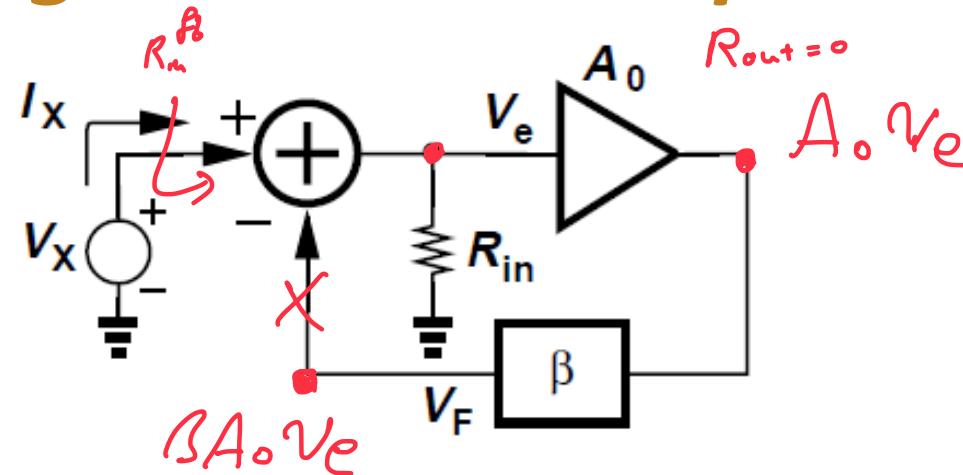Voltage-Voltage Feedback: Input Resistance




- $V_e = I_X R_{in}$ and $V_F = \beta A_0 I_X R_{in}$ \Rightarrow $V_e = V_x - V_F = V_x - \beta A_0 I_X R_{in}$
 - Hence, $I_X R_{in} = V_x - \beta A_0 I_X R_{in}$ and

$$\frac{V_X}{I_X} = R_{in}(1 + \beta A_0)$$

- Input impedance increases by the factor $1+\beta A_0$, bringing the circuit closer to an ideal voltage amplifier
 - Voltage-voltage feedback decreases output impedance and increases input impedance, useful as a buffer stage by a factor of $1 + \text{loop gain}$

Properties of Feedback Circuits

- Terminal Impedance Modification

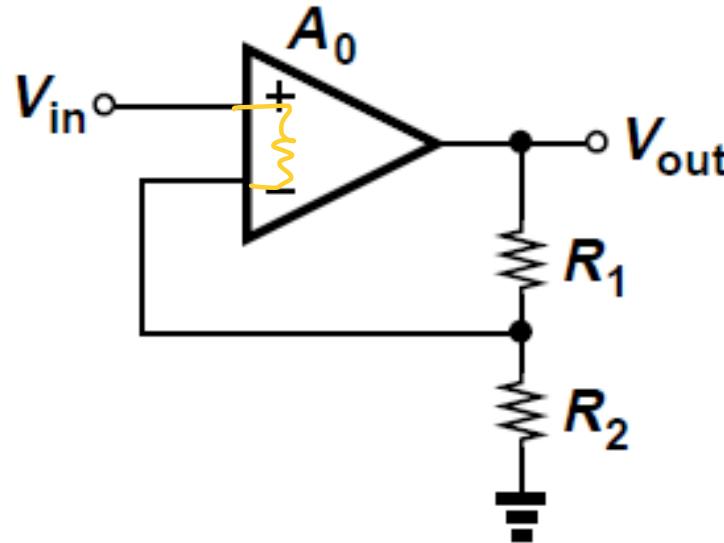

$$R_{in}^f = R_{in} \times (1 + \beta A_0)$$
$$\frac{R_2}{R_1 + R_2}$$



* Large R_1 & R_2

$R_{in, f}$
Feedback
Amp

- Feedback modifies input & output impedances (by a factor of $1 + \beta A$)
- increase or decrease of impedances depend on the feedback type
 - Feedback always improves the impedance ...

Properties of Feedback Circuits

- Bandwidth Modification:

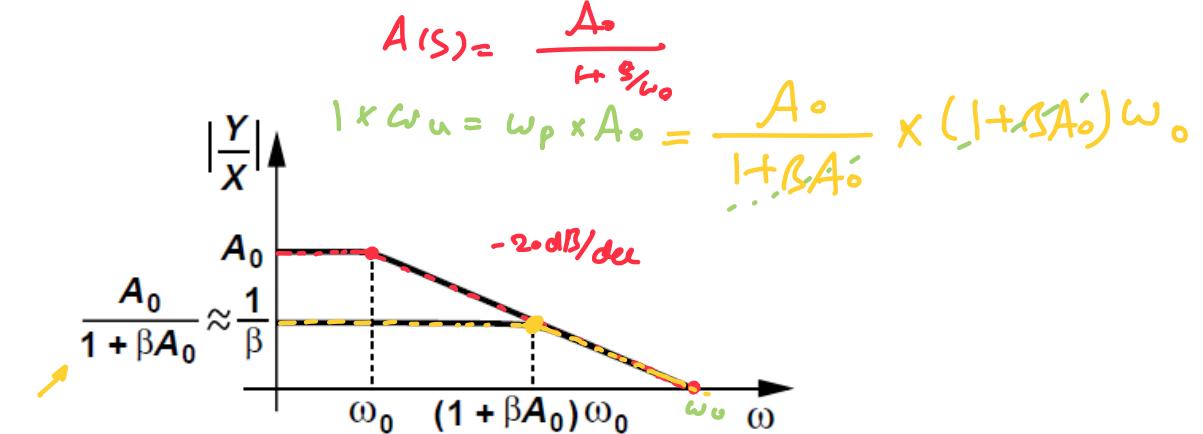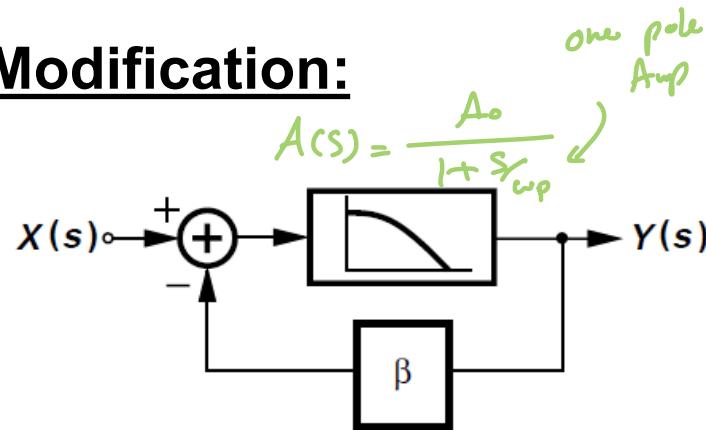

- Suppose the feedforward amplifier above has a one-pole transfer function with A_0 as the low-frequency gain and ω_0 as the 3-dB bandwidth

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

pole of amp.

- Transfer function of the closed-loop system is



$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \beta \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \frac{s}{\omega_0}}} = \frac{A_0}{1 + \beta A_0 + \frac{s}{\omega_0}} = \frac{A_0}{1 + \frac{s}{(1 + \beta A_0) \omega_0}}$$

✓ $\frac{A(s)}{1 + \alpha A(s)}$
 c.l gain
 @ low-freq
 \downarrow
 $\frac{A_0}{1 + \beta A_0}$
 $\omega_p^{cl} = (1 + \beta A_0) \omega_0$

Properties of Feedback Circuits




Bandwidth Modification:

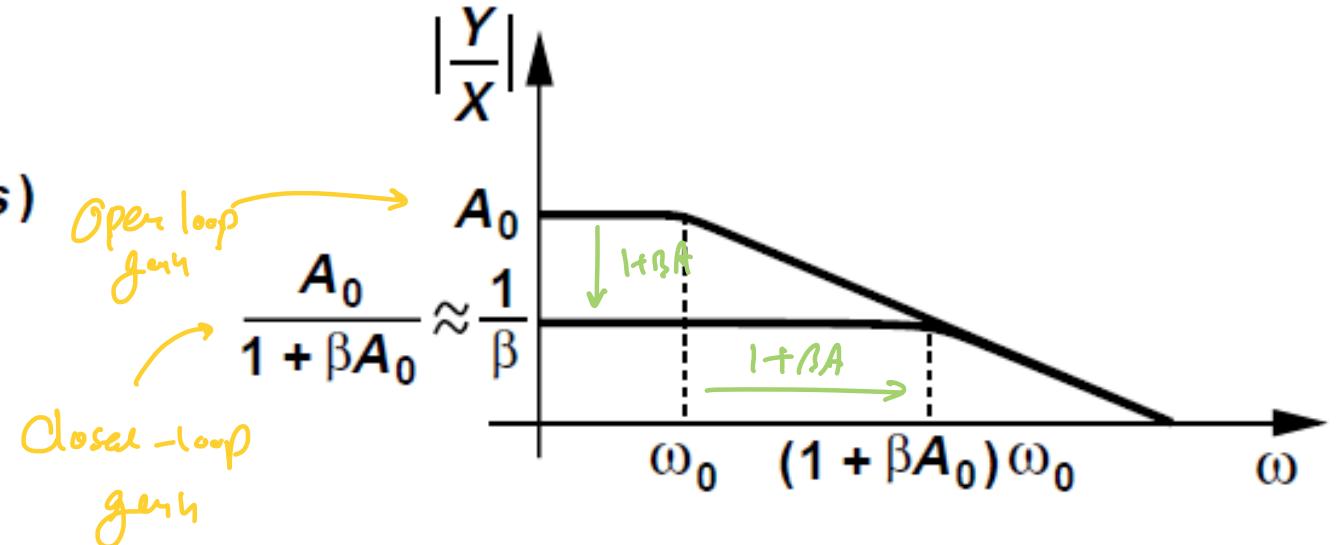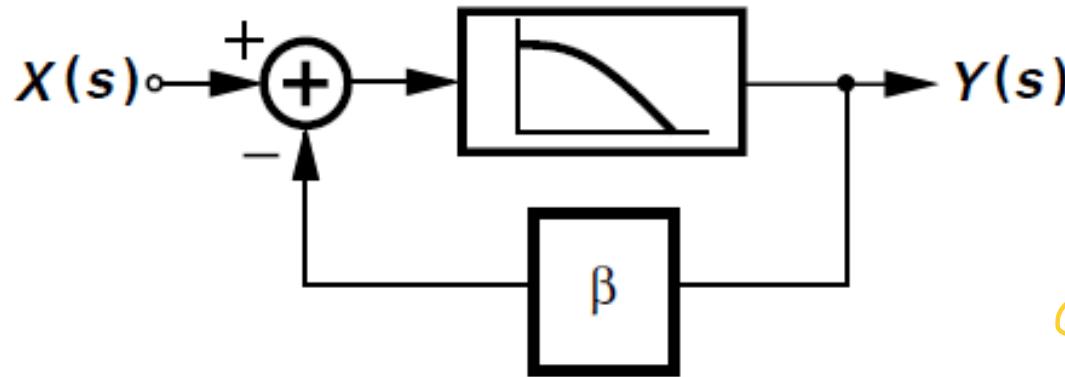

- The closed-loop gain at low frequencies is reduced by a factor of $1 + \beta A_0$, and the 3-dB bandwidth is increased by the same factor, revealing a pole at $(1 + \beta A_0)\omega_0$.
- If A is large enough, closed-loop gain remains approximately equal to $1/\beta$
- At high frequencies, A drops so that βA is comparable to unity and closed-loop gain falls below $1/\beta$

Properties of Feedback Circuits

- Bandwidth Modification:**

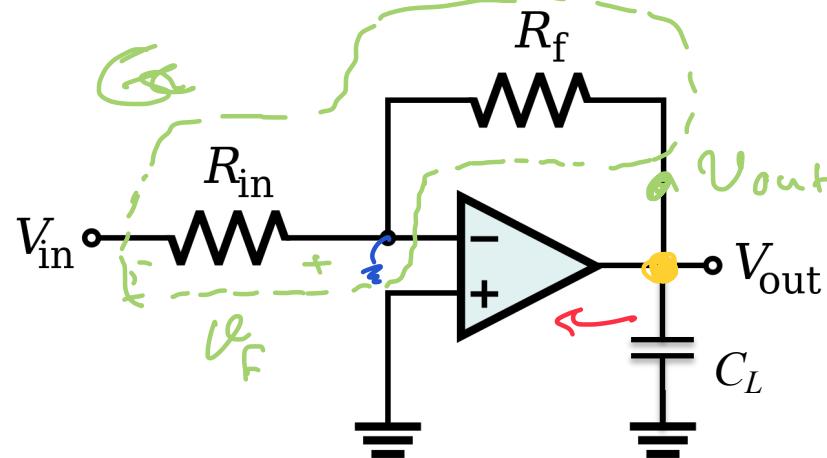

$$A_{Cl} = -\frac{R_f}{R_{in}}$$

$A_{open\ loop} \neq A_o$

$$\left[\begin{array}{l} A_o = -G_m R_{out} \quad \omega_u = \frac{G_m}{C_L} \\ \omega_p = \frac{1}{R_{out} C_L} \\ \beta = \frac{V_F}{V_{out}} = \frac{R_{in}}{R_{in} + R_f} \\ \omega_p^{cl} = \omega_p (1 + \beta A_o) \\ \omega_u^{cl} = \omega_u = \frac{G_m}{C_L} \end{array} \right]$$