 


**1. Cascode Stage.** Design a Cascode amplifier shown in figure below to achieve a gain of 1600. Assume  $V_{DD}=1V$ ,  $V_{th} = 0.3V$ ,  $\lambda_n = 0.2V^{-1}$ ,  $\gamma = 0$ ,  $\mu_n C_{ox} = \frac{100\mu A}{V^2}$ ,  $I_1 = 1mA$ ,  $g_m r_o \gg 1$ .

- Find bias point ( $V_{GS}-V_{th}$  of transistors) to achieve the target gain such that we achieve maximum swing at  $V_{out}$ .
- Find W/L for each transistor.
- Calculate optimal  $V_b$  and  $V_{IN}$  DC bias to maximize output swing. What is this maximum/minimum voltage levels at the output? What is the maximum swing?
- Notice you must generate a specific  $V_b$  externally to maximize the swing. If a lazy designer decides to connect  $V_b$  to  $V_{DD}$  instead, what would be the swing in this case?
- To realize the current source load, we will use a PMOS active load. For PMOS, use the same parameters with  $\lambda_p = 0.2V^{-1}$ ,  $\mu_p C_{ox} = \frac{50\mu A}{V^2}$ . Assume the bias current will remain at 1mA, find the new gain value. What would be the W/L for PMOS if we want to have a  $V_{OD} (V_{GS}-V_{th})$  of 0.1V for this device.
- Repeat part (e) for a PMOS load with 2L gate length.
- It seems like making the PMOS load very large (large W) is beneficial to reduce  $V_{OD}$  and consequently improving the voltage swing. What do you think is the drawback?




*For this HW assume:  $V_{DD}=1V$ ,  $V_{th}=0.3V$ ,  $\mu_n C_{ox} = \frac{200\mu A}{V^2}$ ,  $\lambda = 0.2V^{-1}$ ,  $\gamma = 0$ .*

*\*All the differential amplifiers are symmetric unless we are interested in analyzing mismatch effects in the problem.*

 **2.** Consider the following differential amplifier with  $R_{D1}=R_{D2}=R_D$ :


- If the power consumption is limited to 2mW, what should be  $R_D$  to achieve a differential peak-to-peak swing of 1V?
- Draw the small-signal half-circuits for differential-mode (DM) and common-mode (CM). Clearly determine differential and CM input sources as a result of  $V_{in1}$  and  $V_{in2}$ . (For CM, assume tail current source has an output impedance of  $R_{SS}$ )
- If we need a differential gain of 5, what should be  $g_m$ ,  $V_{OD} (V_{OD} = V_{GS} - V_{TH})$ , and W/L for input devices ( $M_{1,2}$ )? Use  $R_D$  determined in part a.



- d) What is the maximum tolerable differential input voltage range for the circuit to operate in the linear region? (i.e.  $\Delta V_{in1} = ?$ )
- e) For a CM gain of 0.05, what should be the value of  $R_{SS}$ ? ignore output resistance of  $M_{1,2}$  in this part.
- f) If we decide to realize the tail current source with an NMOS, what should be the  $L$  for that device? (Assume that  $\lambda = 0.2V^{-1}$  for  $L = L_0 = 65\text{nm}$ )
- g) What would be  $W$  for this device (tail current NMOS) in order to set its  $V_{OD}$  to 0.2V?
- h) What is the acceptable input common-mode range to keep the amplifier linear after adding the tail device?

3. For the differential pair amplifier circuit shown below: (Write down final answers in terms of key circuit parameters  $g_m$ ,  $r_o$ , etc.)

 - a) Draw the differential and common mode half-circuits. (*Hint*: how can you replace  $R_1$  with two elements such that circuit will be still symmetric to use half-circuit techniques?)
- b) Find the differential and CM small-signal gains.
- c) What's the single-ended and differential output peak-to-peak swings?
- d) What is the CM input range?



4. For a basic differential amplifier (shown in Problem 1), suppose that there are some fluctuations/noise sources on the supply, namely,  $V_{dd}$  that can be modeled as an AC voltage source.

- a) Does this supply cause the differential output to change? How about the CM at each output?
- b) Draw the half-circuit model to find the impact of such a supply noise source at the output.
- c) Calculate the resultant output CM voltage due to the supply noise (in terms of circuit parameters, no need for numerical answers!)
- d) If the  $R_{DS}$  have  $\Delta R_D$  mismatch, what would be the impact of this noise source on the differential output voltage?

5. We can make a differential pair amplifier with PMOS input devices as shown below. Suppose circuits are completely symmetric ( $R_{DS}$  are equal,  $M_{1,2}$  are similar, and each tail current source requires minimum of  $V_{od}$  to operate)

- a) What is the single-ended and differential output swing?

- b) Draw DM and CM half-circuits. (assume that the tail current source has an output impedance of  $R_{ss}$ )
- c) Calculate DM and CM gains.
- d) What is the acceptable input CM range?
- e) Compare the results from (d) with the NMOS diff pair we studied in the class.

